



ESc201, Lecture 10: Sinusoidal steady state analysis - Power

$$p = (1/2)V_m I_m \cos(\phi_v - \phi_i) \\ + (1/2)V_m I_m \cos(\phi_v - \phi_i) \cdot \cos(2\omega t) - (1/2)V_m I_m \sin(\phi_v - \phi_i) \cdot \sin(2\omega t)$$


Hence p (Instantaneous Power) = $P + P \cdot \cos(2\omega t) - Q \cdot \sin(2\omega t)$

and Q (Reactive Power) = $V_{rms} I_{rms} \cdot \sin(\theta)$

Complex Power is $S = P + jQ = V_{rms} I_{rms}^* \angle(\phi_v - \phi_i)$.

And $|S| = \sqrt{P^2 + Q^2}$ is the (Apparent Power) in units of [V.A]

Inductive and Capacitive loads

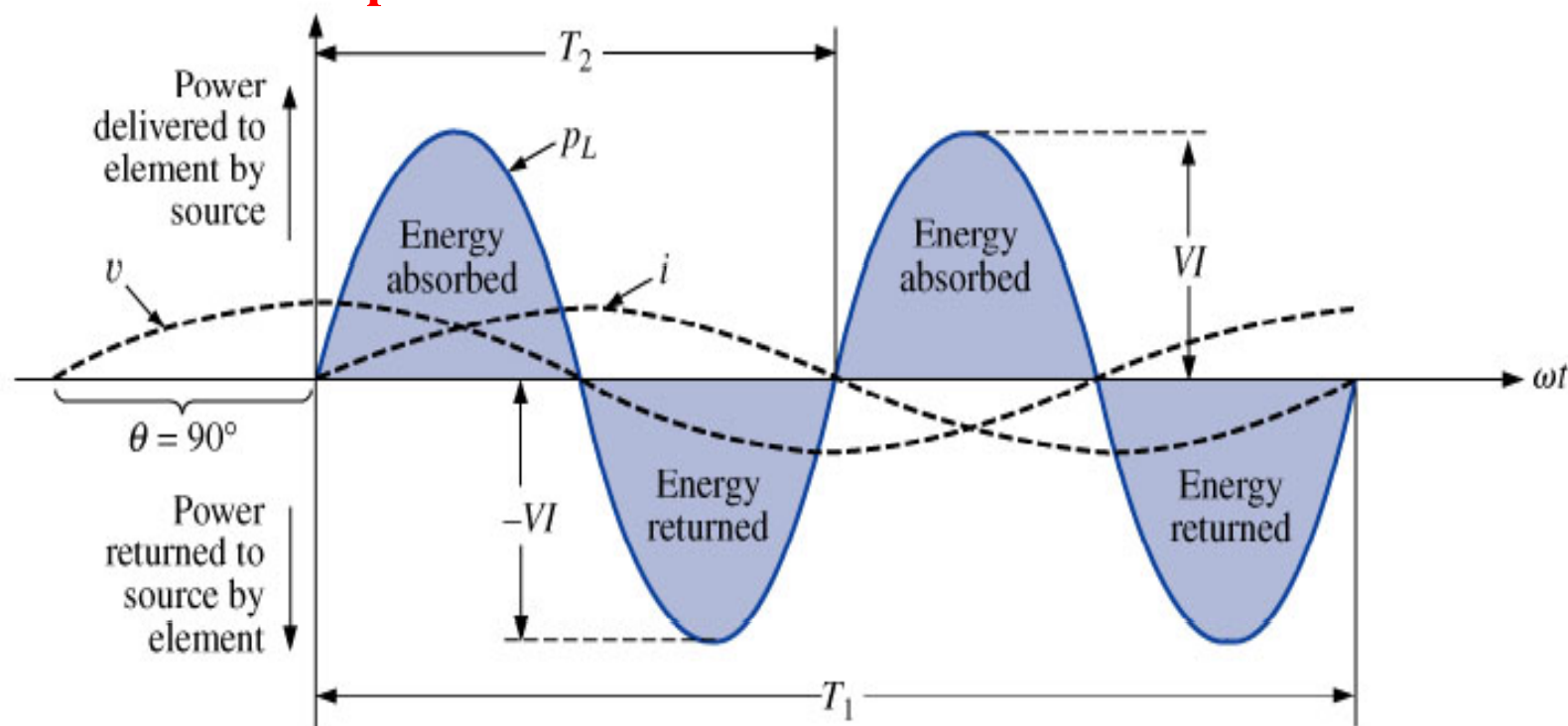


From: Ketan Rajawat



ESc201, Lecture 10: Sinusoidal steady state analysis - Power

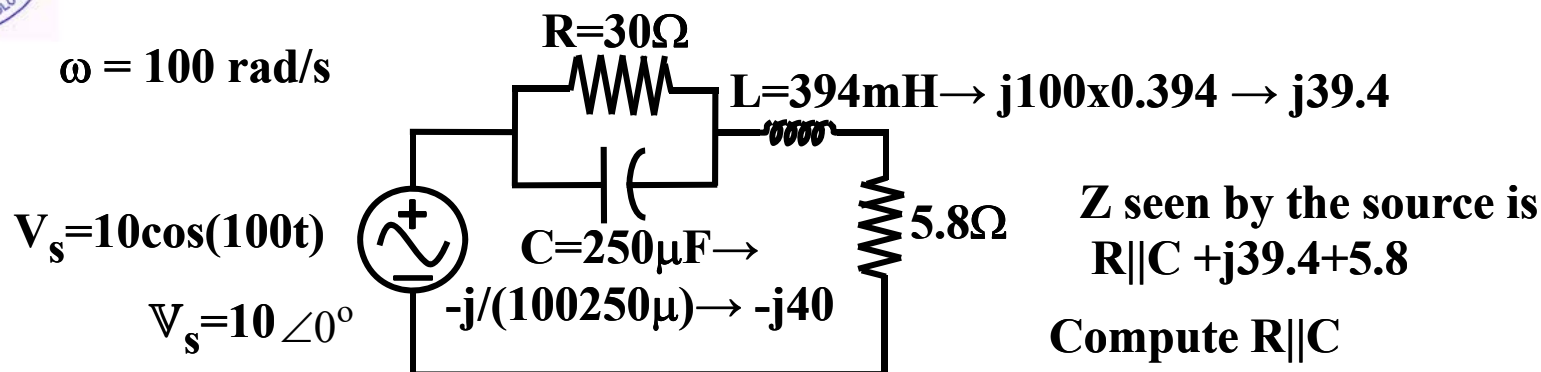Complex Power, Average Power, & Reactive Power delivered by the Source



$$30 \parallel -j40 = \frac{30 \times (-j40)}{30 - j40} = \frac{1200 \angle (-90^\circ)}{50 \angle (-53.13^\circ)} = 24 \angle (-36.9^\circ) = 19.2 - j14.41 \Omega$$

$$\tilde{Z} = 19.2 - j14.41 + j39.4 + 5.8 = 25 + j25 = 35.36 \angle 45^\circ$$

$$\tilde{I}_Z = \frac{10 \angle 0^\circ}{35.36 \angle 45^\circ} = 0.283 \angle -45^\circ = 0.2\sqrt{2} \angle -45^\circ, \quad \tilde{I}_s = -\tilde{I}_Z$$

$$\tilde{S}_s = -\frac{1}{2} \tilde{V}_s \tilde{I}_s^* = -\frac{(10 \angle 0^\circ)(0.2\sqrt{2} \angle -45^\circ)}{2} = -1.0 - j1.0 \text{ VA}$$

$$\tilde{S}_s(\text{Supplying}) = 1.0 + j1.0 \text{ VA (Complex Power)}$$

$$P (\text{Average Power}) = 1 \text{ W}$$


$$Q (\text{Reactive Power}) = 1 \text{ VAR}$$

$$\rightarrow |\tilde{S}_s(\text{Supplying})| = \sqrt{1^2 + 1^2} = \sqrt{2} = \sqrt{P^2 + Q^2}$$



ESc201, Lecture 11: 2-Port Network

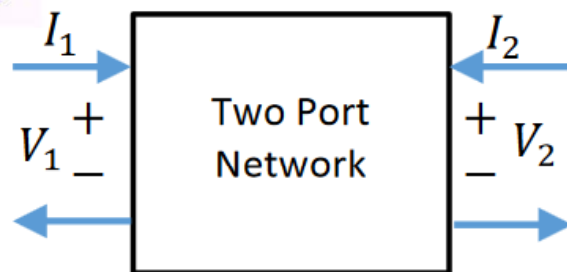Most of the times one is only interested in finding out how the current/voltage changes in a particular element when one input is varied. This is the underlying principle of a 2-port model. The most general description of a 2-port network is carried out in the complex frequency “s” domain. Where $s = \alpha \pm j\omega$.



Z-Parameters $V_1 = z_{11}I_1 + z_{12}I_2$ $V_2 = z_{21}I_1 + z_{22}I_2$ $[Z][I] = [V]$

For a 2-Port Network [Z] is a 2x2 matrix.

$$z_{11} \left(\begin{array}{c} \text{Open circuit} \\ \text{Input Impedance} \end{array} \right) = \frac{V_1}{I_1} \bigg|_{I_2=0} \quad (\Omega)$$

$$z_{22} \left(\begin{array}{c} \text{Open circuit} \\ \text{Output Impedance} \end{array} \right) = \frac{V_2}{I_2} \bigg|_{I_1=0} \quad (\Omega)$$

$$z_{12} \left(\begin{array}{c} \text{Reverse open circuit} \\ \text{Transimpedance} \end{array} \right) = \frac{V_1}{I_2} \bigg|_{I_1=0} \quad (\Omega)$$

$$z_{21} \left(\begin{array}{c} \text{Forward open circuit} \\ \text{Transimpedance} \end{array} \right) = \frac{V_2}{I_1} \bigg|_{I_2=0} \quad (\Omega)$$

Y-Parameters $[Y][V] = [I]$

$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$

$$y_{11} \left(\begin{array}{c} \text{Short Circuit} \\ \text{Input Admittance} \end{array} \right) = \frac{I_1}{V_1} \bigg|_{V_2=0} \quad (\text{S})$$

$$y_{12} \left(\begin{array}{c} \text{Reverse Short Circuit} \\ \text{Transconductance} \end{array} \right) = \frac{I_1}{V_2} \bigg|_{V_1=0} \quad (\text{S})$$

$$y_{21} \left(\begin{array}{c} \text{Forward Short Circuit} \\ \text{Transconductance} \end{array} \right) = \frac{I_2}{V_1} \bigg|_{V_2=0} \quad (\text{S})$$

$$y_{22} \left(\begin{array}{c} \text{Short Circuit} \\ \text{Output Admittance} \end{array} \right) = \frac{I_2}{V_2} \bigg|_{V_1=0} \quad (\text{S})$$

For a 2-Port Network [Y] is also a 2x2 matrix.




ESc201, Lecture 11: 2-Port Network and Frequency Response

(HYBRID) h-Parameters – specially used for amplifiers

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

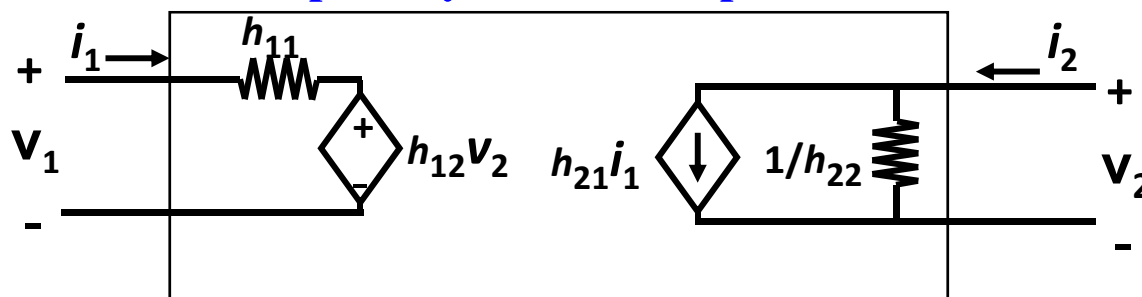

$$h_{11} \left(\begin{array}{c} \text{Short circuit} \\ \text{input Impedance} \end{array} \right) = \frac{V_1}{I_1} \bigg|_{V_2=0} \quad (\Omega)$$


$$h_{12} \left(\begin{array}{c} \text{Reverse open circuit} \\ \text{Voltage Gain} \end{array} \right) = \frac{V_1}{V_2} \bigg|_{I_1=0}$$

$$h_{21} \left(\begin{array}{c} \text{Forward short circuit} \\ \text{Current gain} \end{array} \right) = \frac{I_2}{I_1} \bigg|_{V_2=0}$$

$$h_{22} \left(\begin{array}{c} \text{Open circuit} \\ \text{output Admittance} \end{array} \right) = \frac{I_2}{V_2} \bigg|_{I_1=0} \quad (\text{S})$$

ABCD-Parameters
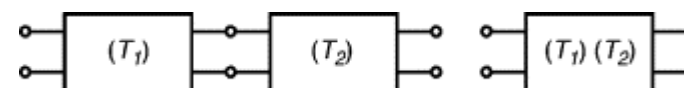
$$\begin{aligned} V_1 &= AV_2 + B(-I_2) \\ I_1 &= CV_2 + D(-I_2) \end{aligned} \quad \begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$



$$\begin{aligned} V_{1a} &= A_a V_{2a} + B_a(-I_{2a}) \\ I_{1a} &= C_a V_{2a} + D_a(-I_{2a}) \end{aligned}$$

$$\begin{aligned} V_{2a} &= V_{1b} & V_{1b} &= A_b V_{2b} + B_b(-I_{2b}) \\ -I_{2a} &= I_{1b} & I_{1b} &= C_b V_{2b} + D_b(-I_{2b}) \end{aligned} \quad \begin{bmatrix} V_{1b} \\ I_{1b} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_b \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix} \quad \begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_a \begin{bmatrix} V_{2a} \\ -I_{2a} \end{bmatrix}$$

$$\begin{bmatrix} V_{1a} \\ I_{1a} \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix}_a \begin{bmatrix} A & B \\ C & D \end{bmatrix}_b \begin{bmatrix} V_{2b} \\ -I_{2b} \end{bmatrix}$$

$$[ABCD]_{\text{cascade}} = [ABCD]_a * [ABCD]_b$$




ESc201, Lecture 11: 2-Port Network

S-Parameters

$$b_1 = S_{11} * a_1 + S_{12} * a_2$$

$$b_2 = S_{21} * a_1 + S_{22} * a_2$$

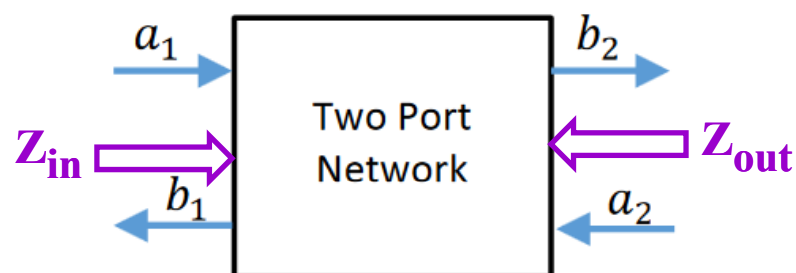

$$S_{11} = \left. \frac{b_1}{a_1} \right|_{a_2=0}$$

$$S_{12} = \left. \frac{b_1}{a_2} \right|_{a_1=0}$$

$$S_{21} = \left. \frac{b_2}{a_1} \right|_{a_2=0}$$

$$S_{22} = \left. \frac{b_2}{a_2} \right|_{a_1=0}$$

Easy to
define but
how to
implement?

At “low” frequencies, one can completely characterize a linear device or network using an impedance matrix, which relates the currents and voltages at each device terminal to the currents and voltages at all other terminals. **But, at microwave frequencies, it is difficult to measure total currents and voltages.**

Instead, one can measure the magnitude and phase of each of the two transmission line waves $V^+(z)$ and $V^-(z)$.

OR can measure the input power at any port “a” and the reflected power at the same port as “b”.


If a source is connected to port 1 and a load Z_L is connected to port 2 and $Z_{out} = Z_L$ then it is called a matched load and there is no reflection of the wave from the load, or $a_2 = 0$.

Similarly if the source is placed at port 2 and load at port 1 such that $Z_{in} = Z_L$ then $a_1 = 0$. Typically, it is much more difficult to determine/measure the scattering parameters of the form S_{nn} , as opposed to scattering parameters of the form S_{mn} (where $m \neq n$) where there is only an exiting wave from port m.

T-Parameters

$$b_1 = T_{11} * a_2 + T_{12} * b_2$$

$$a_1 = T_{21} * a_2 + T_{22} * b_2$$

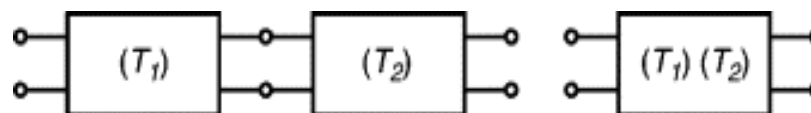

$$[T]_{cascade} = [T]_a * [T]_b$$



ESc201, Lecture 11: 2-Port Network

***a*-Parameters**

$$V_1 = a_{11}V_2 - a_{12}I_2, I_1 = a_{21}V_2 - a_{22}I_2$$

$$a_{11} \left(\begin{array}{c} \text{Voltage} \\ \text{Gain} \end{array} \right) = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad a_{22} \left(\begin{array}{c} \text{Current} \\ \text{Gain} \end{array} \right) = - \left. \frac{I_1}{I_2} \right|_{V_2=0}$$

$$a_{12} \left(\begin{array}{c} \text{Trans} \\ \text{Impedance} \end{array} \right) = - \left. \frac{V_1}{I_2} \right|_{V_2=0} \quad a_{21} \left(\begin{array}{c} \text{Trans} \\ \text{Admittance} \end{array} \right) = \left. \frac{I_1}{V_2} \right|_{V_2=0}$$

***g*-Parameters**

$$I_1 = g_{11}V_1 + g_{12}I_2$$

$$V_2 = g_{21}V_1 + g_{22}I_2$$

$$g_{11} \left(\begin{array}{c} \text{Open circuit} \\ \text{Input Admittance} \end{array} \right) = \left. \frac{I_1}{V_1} \right|_{I_2=0} \quad g_{12} \left(\begin{array}{c} \text{Reverse Short circuit} \\ \text{Current gain} \end{array} \right) = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

$$g_{21} \left(\begin{array}{c} \text{Forward open circuit} \\ \text{Voltage gain} \end{array} \right) = \left. \frac{V_2}{V_1} \right|_{I_2=0} \quad g_{22} \left(\begin{array}{c} \text{Short circuit} \\ \text{Output Impedance} \end{array} \right) = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

***b*-Parameters**

$$V_2 = b_{11}V_1 - b_{12}I_1$$

$$I_2 = b_{21}V_1 - b_{22}I_1$$

$$b_{11} = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad b_{12} = - \left. \frac{V_2}{I_1} \right|_{V_1=0}$$

$$b_{21} = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad b_{22} = - \left. \frac{I_2}{I_1} \right|_{V_1=0}$$



ESc201, Lecture 11: 2-Port Network

Parametric Conversion Table :

(Δ is the determinant of the matrix)

$$z_{11} = \frac{y_{22}}{\Delta y} = \frac{a_{11}}{a_{21}} = \frac{b_{22}}{b_{21}} = \frac{\Delta h}{h_{22}} = \frac{1}{g_{11}}$$

$$z_{12} = -\frac{y_{12}}{\Delta y} = \frac{\Delta a}{a_{21}} = \frac{1}{b_{21}} = \frac{h_{12}}{h_{22}} = -\frac{g_{12}}{g_{11}}$$

$$z_{21} = -\frac{y_{21}}{\Delta y} = \frac{1}{a_{21}} = \frac{\Delta b}{b_{21}} = -\frac{h_{21}}{h_{22}} = \frac{g_{21}}{g_{11}}$$

$$z_{22} = \frac{y_{11}}{\Delta y} = \frac{a_{22}}{a_{21}} = \frac{b_{11}}{b_{21}} = \frac{1}{h_{22}} = \frac{\Delta g}{g_{11}}$$

$$y_{11} = \frac{z_{22}}{\Delta z} = \frac{a_{22}}{a_{12}} = \frac{b_{11}}{b_{12}} = \frac{1}{h_{11}} = \frac{\Delta g}{g_{22}}$$

$$y_{12} = -\frac{z_{12}}{\Delta z} = -\frac{\Delta a}{a_{12}} = -\frac{1}{b_{12}} = -\frac{h_{12}}{h_{11}} = \frac{g_{12}}{g_{22}}$$

$$y_{21} = -\frac{z_{21}}{\Delta z} = -\frac{1}{a_{12}} = -\frac{\Delta b}{b_{12}} = \frac{h_{21}}{h_{11}} = -\frac{g_{21}}{g_{22}}$$

$$y_{22} = \frac{z_{11}}{\Delta z} = \frac{a_{11}}{a_{12}} = \frac{b_{22}}{b_{12}} = \frac{\Delta h}{h_{11}} = \frac{1}{g_{22}}$$

Conversion for the others are also

(Whenever divided by Δ , $\Delta \neq 0$ is a must condition. there but not as frequently used.

$$h_{11} = \frac{\Delta z}{z_{22}} = \frac{1}{y_{11}} = \frac{a_{12}}{a_{22}} = \frac{b_{12}}{b_{11}} = \frac{g_{22}}{\Delta g}$$

$$h_{12} = \frac{z_{12}}{z_{22}} = -\frac{y_{12}}{y_{11}} = \frac{\Delta a}{a_{22}} = \frac{1}{b_{11}} = -\frac{g_{12}}{\Delta g}$$

$$h_{21} = -\frac{z_{21}}{z_{22}} = \frac{y_{21}}{y_{11}} = -\frac{1}{a_{22}} = -\frac{\Delta b}{b_{11}} = -\frac{g_{21}}{\Delta g}$$

$$h_{22} = \frac{1}{z_{22}} = \frac{\Delta y}{y_{11}} = \frac{a_{21}}{a_{22}} = \frac{b_{21}}{b_{11}} = \frac{g_{11}}{\Delta g}$$

$A = -\Delta h/h_{21}$, $B = -h_{11}/h_{21}$, $C = -h_{22}/h_{21}$, $D = -1/h_{21}$, $[Y] = [Z]^{-1}|_{\Delta z \neq 0}$, $[Z] = [Y]^{-1}|_{\Delta y \neq 0}$