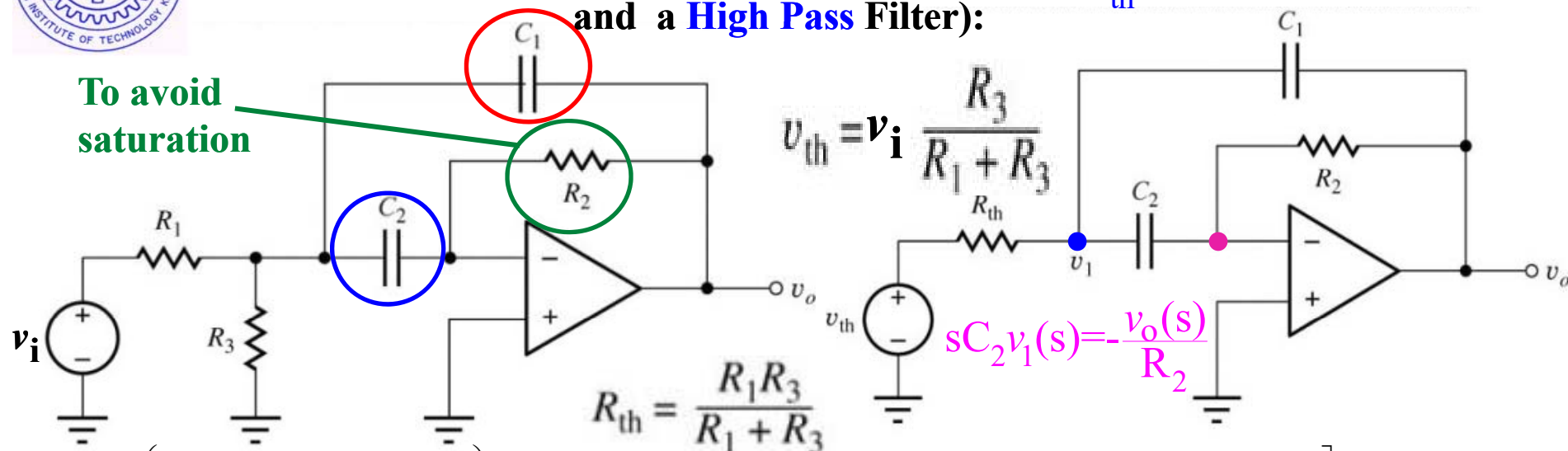




ESc201, Lecture 26: Operational Amplifier Band Pass Filter (Combination of a **Low Pass** and a **High Pass** Filter):

$$\frac{v_{th} - v_1(s)}{R_{th}} = sC_1(v_1(s) - v_o(s)) + sC_2v_1(s)$$




$$\frac{v_{th}}{R_{th}} = \left(s(C_1 + C_2) + \frac{1}{R_{th}} \right) v_1(s) - sC_1v_o(s) = s \left[-(C_1 + C_2) \frac{v_o(s)}{sC_2R_2} - C_1v_o(s) \right] + \frac{v_o(s)}{R_{th}sC_2R_2}$$

$$\omega_o = \frac{1}{\sqrt{R_{th}R_2C_1C_2}} \quad Q = \sqrt{\frac{R_2}{R_{th}}} \frac{\sqrt{C_1C_2}}{C_1 + C_2} \frac{1}{\sqrt{R_2}}$$

$$A_{BP}(s) = \frac{v_o(s)}{v_{th}(s)} = - \sqrt{\frac{R_3}{R_1 + R_3}} \frac{R_2C_2}{R_1C_1} \frac{s\omega_o}{s^2 + s\frac{\omega_o}{Q} + \omega_o^2}$$

For $C_1 = C_2 = C$, and $\omega_o = \frac{1}{C\sqrt{R_{th}R_2}}$

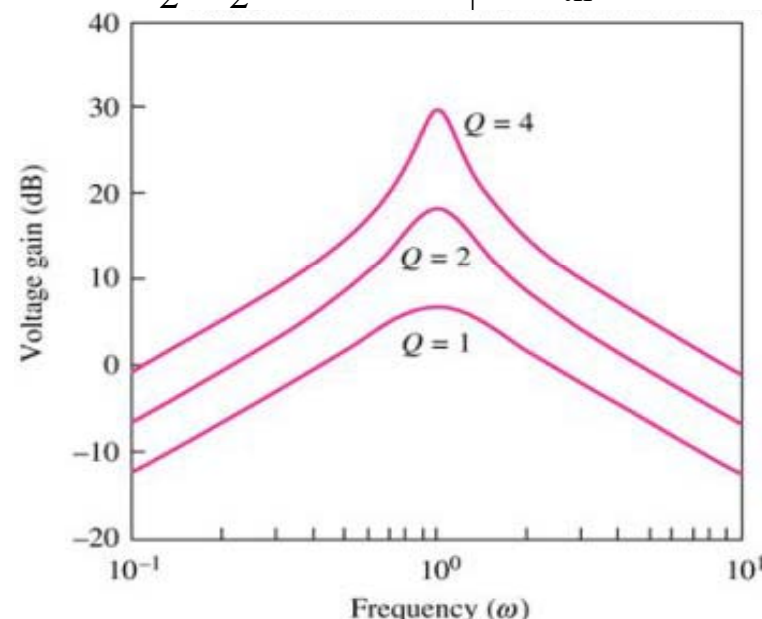
$$BW = \frac{2}{R_2C} \quad \frac{\omega_o}{Q} \propto \frac{1}{R_2}, \text{ and } \omega_o^2 \propto \frac{1}{R_2} \quad Q = \sqrt{\frac{R_2}{R_{th}}}$$





ESc201, Lecture 26: Operational Amplifier Schmitt Trigger:

Positive Feedback – Inverting input

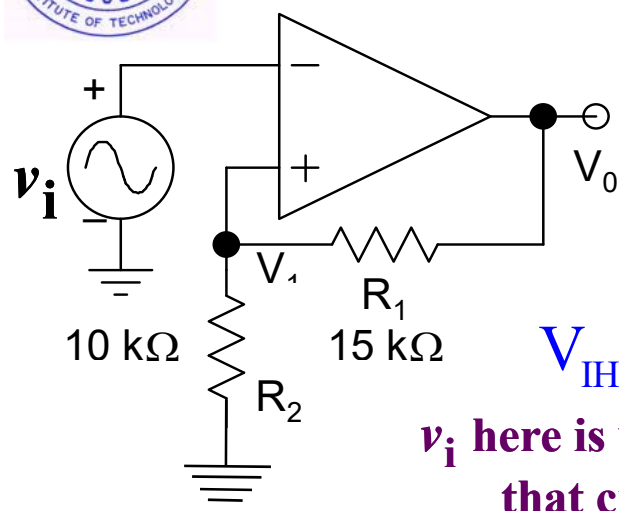

$$v_o = A_v (v_+ - v_-)$$

$$v_+ = v_o \frac{R_2}{R_1 + R_2}$$

$$V_{IH} = +4.8V, V_{IL} = -4.8V$$

v_i here is v_{trigger} the Trigger Signal that creates change of state.

Let the output be high (+12V) and hence input has to be low ($\leq -4.8V$). As v_i increases, nothing happens till v_i reaches 4.8V, when the output toggles from +12V to -12V. So the toggling from V_{OH} to V_{OL} does not happen at the same input. The loop formed is called Hysteresis.

Thus, the circuit has two stable states, giving the name “bistable circuit”. For a change of state at the output, an appropriate trigger signal needs to be applied at the input.

Within the Hysteresis width ($V_{IH} - V_{IL}$), the output is indeterminate and depends on the direction of change of the Trigger input. **Is Hysteresis good or bad? Usually unwanted.**


But imagine the input has noise added. Then Hysteresis prevents the output from chattering - good. Schmitt Trigger acts as an Effective Noise Suppressor

$$v_- > v_+ \Rightarrow v_o = -V_{\text{sat}}$$

$$v_- < v_+ \Rightarrow v_o = +V_{\text{sat}}$$


Let $R_2 = 10k, V_{CC} = +12V, V_{EE} = -12V,$
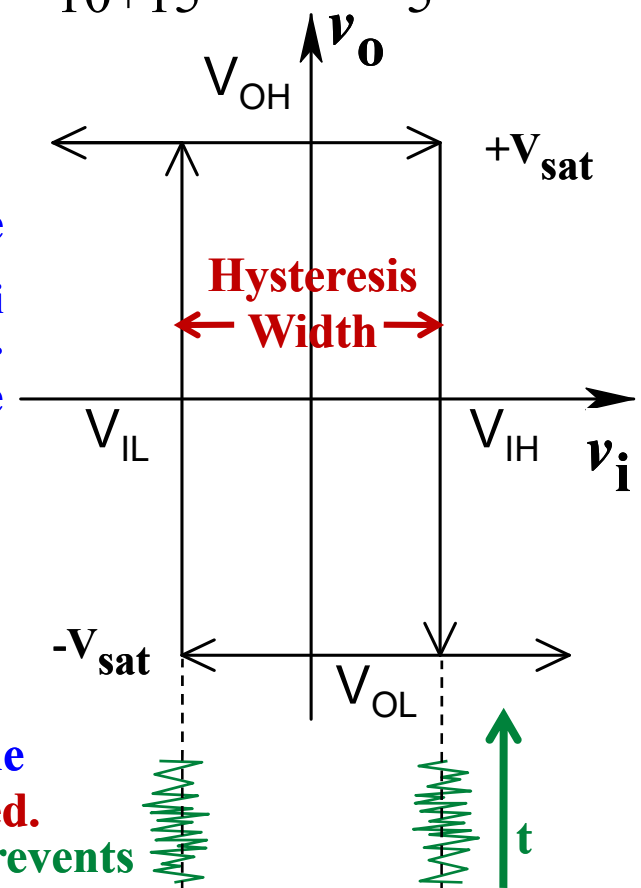
$$v_+ = \pm V_{\text{sat}} \frac{10}{10+15} = \pm 12 \times \frac{2}{5} = \pm 4.8V$$





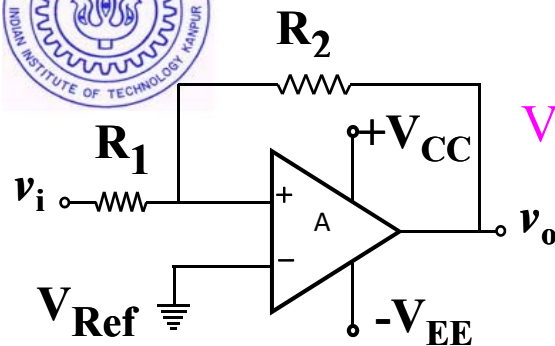ESc201, Lecture 26: Operational Amplifier –Non-Inverting Schmitt Trigger



By Superposition


$$V_+ = \frac{R_2}{R_1 + R_2} v_o + \frac{R_1}{R_1 + R_2} v_i$$

Due to *positive feedback*, the output v_o will be at V_{+sat} for $V_+ > V_-$, and at $-V_{sat}$ for $V_- > V_+$. For $V_- = 0$, if v_o is at V_{+sat} , then no positive of V_i can change the state of the output.


To switch v_o to V_{-sat} , V_+ must be pulled below ground, (which is the potential of V_-) and it would be possible only if v_i goes below $-(R_1/R_2)V_{+sat}$. This corresponds to the Threshold Low (V_{TL}) of the circuit.

Similarly when V_o is at V_{-sat} , to cause a change in the state of the output V_i must be more positive than $-(R_1/R_2)V_{-sat}$. This corresponds to the Threshold High (V_{TH}) of the circuit. ($V_{TH} - V_{TL}$) is then the Hysteresis width.

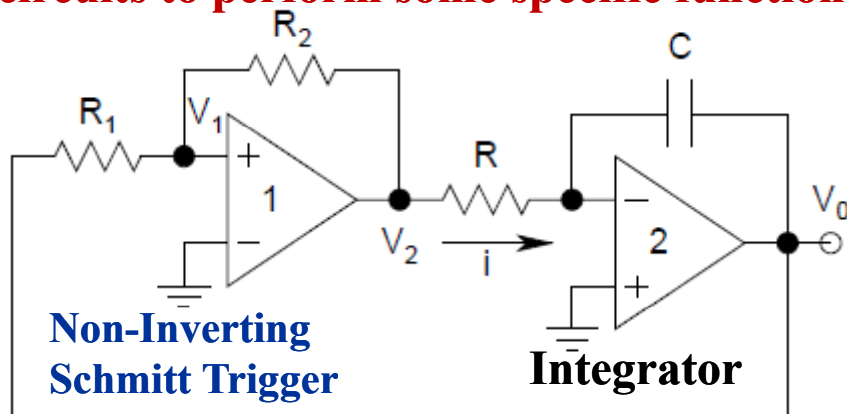This non-inverting Schmitt Trigger circuit is not much used unless it is followed by other circuits to perform some specific functions, for example:



Triangular Wave Generator

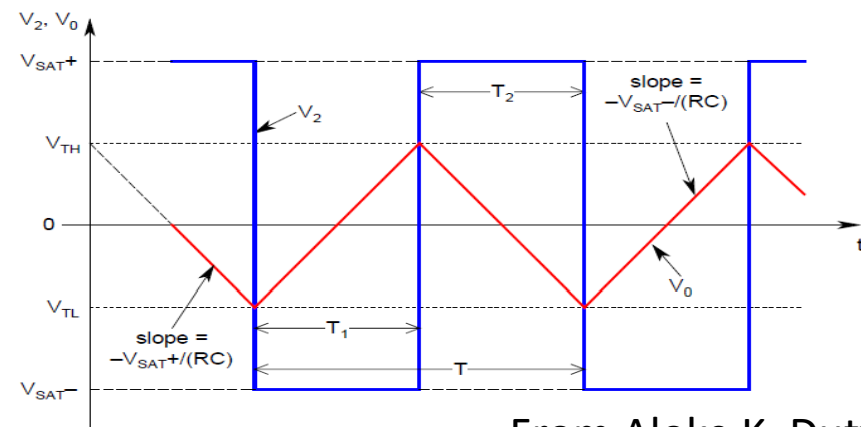


From Alope K. Dutta




ESc201, Lecture 26: Operational Amplifier - Other Applications

A special case of non-inverting amplifier, also called **Voltage Follower** with infinite R_1 and zero R_2 . Hence $A_v = 1$.

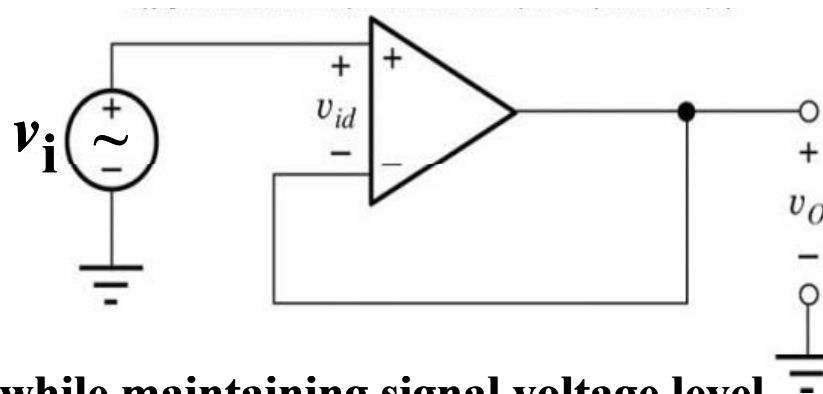Provides excellent impedance-level transformation while maintaining signal voltage level. Ideal voltage buffer does not require any input current and can drive any desired load resistance without loss of signal voltage. Unity-gain buffer is used in many sensor and data acquisition systems.



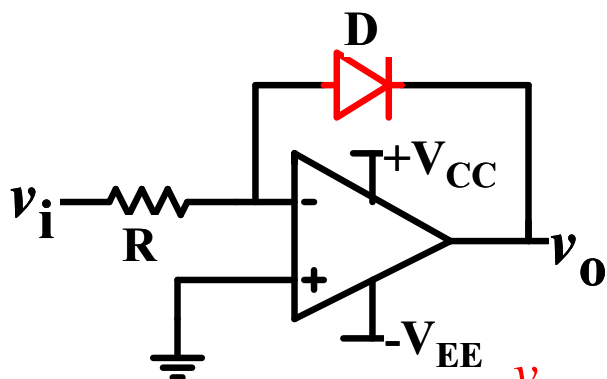Log Amplifier or Temperature Sensor: $I_i = I_D = I_S(e^{V_D/V_T} - 1) \quad ; \quad V_T = \frac{k_B T}{q}$



$$\therefore \frac{v_i}{R} = I_S(e^{-v_o/V_T} - 1)$$


$$\frac{v_i}{I_S R} + 1 = e^{-v_o/V_T}$$

which gives $-v_o = V_T \times \ln(1 + \frac{v_i}{RI_S}) \cong V_T \times \ln(\frac{v_i}{RI_S})$

$$v_o = -V_T \times \ln(\frac{v_i}{RI_S})$$

But $I_i = I_S$ for $i_- = 0$, where the diode saturation current I_S is a function of temperature also.

Antilog Amplifier

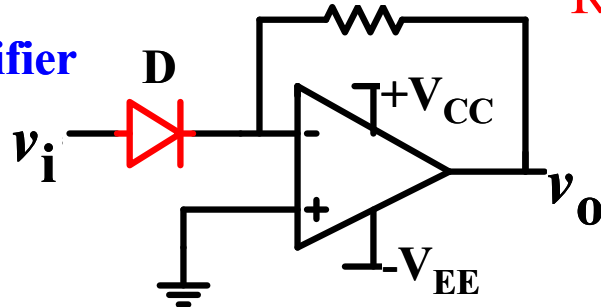


$$v_o = -RI_S(e^{v_i/V_T} - 1) \cong -RI_S \times e^{v_i/V_T}$$



ESc201, Lecture 26: Operational Amplifier

Example of summer/subtractor

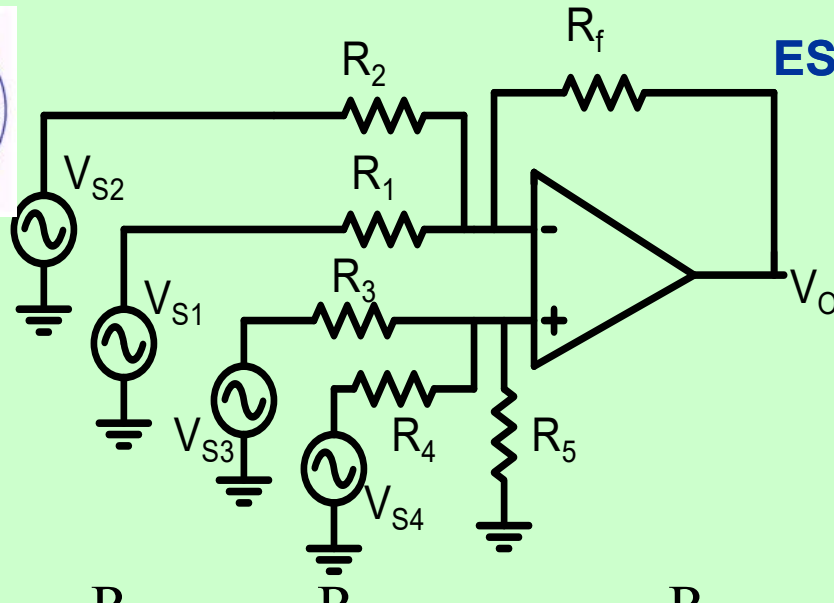

$$v_O = -10v_{S1} - 4v_{S2} + 5v_{S3} + 2v_{S4}$$

$$R_P = R_3 \parallel R_4 \parallel R_5$$

Choose : $R_f = 10K$


Then by Superposition:

$$v_O = -\left(\frac{R_f}{R_1}\right)v_{S1} - \left(\frac{R_f}{R_2}\right)v_{S2} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_3} v_{S3} + \left(1 + \frac{R_f}{R_1 \parallel R_2}\right) \times \frac{R_P}{R_4} v_{S4}$$

$$\Rightarrow R_1 = 1K \quad \Rightarrow R_2 = 2.5K \quad \Rightarrow \frac{R_P}{R_3} = 0.33 \quad \Rightarrow \frac{R_P}{R_4} = 0.133 \quad \Rightarrow \frac{R_4}{R_3} = 2.5$$


Now choose : $R_3 = 1K \Rightarrow R_4 = 2.5K \Rightarrow R_P = 0.33K \Rightarrow R_5 = 0.625K$

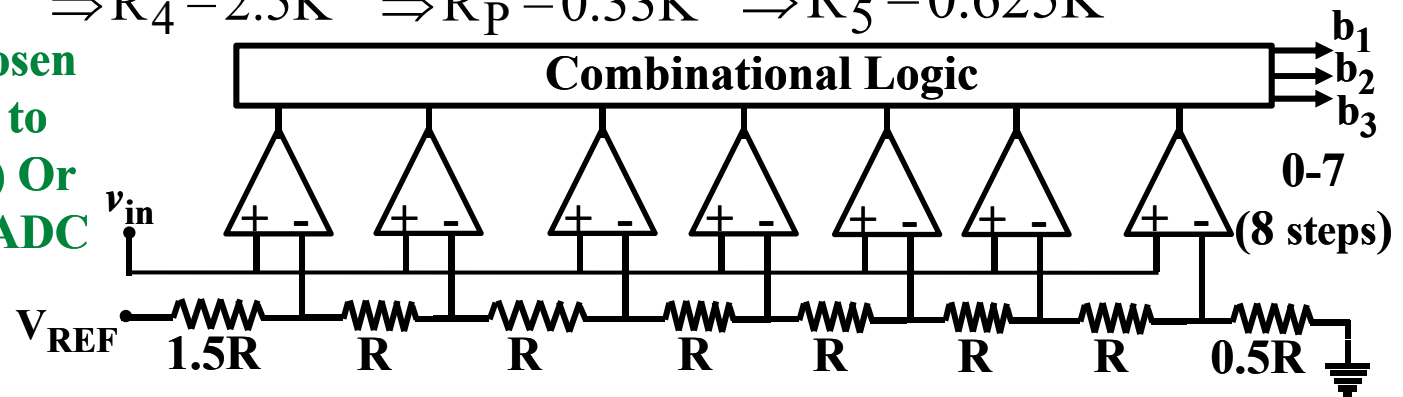The ratios can be so chosen that one gets an Analog to digital converter (ADC) Or simply a flash (fastest) ADC using a comparator is:



Requires $2^n - 1$ comparators and reference voltages for n -bit conversion.

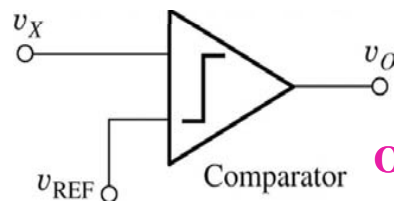Other types are Counting ADC, D-S, Successive Approximation, Single-Ramp, Dual-Ramp, etc.







ESc201, Lecture 25: Operational Amplifier

Digital to Analog Converters : (DAC)
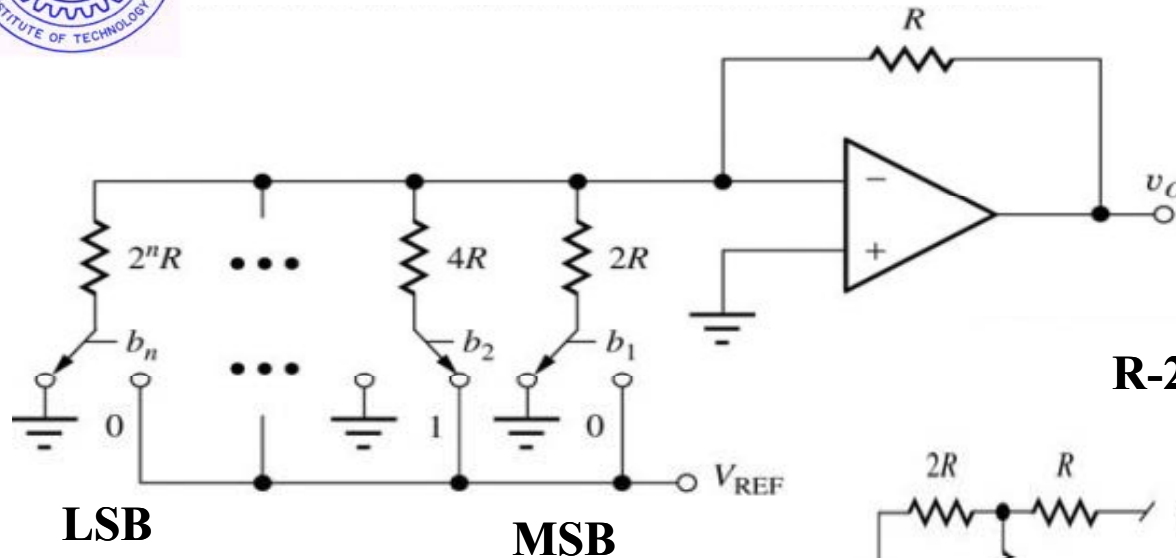
$$v_o = V_{REF}(b_1 2^{-1} + b_2 2^{-2} + \dots + b_n 2^{-n})$$



Inverted R-2R Ladder

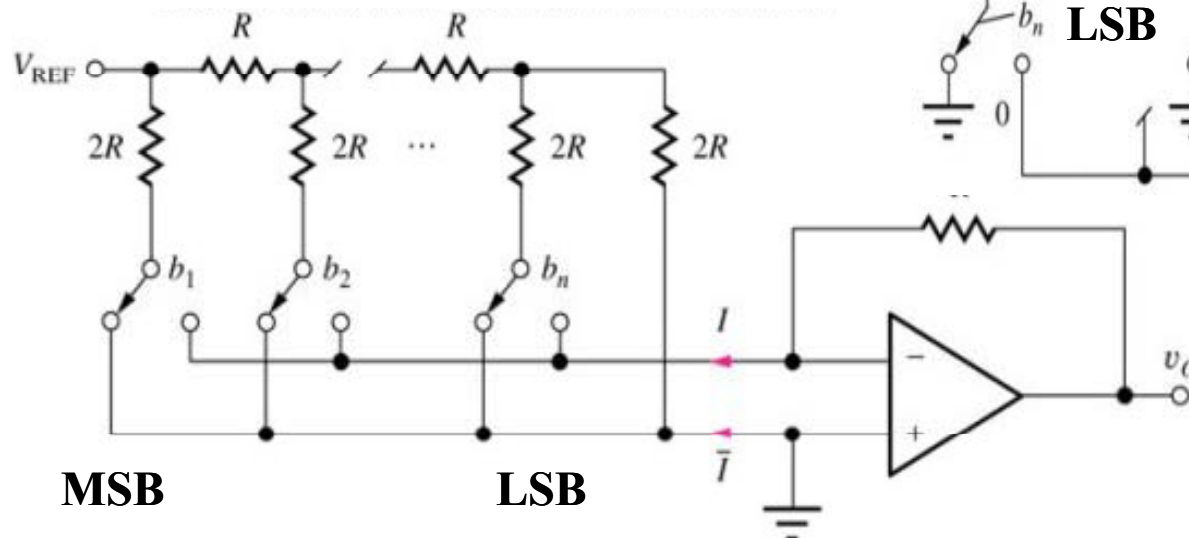

R-2R Ladder

