




ESc201, Lecture 13: Diodes

Not a bilinear device

Circuit Symbol for a Diode


Anode

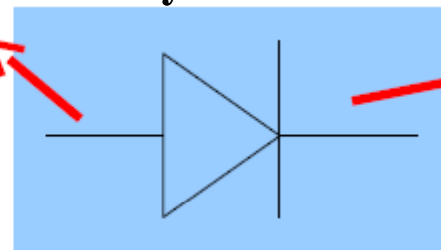

Cathode



Direction of current flow

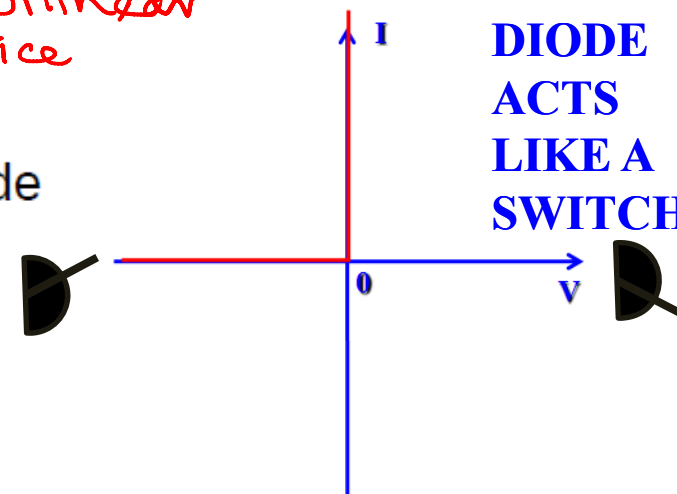

Some Special Diodes:

- Diode Solar Cell
 - Photodiode (PD)
 - Light Emitting Diode (LED)
 - LASER Diode
 - Tunnel Diode
 - Varactor Diode
 - Gunn Diode
-
- Schottky Diode
 - Step Recovery Diode

Could be two different materials or the same material with different kind of doping of impurities.

Electrons coming into a neutral material makes negatively charged ion-cores.

Electrons leaving a neutral material leaves positively charged ion-cores

ion cores are immobile

Lot of absence of free Electrons
OR Lot of Vacancies.


Large concentration Gradient at the junction and hence electrons and vacancies would inter-diffuse.

Lot of free Electrons.

This gives rise to a Built-in Potential at the junction.


Separation of charges mean there is an Electric field

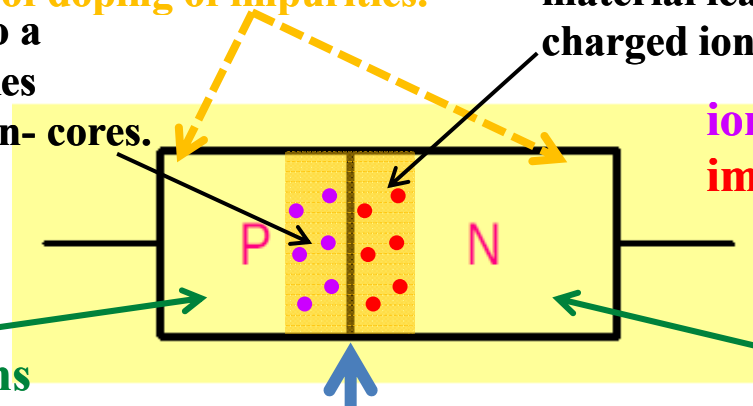$E = -\frac{dV}{dx}$ and hence there must be a potential gradient





ESc201, Lecture 13: Diodes

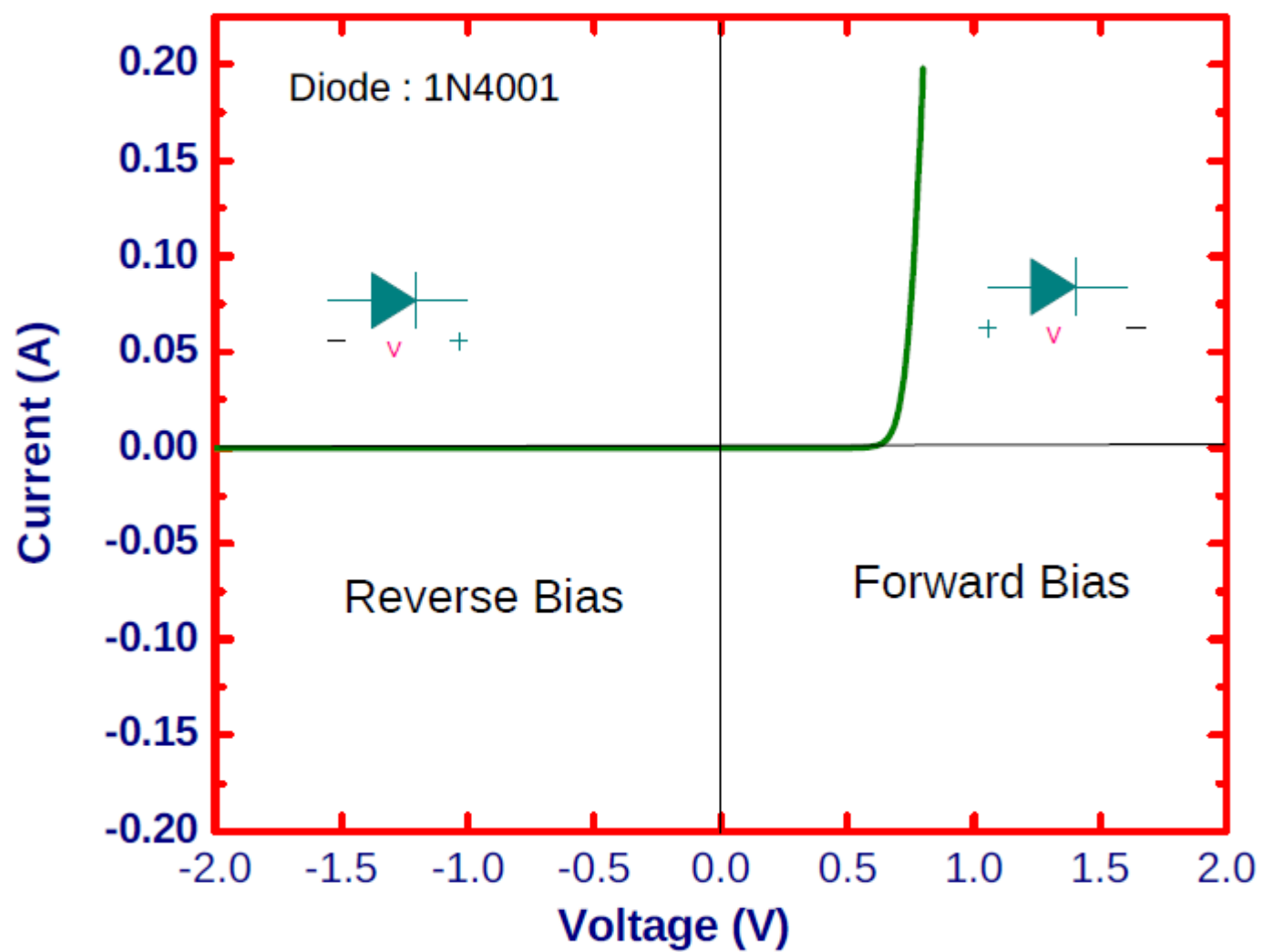




ESc201, Lecture 13: Diodes

Diodes having breakdown voltage 2-5 V may *break down by a combination* of both Avalanche and Zener mechanisms

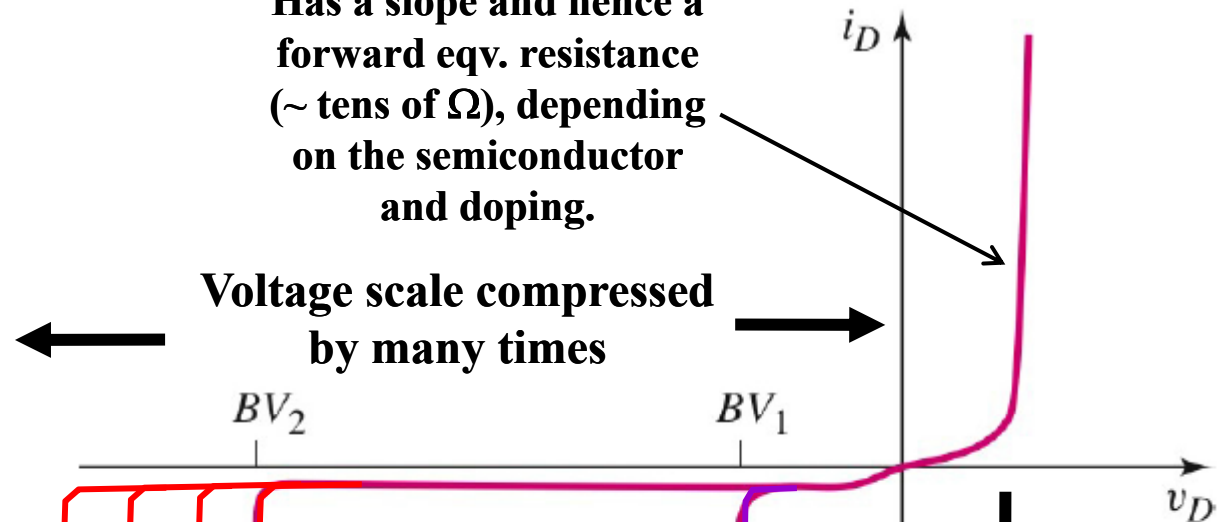Has a slope and hence a forward eqv. resistance (\sim tens of Ω), depending on the semiconductor and doping.



Voltage scale compressed by many times

BV_2

BV_1

v_D

Current scale Magnified by many orders

Avalanche Breakdown

Has a slope and hence an equivalent resistance ($< 100\Omega$) ($BV_2 \sim 100-1\text{kV}$) depending on the semiconductor and the diode structure.

Low doped

High doped

BV_2 increases with T

Zener Breakdown Has a slope and hence an eqv. resistance ($\sim 50-200\Omega$), ($BV_1 \sim 5-8\text{V}$) depending on the semiconductor and doping.



 **Ideal Diode**


ESc201, Lecture 13: Diodes

Equivalent circuits

Forward

Forward

resistance, r_F

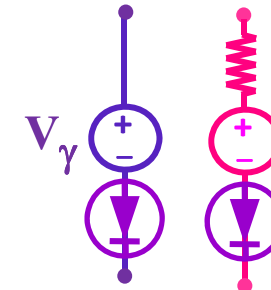




V_γ

Reverse

Breakdown

resistance

r_A or r_Z

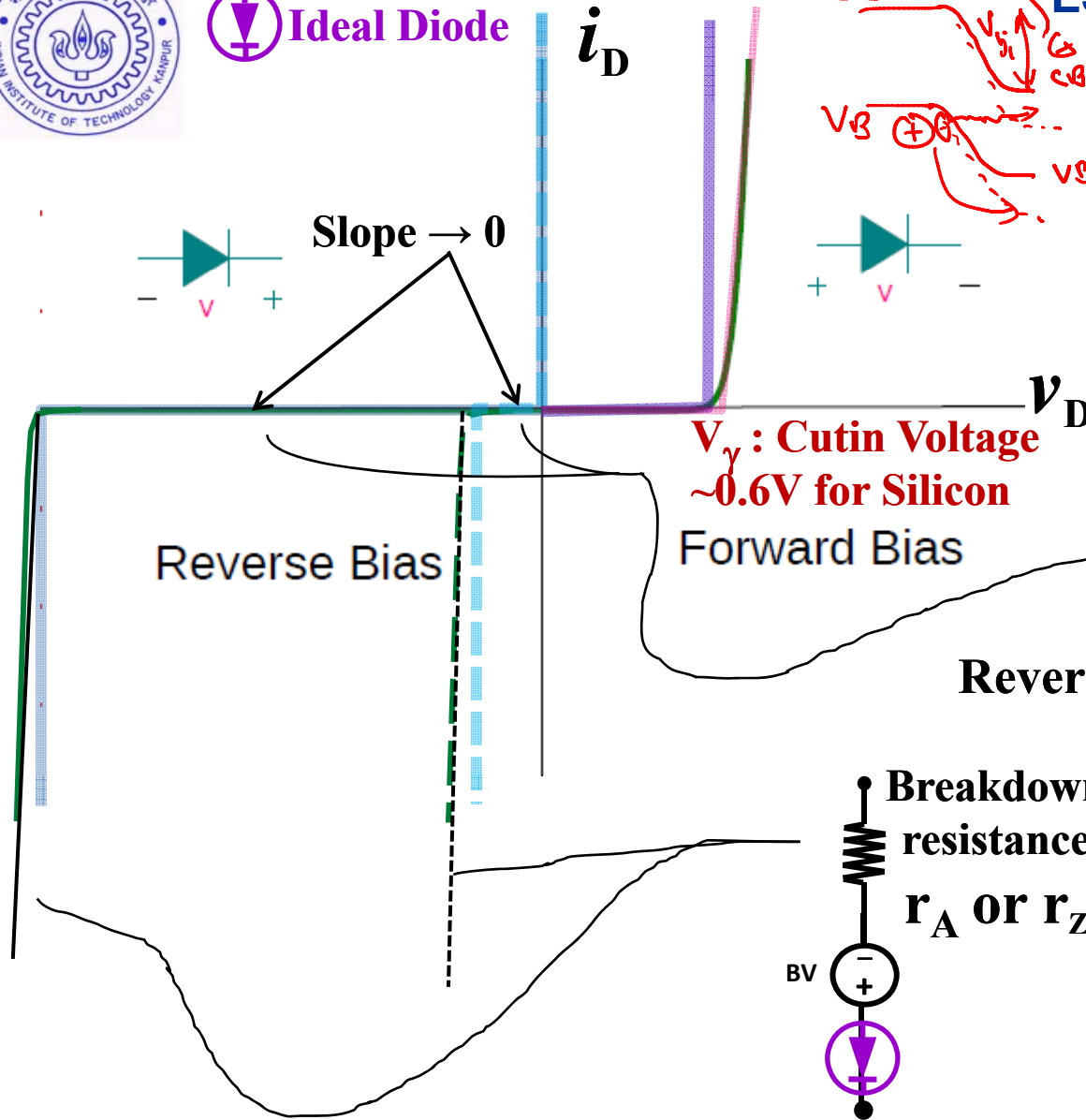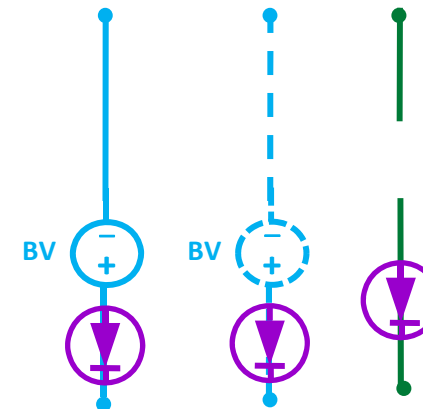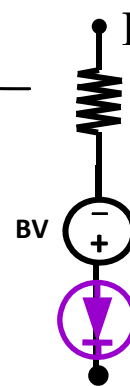



ESc201, Lecture 13: Diodes

Diode I-V Relation :

$$I_D = I_S \left[e^{q \frac{V_D}{n k_B T}} - 1 \right]$$

$$\begin{aligned} V_T &= (k_B T)/q \\ &= 25.9 \text{ mV at } 300^\circ \text{K.} \\ &\approx 26 \text{ mV at } 300^\circ \text{K.} \end{aligned}$$

I_D is the diode current.

I_S is the reverse saturation current
(~ tens of pA – few nA).

k_B is the Boltzman constant.

T is the absolute temperature.


n is the ideality constant (close to 1 for good diodes).

V_D is the voltage across the Diode.

For V_D positive (Forward Bias) and large
with respect to V_T , I_D is exponential.

For V_D negative
(Reverse Bias and less
than Breakdown voltage),
the exponential term
rapidly decays and
 $I_D = -I_S$.

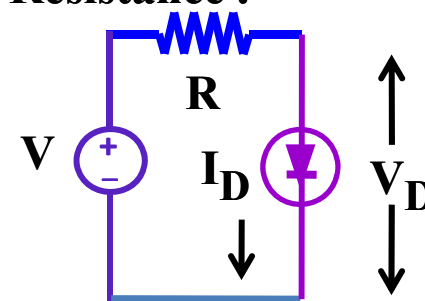When the diode is connected, at
forward bias, in series with a Voltage
Source and a Resistance .



I_{DQ} quiescent
operating current. I_{DQ}


Load Line Equation:

$$I_D = (V - V_D)/R.$$

Diode Equation:

$$I_D = I_S [\text{Exp}(V_D/V_T) - 1].$$

Can be solved iteratively.


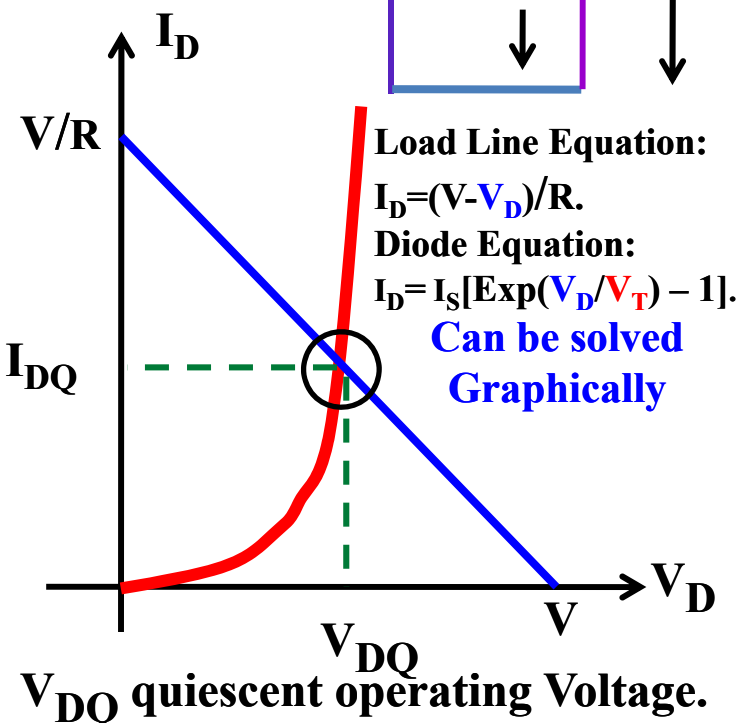




ESc201, Lecture 13: Diodes

Some Special Diodes:


- Diode Solar Cell
- Photodiode (PD)

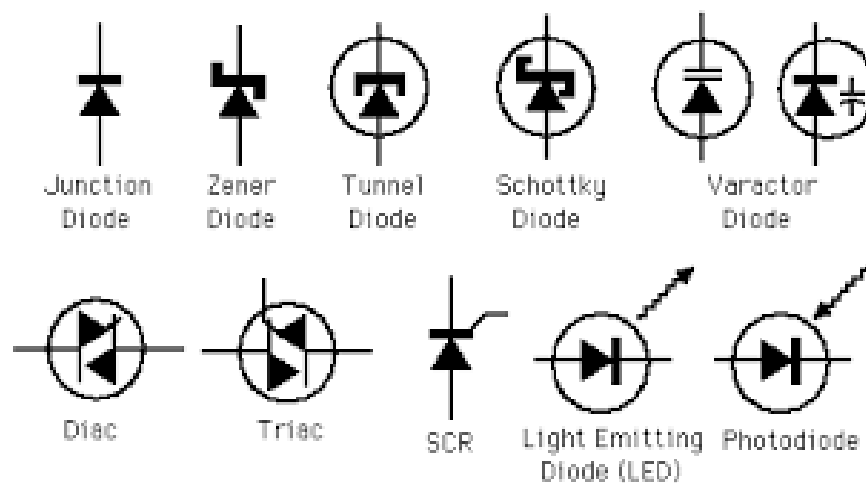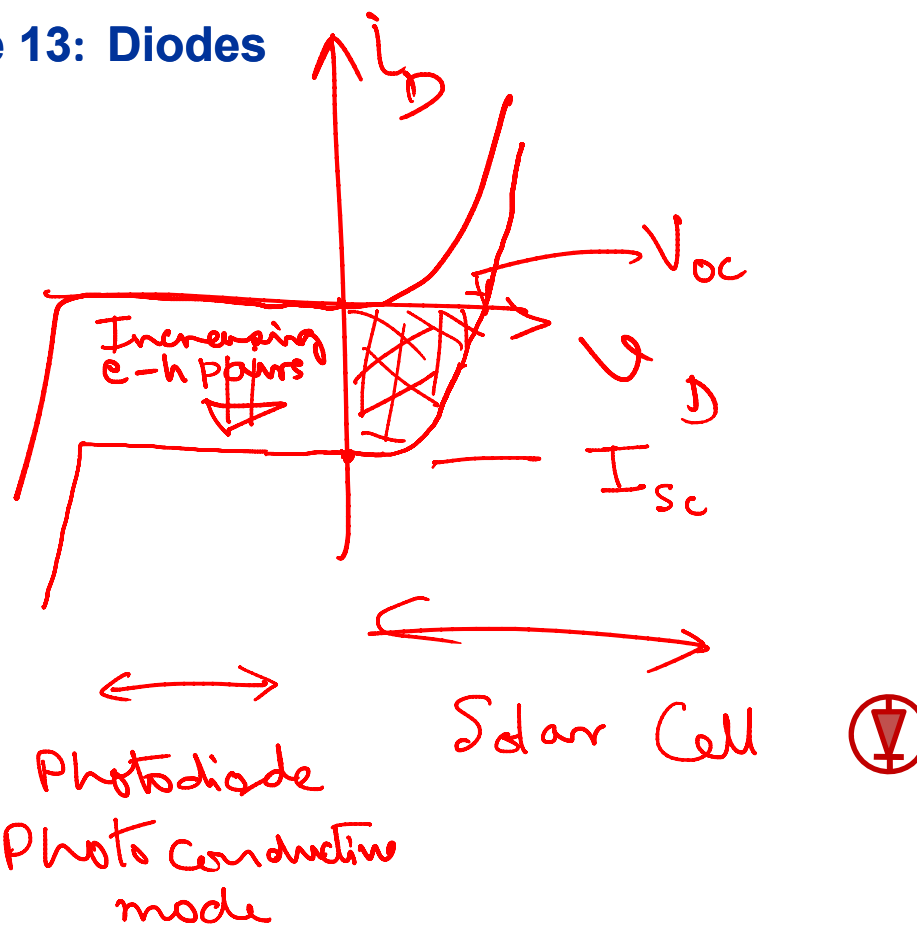





ESc201, Lecture 13: Diodes

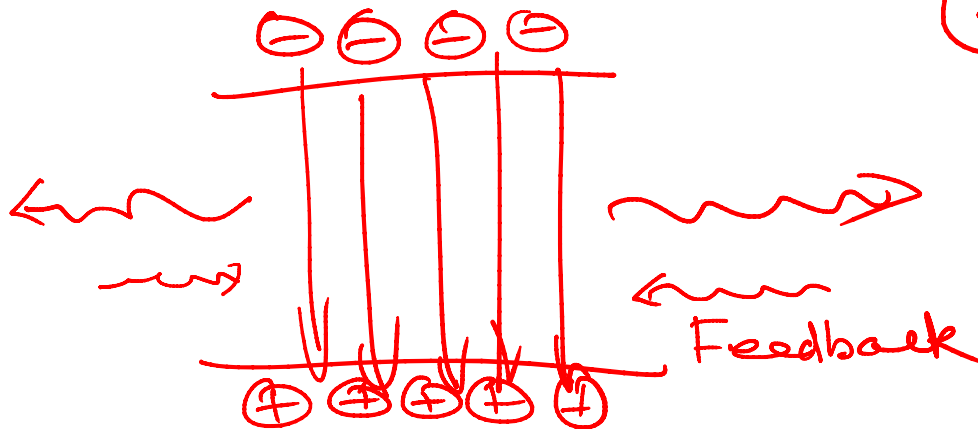- Light Emitting Diode (*LED*)
- LASER Diode



→ Same wavelength and polarization

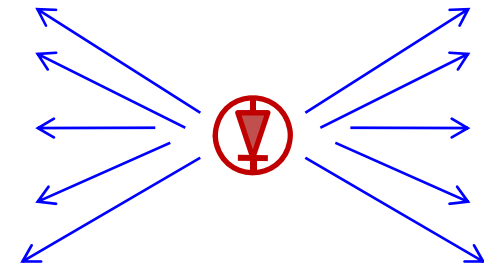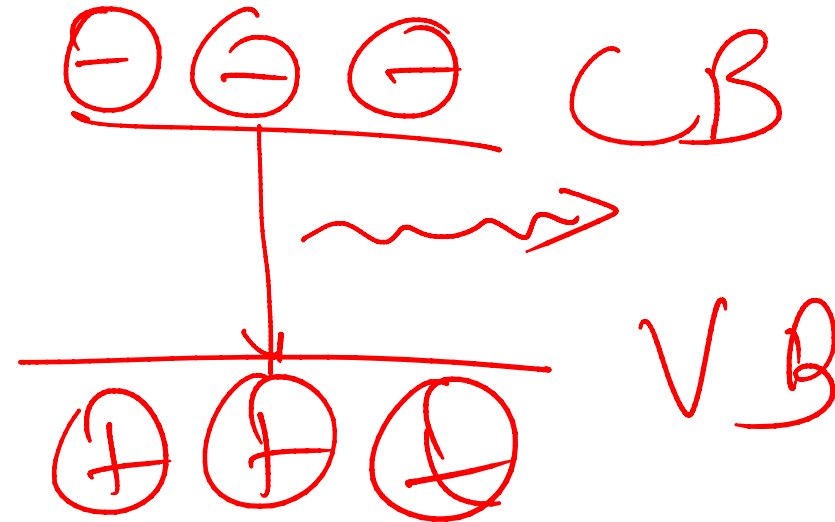


Wavelengths spread
over a large
spectrum.
No co-relation
between the photons.




ESc201, Lecture 12: Diodes

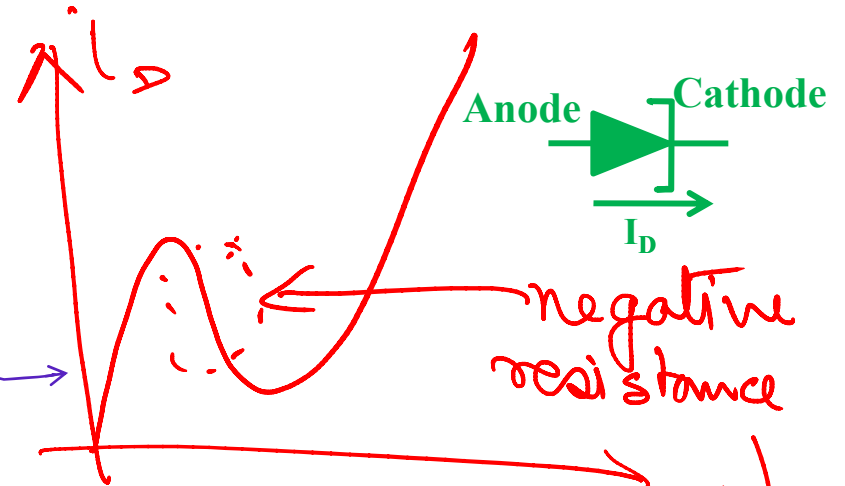- Tunnel Diode
- Varactor Diode
- Gunn Diode
- Schottky Diode



Cathode

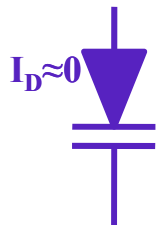

Anode

With bias the depletion width increases or decreases
∴ Separation of charge (Capacitor)
Capacitance value can be varied with applied voltage

Used as an oscillator




Avalanche

Termed as transferred electron device.

Used as a high (GHz) frequency oscillator
But not much used now as the powers of these are very low.

It can also use as an amplifier.

Anode

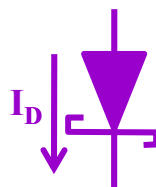

Cathode

Metal/Semiconductor Junction

Holes and electrons do not conduct current. Only movement of electrons

These are fast diodes (For high speed operation)

Low cut in voltage ($V_f \approx 0.1-0.2V$), low B_V , low capacitance



ESc201, Lecture 12: Diodes

– Avalanche Breakdown Diode



specifically designed to undergo breakdown at specific reverse voltage to prevent the damage.

– Step Recovery Diode



Stores the charge from positive pulse and uses in the negative pulse of the sinusoidal signals. The rise time of the current pulse is equal to the snap time. Due to this phenomenon it has speed recovery pulses.

Cut-off frequency range of 200-300 GHz. In the operations which are performing at 10GHz range these diodes play a vital role.