 




ESc201, Lecture 32: (Digital)

Carry Look Ahead (CLA)

Multi-bit binary adders built by 1-bit Full Adder becomes a botheration for large numbers. This is because the higher order bit addition has to wait for the trickling down of the carry bit from the low order bits. But there are no free lunches.



For the 1st stage of the Carry Generator Circuit, the Generate term, $G_i = A_i B_i$, is just an AND gate, and to get the Propagate term $P_i = A_i + B_i$, it is an OR gate. For the 2nd stage (Example: $C_0 = G_0 + P_0 C_{in}$) to generate C_i . Similarly the last term of C_3 is $P_3 P_2 P_1 P_0 C_2$. Hence with the increase in the number of bits, the number of Fan-in's to the AND gate increases and it lands up in a law of diminishing returns.

Implementation : Not suitable for more than 8-bits.



ESc201, Lecture 32: (Digital) Combinational Logic Topics left

1. Decoders, Encoders




2. Multiplexers

3. Adder/Subtractors, Multipliers

4. Comparators

5. Parity Generators

6.

  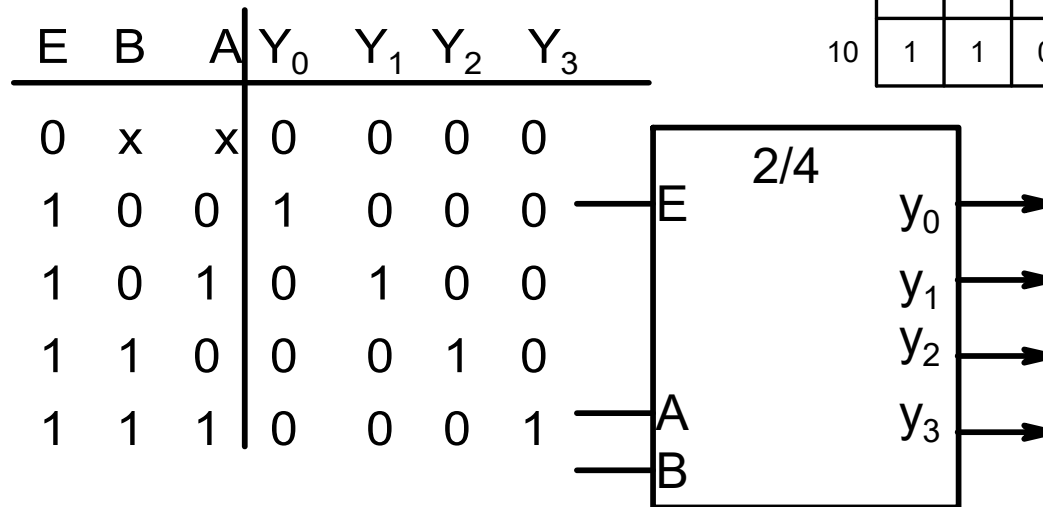

| BA | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| DC | 1 | 0 | 1 | 1 |
| 00 | 1 | 0 | 1 | 1 |
| 01 | 0 | 1 | 1 | 0 |
| 11 | 0 | 1 | 0 | 0 |
| 10 | 1 | 1 | 0 | 0 |

Decoders with 'Enable' input

| Dec or Function | Input | | | | | Output | | | | | | |
|-----------------|-------|---|---|---|----|--------|---|---|---|---|---|---|
| | D | C | B | A | BI | a | b | c | d | e | f | g |
| 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 |
| 10 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 11 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 12 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 13 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 14 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 15 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| BI | x | x | x | x | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

$$a = (\bar{D} + \bar{B}) \cdot (\bar{C} + A) \cdot (D + C + B + \bar{A})$$


'Enable' used to blank a digit when not used or to hold a value steady.



ESc201, Lecture 32: Digital : Binary Coded Decimal (BCD)


Code each number 0-9 into 4 bits and concatenate, such as:

 136 = 0001 0011 0110 = 0001 0011 0110 \neq 310
 1 3 6



Sometimes it is simpler to implement functions using BCD than raw binary. But, inefficient due to a large waste of states (10-15) of the 4-bits. An example is a 7-segment display decoder.

Encoders (Inverse of decoders)

 

| d_1d_0 | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| d_3d_2 | 00 | 01 | 11 | 10 |
| 00 | x | 0 | x | 1 |
| 01 | 0 | x | x | x |
| 11 | x | x | x | x |
| 10 | 1 | x | x | x |

$$A = \overline{d_2} \overline{d_0}$$

| d_1d_0 | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| d_3d_2 | 00 | 01 | 11 | 10 |
| 00 | x | 0 | x | 0 |
| 01 | 1 | x | x | x |
| 11 | x | x | x | x |
| 10 | 1 | x | x | x |

$$B = \overline{d_1} \overline{d_0}$$

Errors:

- Suppose high quality filters, amplifiers, antennas etc. are available.
- In typical communication systems, error rates are low, e.g. 1 bit error every 100,000 bits
- But not zero! What happens when a bit flips?
- **Bit flip error: 0 instead of 1 or 1 instead of 0**
- Suppose 100 is transmitted, but a bit error may result in 000 being received.

100
(4) 000
(0)

Single bit flip results in a catastrophic error !!!



ESc201, Lecture 32: (Digital)

Error detection and correction -- Parity

Even parity: Set MSB so as to ensure that the total number of ones in the string are even.

ASCII code of "S"



Receiver counts
odd number of 1s,
error detected!

Sender sets
parity bit to 0

Interference
changes bit

A 1-bit error changes the parity and thus can be detected. But what if two errors are there ? One needs to add one more bit. Hence nothing is full proof and 1 bit needed for seven message bits. Efficiency is 14% !!

Error detection and correction -- Checksum

Checksum: When data is to be transmitted over a large distance, as single Parity bit is not really effective, as the data is subjected to burst noise which may persist for several ms. This will change the data in the process. The Checksum character is obtained by summing all the messages and is transmitted to the receiver after the message is sent. The receiver receives the checksum and figures out if a correction is needed.

Example: The checksum code for a block of messages $(48)_{16}$, $(65)_{16}$, $(6C)_{16}$, $(70)_{16}$, and $(21)_{16}$. Sum gives in the LSB $8+5+C+0+1=26$. Divide by 16 gives 1 as dividend (to be carried over to next higher bit) and 10 as remainder $= (A)_{16}$. In the next higher bit (here MSB) the sum is $1(\text{carry})+4+6+6+7+2=26$. Again divide by 16 to get 10 as remainder $= (A)_{16}$ with a carry over of 1 out of the MSB. Ignoring this carry, the sum is $(AA)_{16}$.


Hence the checksum is $(AA)_{16}$. This, however, is not the only algorithm and others more complex ones are commonly what is commercially used.



ESc201, Lecture 32: (Digital) Multiplexers (MUX)

Multiplexing means to transmit a large number of information units over a small number of lines (or channels in communication). A Multiplexer, in general, may have M-data inputs and 1 or more output lines. The path of the M-inputs to the output line is controlled by combinational circuits by a set of N-select lines. The relation between M-input lines to 1-output line is given by $M=2^N$, an N-bit binary code can generate 2^N address codes, where each address code controls one input out of M. Besides the inputs and output there is usually one more input called the 'Enable' line. Usually the 'Enable' line is low for the MUX to be active and it can be made inactive by applying a high-input to the 'Enable' line. Then the truth table for a 8-to-1 MUX is:

| Enable (EN) | Select Inputs | | | Selected Input | Output Y will be the same as one Input |
|----------------|----------------|----------------|----------------|-------------------|--|
| | S ₂ | S ₁ | S ₀ | | |
| 0 | 0 | 0 | 0 | I ₀ | I ₀ |
| 0 | 0 | 0 | 1 | I ₁ | I ₁ |
| 0 | 0 | 1 | 0 | I ₂ | I ₂ |
| 0 | 0 | 1 | 1 | I ₃ | I ₃ |
| 0 | 1 | 0 | 0 | I ₄ | I ₄ |
| 0 | 1 | 0 | 1 | I ₅ | I ₅ |
| 0 | 1 | 1 | 0 | I ₆ | I ₆ |
| 0 | 1 | 1 | 1 | I ₇ | I ₇ |
| 1 | X | X | X | None | 0 |

 


The combinational circuit can now be built up with the algebra on the right. (m's are the minterms)

$$\begin{aligned}
 Y &= (\overline{S_2} \cdot \overline{S_1} \cdot \overline{S_0} \cdot I_0 \\
 &+ \overline{S_2} \cdot \overline{S_1} \cdot S_0 \cdot I_1 \\
 &+ \overline{S_2} \cdot S_1 \cdot \overline{S_0} \cdot I_2 \\
 &+ \overline{S_2} \cdot S_1 \cdot S_0 \cdot I_3 \\
 &+ S_2 \cdot \overline{S_1} \cdot \overline{S_0} \cdot I_4 \\
 &+ S_2 \cdot \overline{S_1} \cdot S_0 \cdot I_5 \\
 &+ S_2 \cdot S_1 \cdot \overline{S_0} \cdot I_6 \\
 &+ S_2 \cdot S_1 \cdot S_0 \cdot I_7) \overline{EN} \\
 &= \left(\sum_{i=0}^{2^n-1} m_i I_i \right) \overline{EN}
 \end{aligned}$$




ESc201, Lecture 32: (Digital) MUX Application

MUX expansion:
TWO 2x1 MUX
to 4x1 MUX.

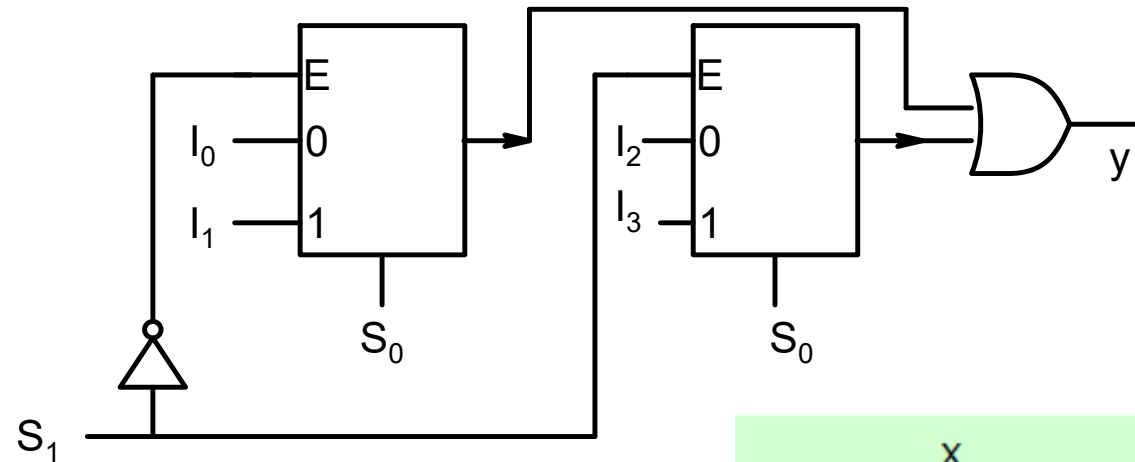

MUX + priority encoders--- who gets to use a Printer first?

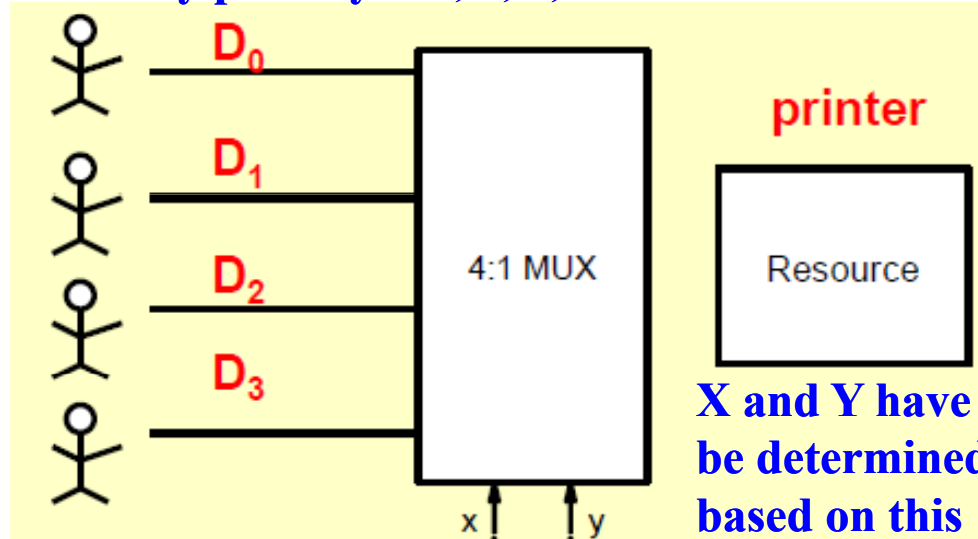Let's say priority is 3, 2, 1, and 0 with user 3 having the highest Priority



| R_0 | R_1 | R_2 | R_3 | x | y |
|-------|-------|-------|-------|---|---|
| 0 | 0 | 0 | 0 | x | x |
| 1 | 0 | 0 | 0 | 0 | 0 |
| x | 1 | 0 | 0 | 0 | 1 |
| x | x | 1 | 0 | 1 | 0 |
| x | x | x | 1 | 1 | 1 |

X and Y have to be determined based on this priority order and the requests to use the resource.

$$X = R_2 + R_3$$

$$Y = R_1 \overline{R_2} + R_3$$

| | | X | | | |
|-----------|----|-----------|----|----|----|
| | | $R_1 R_0$ | 00 | 01 | 11 |
| $R_3 R_2$ | 00 | 0 | | 0 | 0 |
| | 01 | 1 | 1 | 1 | 1 |
| | 11 | 1 | 1 | 1 | 1 |
| | 10 | 1 | 1 | 1 | 1 |

Y

| $R_1 R_0$ | 00 | 01 | 11 | 10 |
|-----------|----|----|----|----|
| $R_3 R_2$ | 00 | 0 | 1 | 1 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 1 | 1 | 1 | 1 |