




ESc201, Lecture 18: Bipolar Junction Transistor (ONLY FOR ADVANCED STUDY)

DISREGARD
NOW



$$\Delta p_c = 0, I_{EN} = a \Delta p_E \text{ \& \; } I_{CN} = b \Delta p_E \quad a = \frac{q A D_E}{L_P} \coth\left(\frac{W_b}{L_P}\right)$$
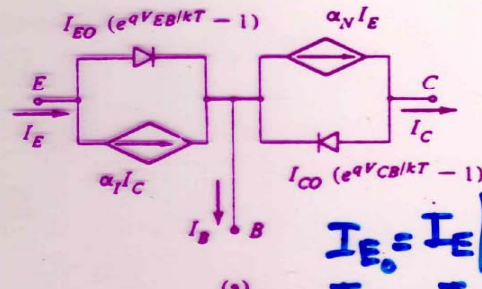
$$\Delta p_E = 0, I_{EI} = -b \Delta p_c \text{ \& \; } I_{CI} = -a \Delta p_c \quad b = \frac{q A D_P}{L_P} \coth\left(\frac{W_b}{L_P}\right)$$



$$I_E = I_{EN} + I_{EI}$$
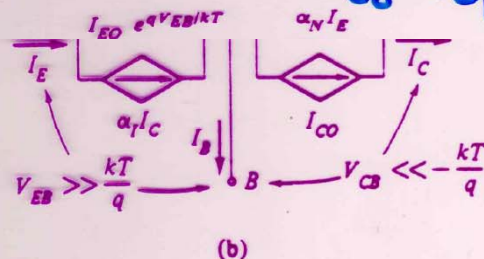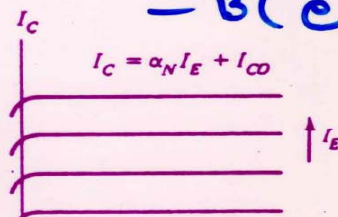
$$= A \left(e^{qV_{EB}/kT} - 1 \right) - B \left(e^{qV_{CB}/kT} - 1 \right)$$



$$I_C = I_{CN} + I_{CI}$$

$$= B \left(e^{qV_{EB}/kT} - 1 \right) - A \left(e^{qV_{CB}/kT} - 1 \right)$$

$$I_E = I_{ES} \left(e^{qV_{EB}/kT} - 1 \right) - \alpha_I I_{CS} \left(e^{qV_{CB}/kT} - 1 \right)$$

$$I_C = \alpha_N I_{ES} \left(e^{qV_{EB}/kT} - 1 \right) - I_{CS} \left(e^{qV_{CB}/kT} - 1 \right)$$

Emitter Saturation Current (normal) with $V_{CB} = 0$

Collector Saturation current with $V_{EB} = 0$



ESc201, Lecture 17: Bipolar Junction Transistor

Why $V_{BE} = 0.7\text{ V}$?

Note: I_E (and thus I_C) varies exponentially with respect to V_{BE} .

A small change in V_{BE} can cause a very large change in I_C .

As a rule of thumb, V_{BE} under the forward active mode is assumed to get pinned at 0.7 V, slightly greater than 0.6V used for cut-in voltage V_{on} .

This is only a heuristic used for quick estimate

The answer may not be accurate, however, good enough!

$$I_{E_S} \cong \text{pA-nA}$$

$$I_E = I_{E_S} \left[e^{q \frac{V_{BE}}{nk_B T}} - 1 \right] \cong I_{E_S} \times e^{q \frac{V_{BE}}{nk_B T}} \quad n=1 = I_{E_S} \times e^{\frac{V_{BE}}{V_T}}$$

$V_T = (k_B T)/q$
 $= 25.9\text{mV at } 300^\circ\text{K.}$
 $\approx 26\text{mV at } 300^\circ\text{K.}$

Current Gain

The sum of the collection component and the recombination component must always equal the injection component (charge conservation)

$$I_E = I_B + I_C$$

$$\text{Common Emitter Current Gain } (\beta) = I_C / I_B$$

$$\text{Common Base Current Gain } (\alpha) = I_C / I_E$$

$$\text{Thus, } \beta = \alpha / (1 - \alpha) \text{ and } \alpha = \beta / (\beta + 1)$$

For a good transistor I_B should be as small as possible or $\alpha \rightarrow 1$ and hence β is quite large (100 – 500)

Closer is the value of α to 1, better is the BJT !




ESc201, Lecture 18: Bipolar Junction Transistor

Modes of Operation : BE and BC junction can either be forward biased or reverse biased, which gives 4 possible modes of operation.

1. Forward Active Mode: BE junction forward biased AND BC junction reverse biased.
2. Reverse Active Mode: BE junction reverse biased AND BC junction forward biased.
3. Saturation Mode: Both junctions forward biased.
4. Cutoff Mode: Both junctions Reverse biased.


Common Emitter (CE) Configuration

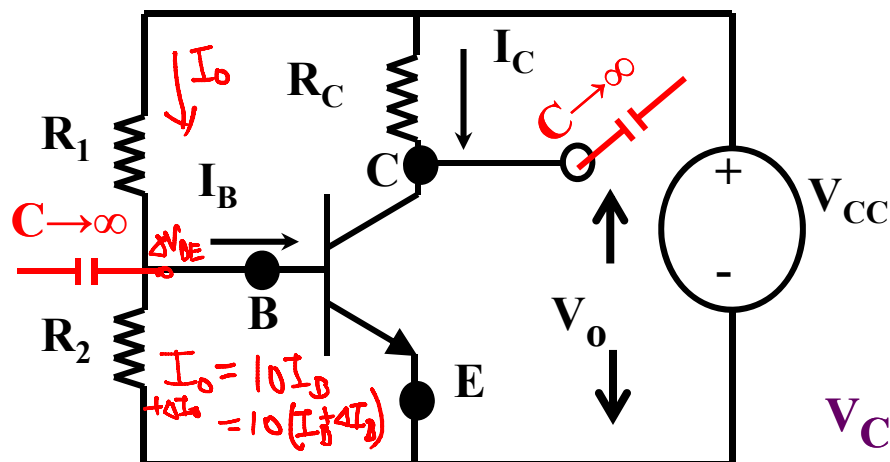

Once V_{CE} drops below 0.7 V, the BJT enters the saturation mode of operation. With further reduction in V_{CE} , the BJT moves deeper into saturation. This is the digital mode of operation of BJTs. However, BJTs used in analog circuits should never ever enter this mode of operation. Always check for analog circuits if V_{CE} is $>0.7V$.

$$V_{CEsat} \approx 0.2V$$

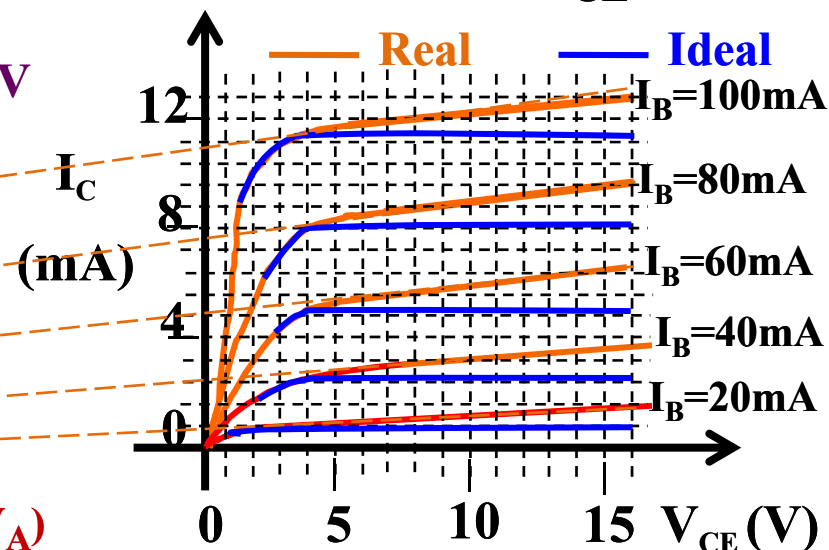This course would only deal with Ideal characteristics




All meet the x-axis at a point, called the EARLY voltage (V_A)




ESc201, Lecture 18: Bipolar Junction Transistor

Common Base (CB) Configuration

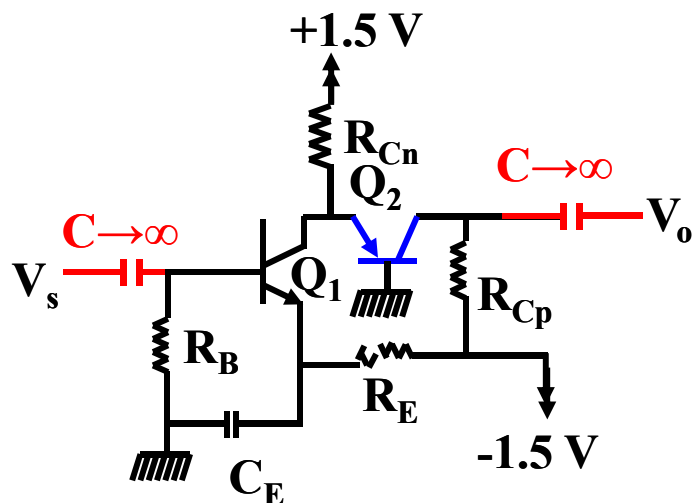


$$= \frac{eA}{t}$$

Common Collector (CC) Configuration

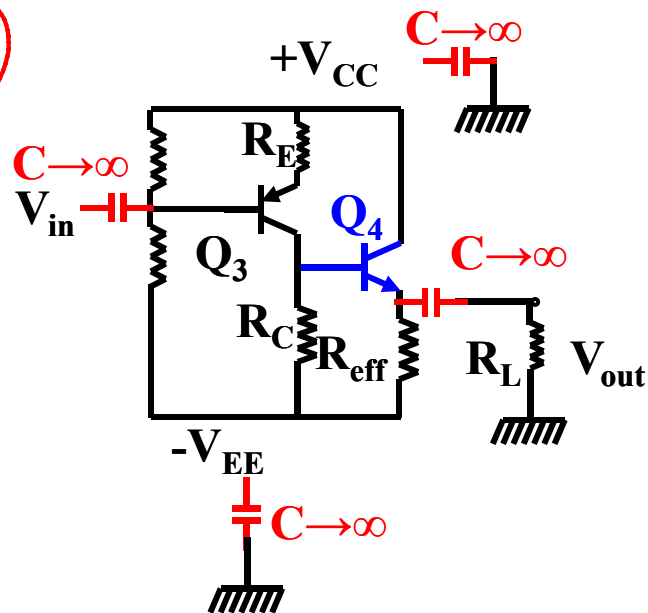

Non-inverting voltage gain and output resistance very similar to CE configuration
But input impedance much lower than CE

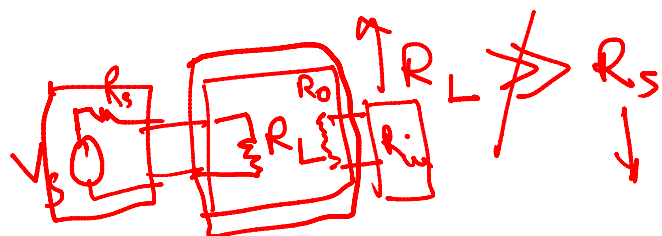High Input Impedance
But Low output Impedance
with Gain $\approx < 1$.



$$R_o \ll R_{in}$$





ESc201, Lecture 18: Bipolar Junction Transistor

Henceforth : Only Common Emitter (CE) Configuration in this course

If I_B varies from $0 \rightarrow 15 \rightarrow 30 \mu A$ linearly, the collector current swing is distorted as I_C which should have reached $6mA$ does not do so because of saturation.

Saturation Region

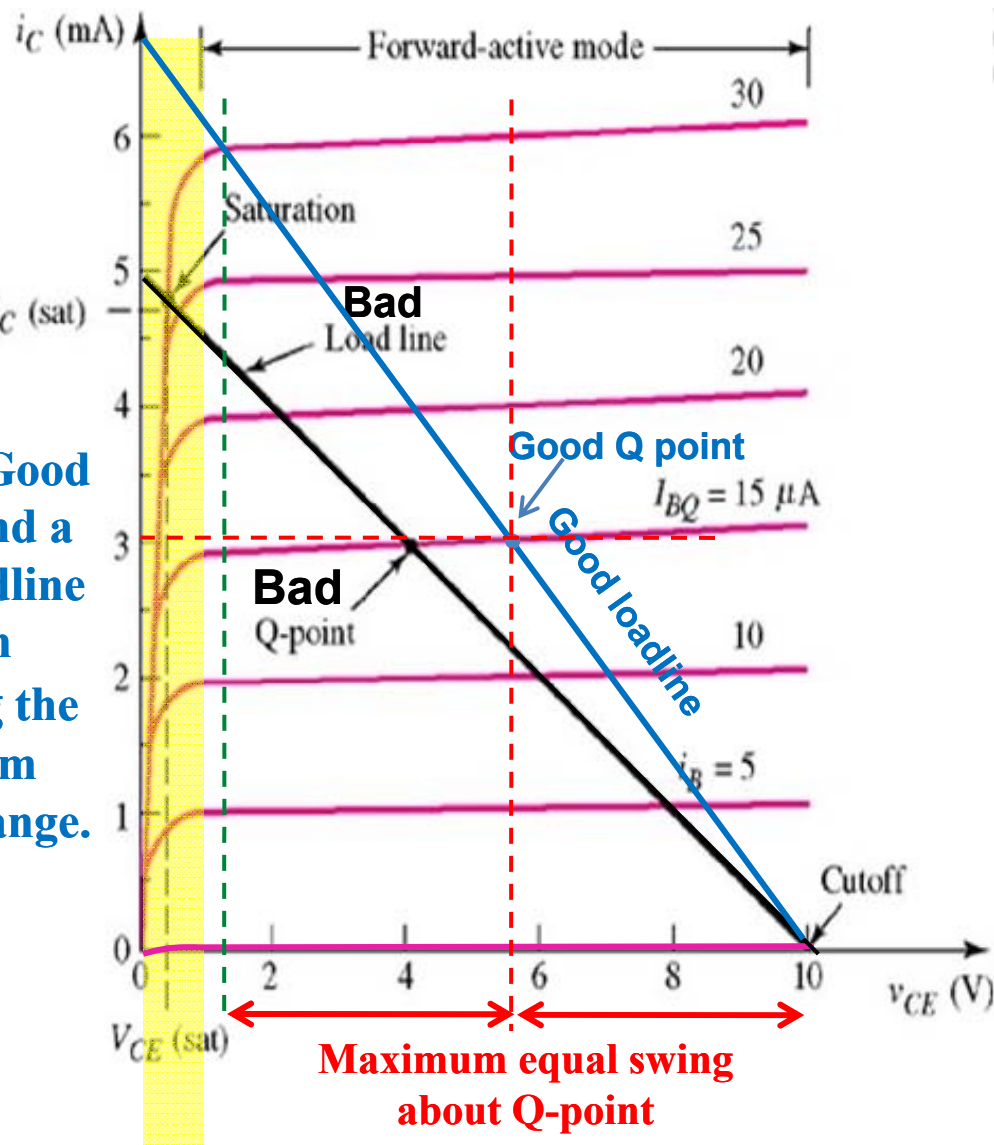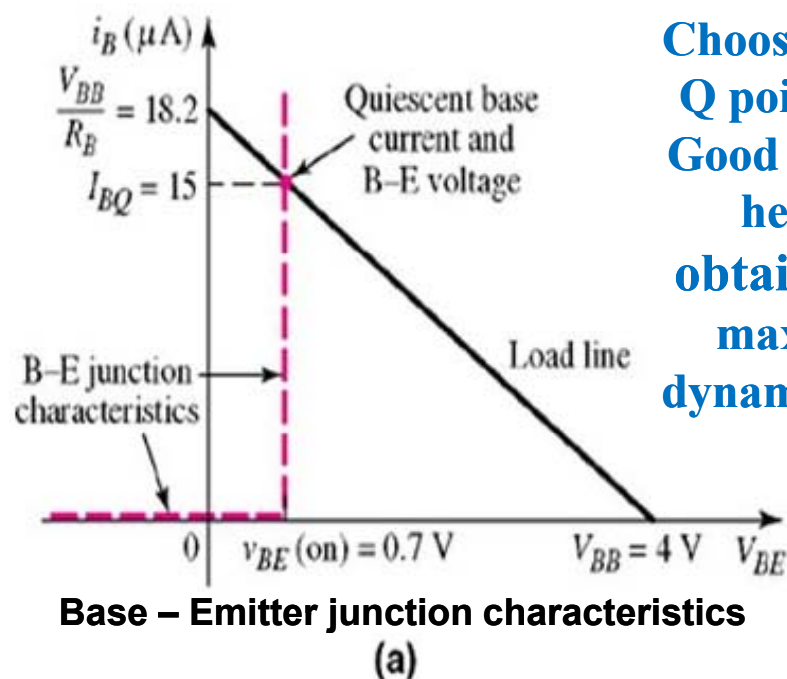
Choosing Good Q point and a Good Loadline helps in obtaining the maximum dynamic range.





ESc201, Lecture 18: Bipolar Junction Transistor

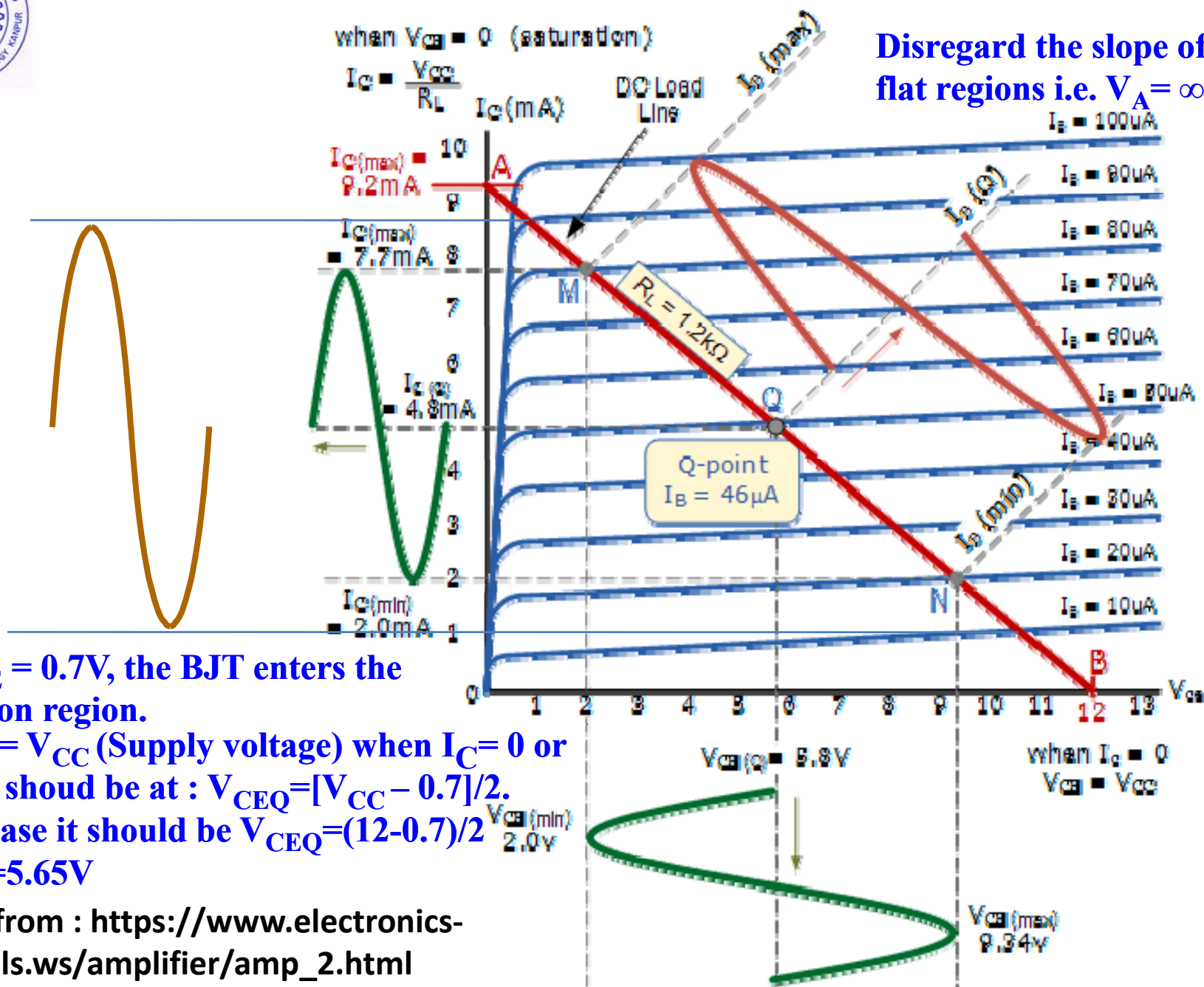Disregard the slope of the flat regions i.e. $V_A = \infty$





ESc201, Lecture 18: Bipolar Junction Transistor

Then, the transistor is replaced by its – *small signal ac model*


Subsequently, usual network analysis is done to obtain:

- 1) Voltage Gain (A_v)
- 2) Current Gain (A_i)
- 3) Power Gain ($A_p = |A_i \cdot A_v|$)
- 4) Input Resistance (R_{in})
- 5) Output Resistance (R_{out})

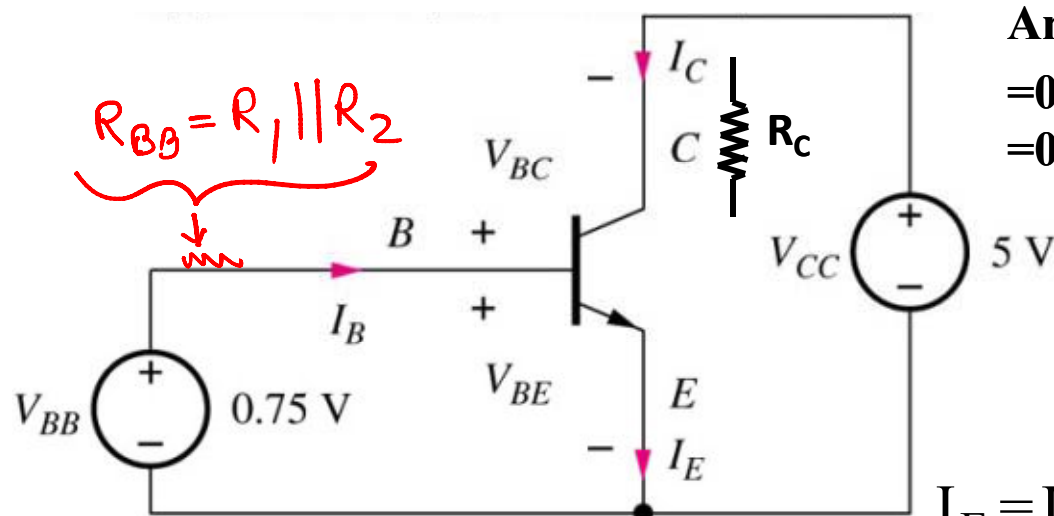Problem of Biasing: Terminal voltages and currents.

Given data: $V_{BB} = 0.75V$, $V_{CC} = 5.0V$, $I_S = 10^{-16} A$, $\beta_F = 50$, $\beta_R = 1$, $V_T = 25.0 mV$.

What is the maximum value of a resistance added to the collector (R_C)?



Analysis: $V_{BE} = 0.75 V$, $V_{BC} = V_{BB} - V_{CC} = 0.75V - 5.0V = -4.3V$ or $V_{CE} = 5V > V_{BE} = 0.75V$. The BJT is forward active mode.

$$I_E \cong I_{E_S} \times e^{\frac{V_{BE}}{V_T}}$$

$$= 10^{-16} \times e^{0.75/0.025} = 1.07mA$$


$$I_E = I_B + I_C = 1.05 + 0.0214 = 1.0714mA$$

$$\alpha_F = \frac{I_C}{I_E} = \frac{I_C}{1.07mA} = \frac{\beta}{\beta + 1} = \frac{50}{51} = 0.9804, I_C = 1.05mA$$

$$I_B = \frac{I_C}{\beta_F} = \frac{1.05mA}{50} = 21.0\mu A$$


$$V_{R_C} = I_C \times R_C = 5 - 0.75V \text{ or } R_{C_{max}} = 4.05k\Omega$$
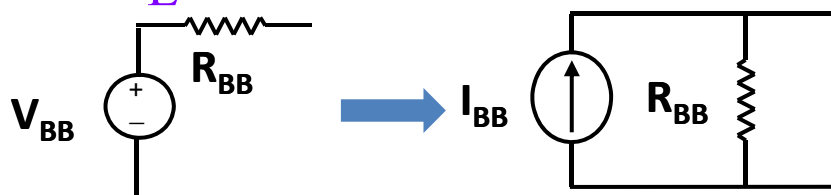
$$\text{or } R_{C_{req}} = 2.025k\Omega \text{ for best biasing}$$





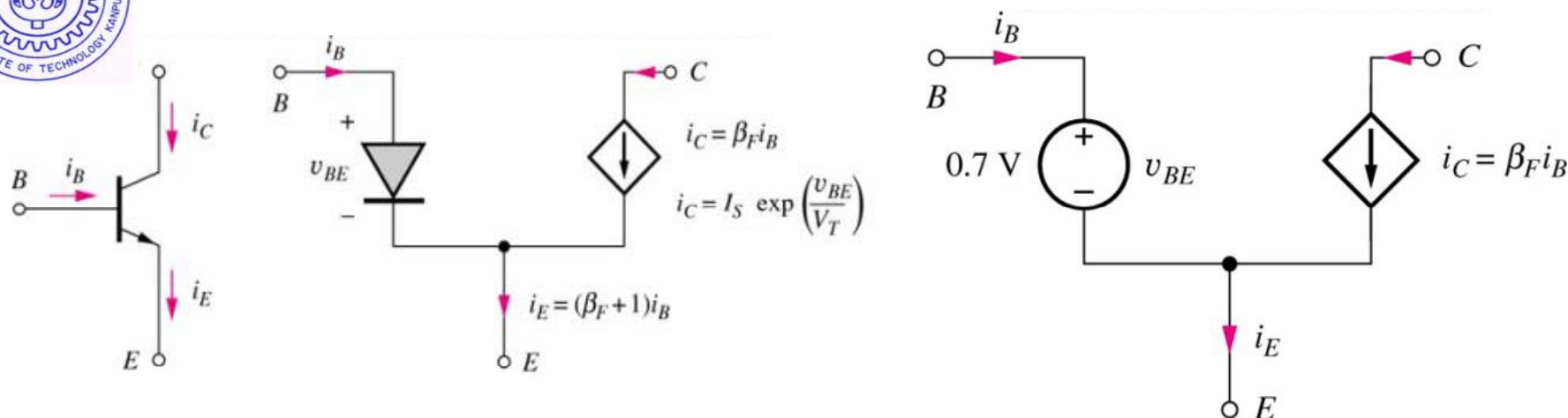ESc201, Lecture 18: Bipolar Junction Transistor



Current in base-emitter diode is amplified by common-emitter current gain β_F and appears at collector-base and collector currents are exponentially related to base-emitter voltage.

Base-emitter diode is replaced by constant voltage drop model ($V_{BE} = 0.7 \text{ V}$) since it is forward-biased in forward-active region.

DC base and emitter voltages differ by 0.7 V diode voltage drop in forward-active region.

