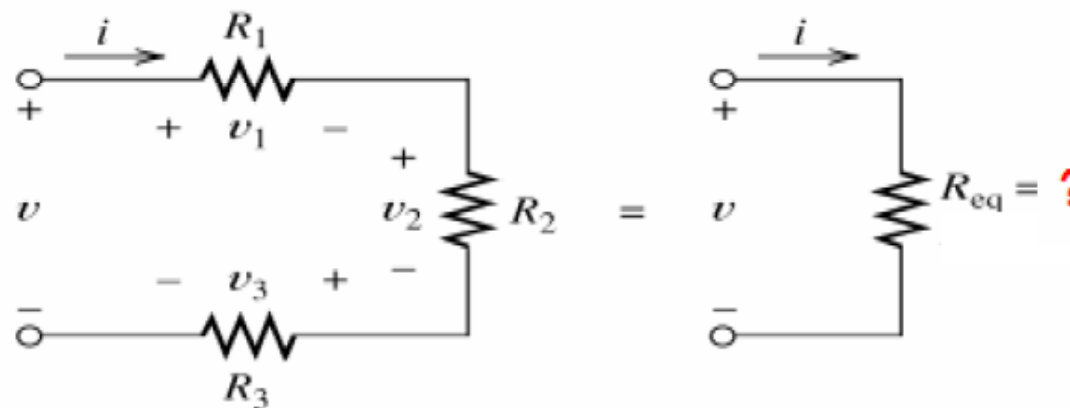




ESc201, Lecture 4: Circuit Analysis

From Rajshekhar

Series Resistances



(a) Three resistances
in series

(b) Equivalent
resistance

From (a)

$$v_1 = R_1 i$$

$$v_2 = R_2 i$$

$$v_3 = R_3 i$$

Using KVL :

$$v = v_1 + v_2 + v_3$$

$$= (R_1 + R_2 + R_3) i$$

From (b)

$$v = R_{eq} i$$

Thus,


$$R_{eq} = R_1 + R_2 + R_3$$

Both circuits are equivalent as far as **v vs. i** relation is concerned.




ESc201, Lecture 4: Circuit Analysis

Parallel Resistances

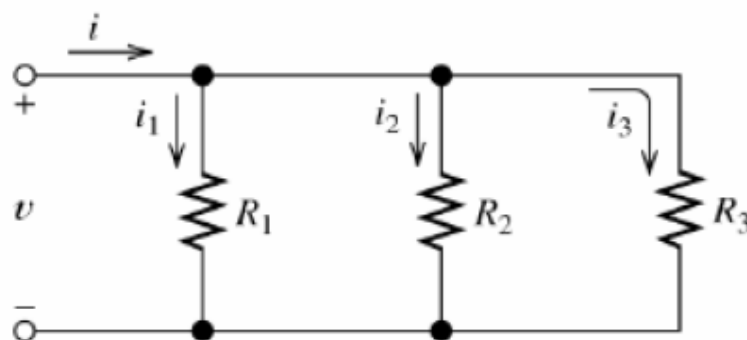

(a) Three resistances in parallel

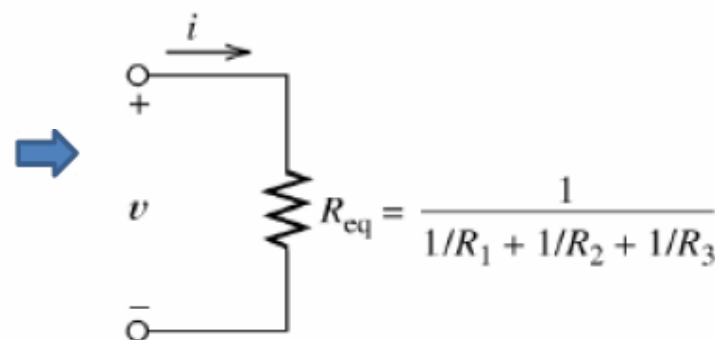

(b) Equivalent resistance

From (a):

$$i_1 = v / R_1$$

$$i_2 = v / R_2$$

$$i_3 = v / R_3$$

By KCL

$$i = i_1 + i_2 + i_3$$

$$= \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) v$$

From (b)

$$i = \left(\frac{1}{R_{eq}} \right) v$$

Thus,

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$



ESc201, Lecture 4: Circuit Analysis – Super Node


The concept of Supernode is used to reduce the number of nodal equations. i.e Node 1 and node 2 are merged together into a super node. KCL is applied to the super node.

Sum of currents leaving a super node is zero. At the Supernode:

$$\frac{V_1}{R_2} + \frac{V_1 - V_3}{R_1} + \frac{V_2 - V_3}{R_3} + \frac{V_2}{R_4} = 0$$

Obviously known $V_2 - V_1 = 10 \text{ V}$

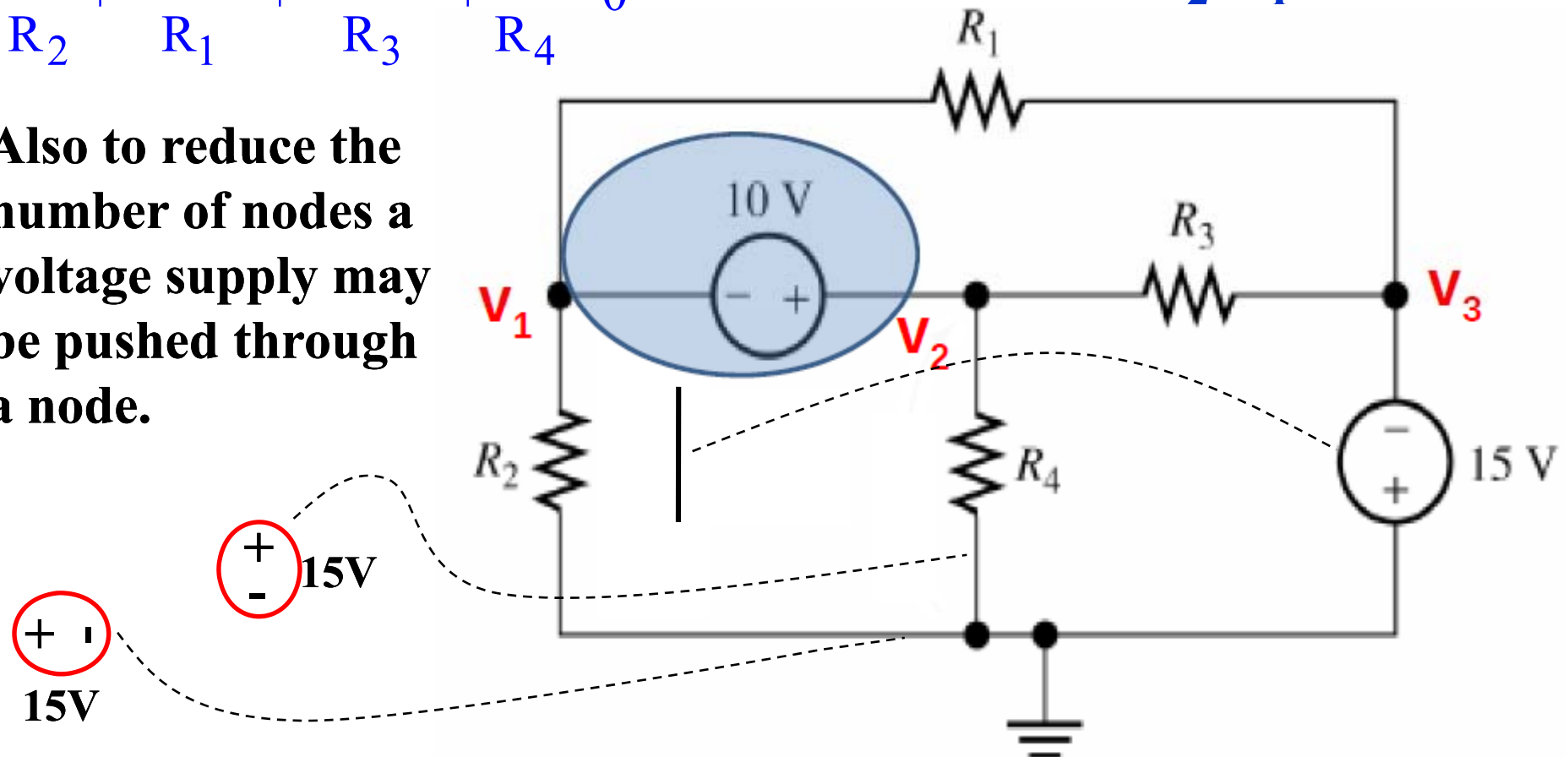Also to reduce the number of nodes a voltage supply may be pushed through a node.





From ADutta

ESc201, Lecture 4: Circuit Analysis – Super Mesh-1

Loop containing an independent current source:

Concept of *Supermesh*

Nodes A, B, and C are same node, similarly, nodes E, F, and G are same.

KVL around the mesh ABHFGA and HDEFH cannot be written, since the potential dropped across the 5A current source is unknown.

Supermesh: A mesh containing parts of other meshes i.e. ABHDEFGA.

KVL around this loop:

$$(I_1 - I_2) \times 5 + (I_3 - I_2) \times 3 + I_3 \times 1 - 5 = 0, \text{ OR } 5I_1 - 8I_2 + 4I_3 = 5 \text{ with } I_1 - I_3 = 5A$$


$$\text{Gives : } 9I_1 - 8I_2 = 25$$

Similarly KVL around BCDHB:

$$4I_2 + 3(I_2 - I_3) + 5(I_2 - I_1) = 0 \text{ or } 12I_2 - 5I_1 - 3I_3 = 0 \text{ or } 12I_2 - 8I_1 + 3(I_1 - I_3) = 0$$

$$15 = 8I_1 - 12I_2 \text{ or } -15(2/3) = -8(2/3)I_1 + 8I_2$$
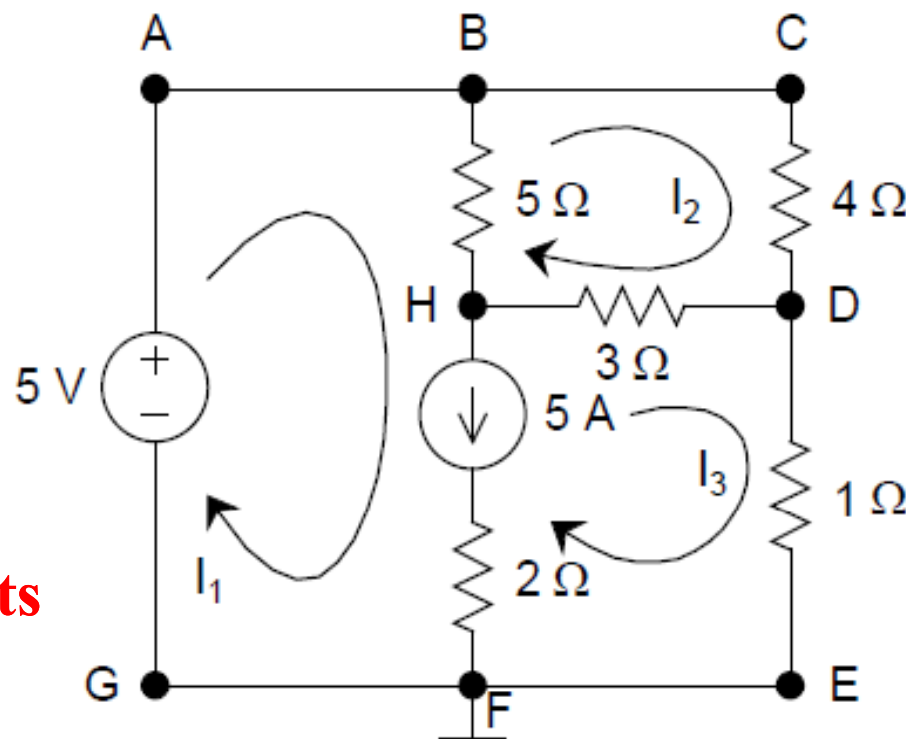
$$\text{Finally gives : } I_1 = (1/3.67)[25 - 15(2/3)] = 4.09 \text{ A, } I_2 = 1.48 \text{ A, } I_3 = -0.91 \text{ A}$$





ESc201, Lecture 4: Circuit Analysis – Super Mesh-2

$I_1 = 5A$, and mesh equations for I_1 and I_3 cannot be written.

But $3(I_3 - I_2) = V_x$

Also because of the current source $V_x/5$, $(V_x/5) = I_3 - I_1$.

Hence $I_3 = 5 + (3/5)(I_3 - I_2)$

or $(2/5)I_3 + (3/5)I_2 = 5$


$3I_2 + 2I_3 = 25$

And from mesh 2, $4I_2 + 3(I_2 - I_3) + 5(I_2 - 5) = 0$

Or $12I_2 - 3I_3 = 25$ giving $8I_2 - 2I_3 = 25(2/3)$

$11I_2 = 25(5/3)$ or $I_2 = 3.79 A$

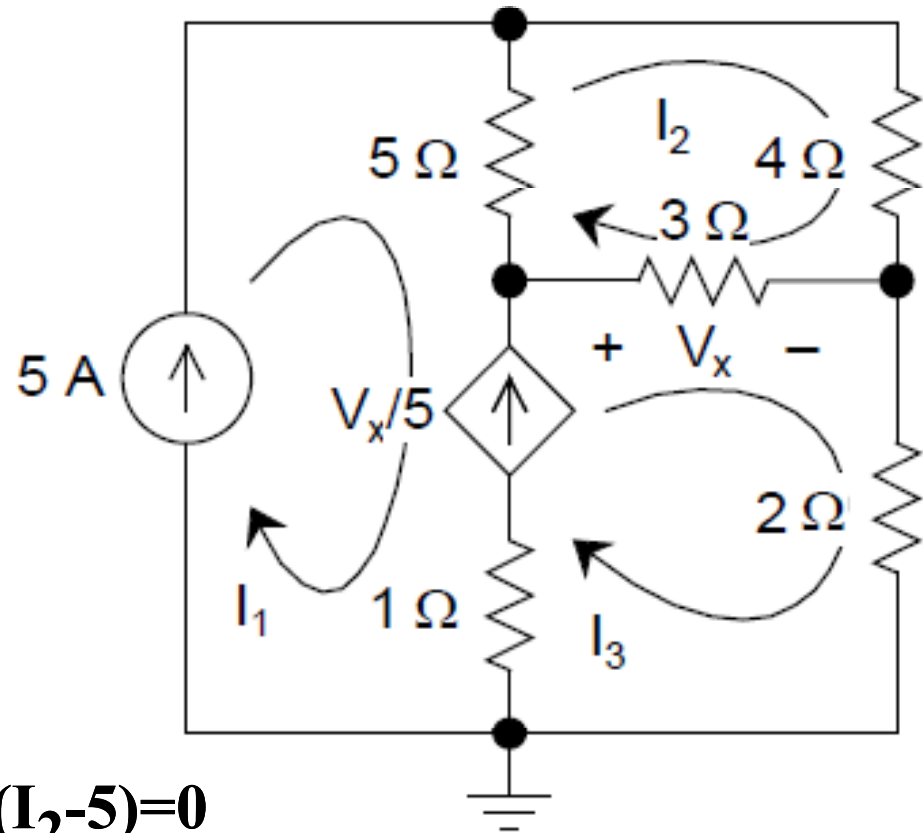$I_3 = (1/2)(25 - 3 \times 3.79) = 6.82 A$







EE Sc201, Lecture 4: Circuit Analysis – Superposition

From GRajshekhhar

Applicable to only linear circuits

Homogeneity

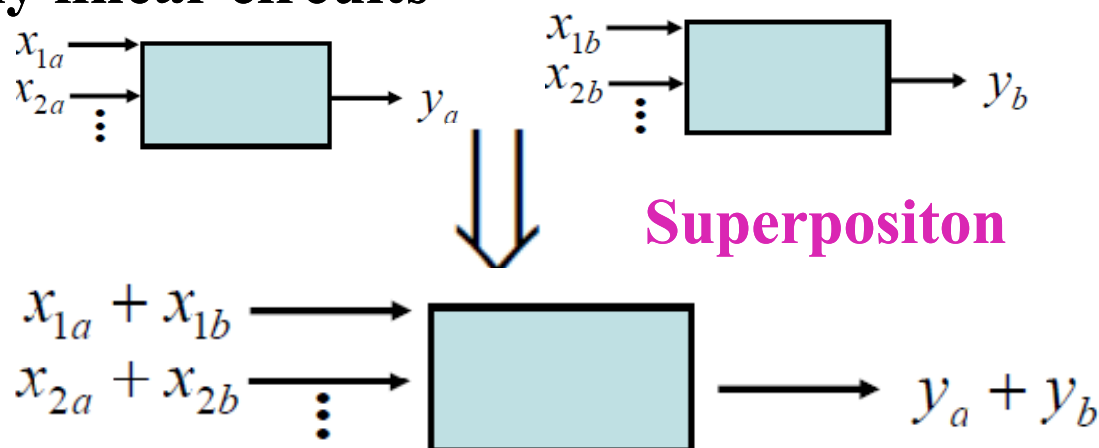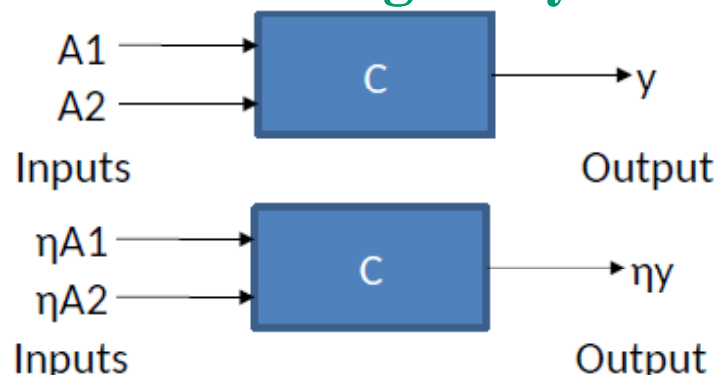

Steps:

1. Take one source at a time and null all other independent sources:
i.e. **Short** all other **independent voltage sources**, and **open** all other **independent current sources**.
Remember not to touch any of the dependent sources.
2. By adopting KCL, KVL, node voltage, or mesh current method, evaluate the currents through all branches, as well as the node voltages.
3. **Repeat steps 1 and 2 till all the sources are exhausted.**
4. Finally, the current through any branch or the voltage at any node is found as a linear superposition of all the currents flowing through that branch or the voltages appearing at that node, contributed by the different sources.



ESc201, Lecture 4: Circuit Analysis – Superposition

Step 1(a) : Short V_{s1}

Then R_1 and R_2 are in parallel and current through R_3 (B to A) is:

$$I_{R_3} = I_{s2} - KI'_x = I'_{R_1} + I'_x$$

$$= I'_{R_1} + V'_A / R_2$$

$$I_{s2} - K(V'_A / R_2) = V'_A (R_1 + R_2) / R_1 R_2$$

Find V'_A

$$\text{and } I'_x = V'_A / R_2, I'_{R_1} = V'_A / R_1$$


Step 1(b) : Open I_{s2}

$$\text{Then } (V''_A - V_{s1}) / R_1 = I''_{R_1} \text{ and } I''_x = V''_A / R_2$$

$$(I''_x R_2 - V_{s1}) / R_1 = I''_{R_1}$$

$$\text{Current through } R_3 \text{ (A to B)} = KI''_x = -I''_{R_1} - I''_x$$

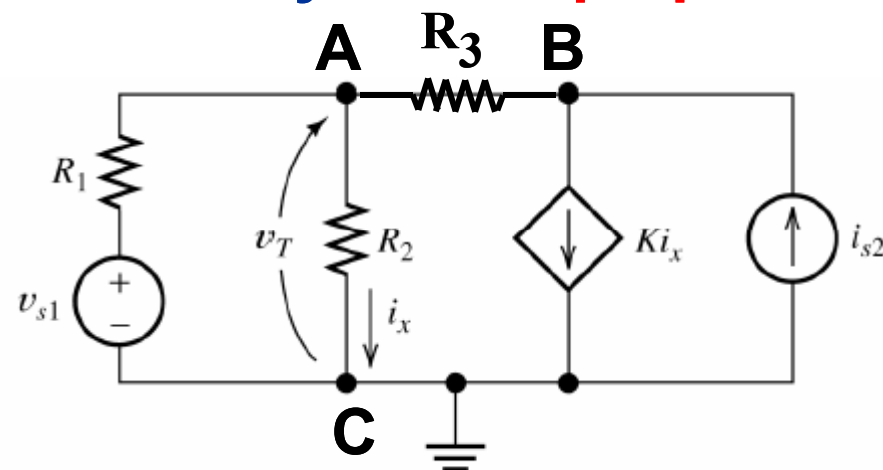Two equations for I''_x and I''_{R_1} and solve for each.



Step 2 :

$$\text{Then } I_x = I'_x + I''_x$$



$$\text{and } I_{R_1} = I'_{R_1} + I''_{R_1}$$

$$\text{and } V_A = V'_A + V''_A$$



ESc201, Lecture 4: Circuit Analysis – Laboratory

Esc 201A Expt. 1

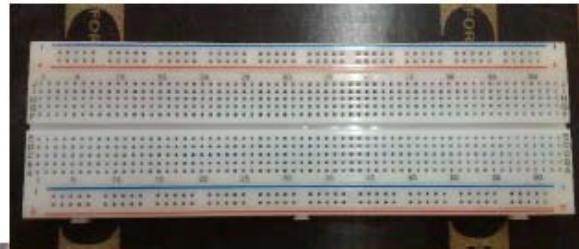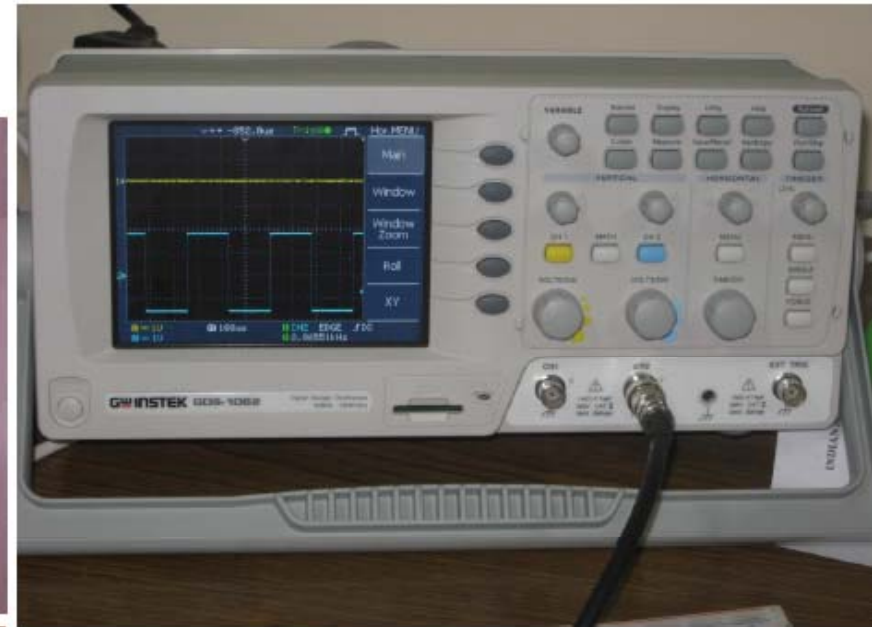



ESc201, Lecture 4: Circuit Analysis – **Laboratory**

