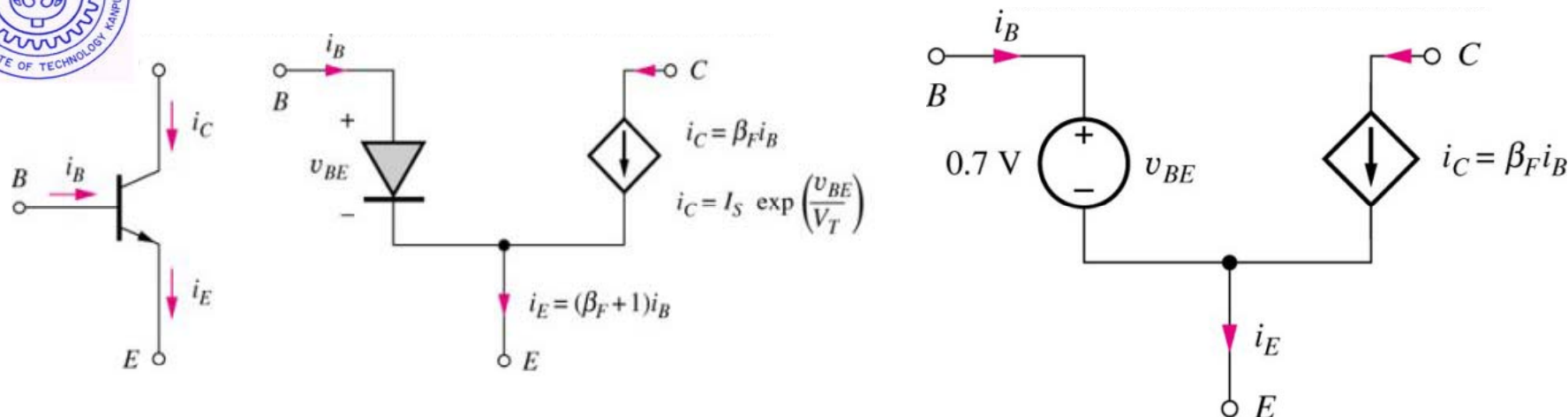




## ESc201, Lecture 19: Bipolar Junction Transistor (Small signal Model)




Current in base-emitter diode is amplified by common-emitter current gain  $\beta_F$  and appears at collector-base and collector currents are exponentially related to base-emitter voltage.

Base-emitter diode is replaced by constant voltage drop model ( $V_{BE} = 0.7 \text{ V}$ ) since it is forward-biased in forward-active region.

DC base and emitter voltages differ by 0.7 V diode voltage drop in forward-active region.


$$R_{BB} = R_1 \parallel R_2$$

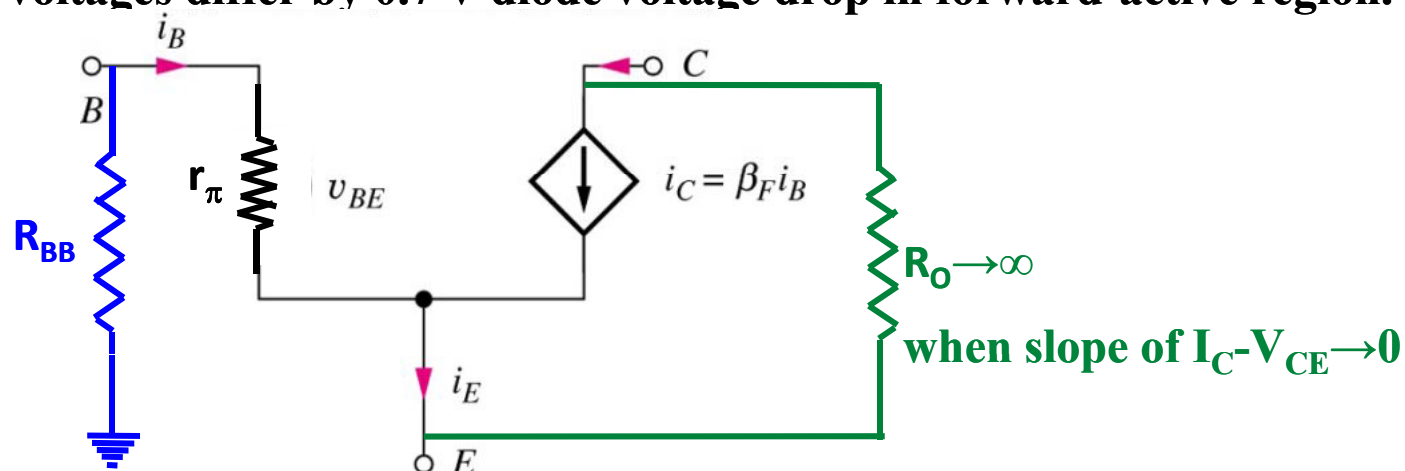Later use just  $R_B$  instead of  $R_{BB}$ .





## ESc201, Lecture 19: Bipolar Junction Transistor (A.C. small signal Model)

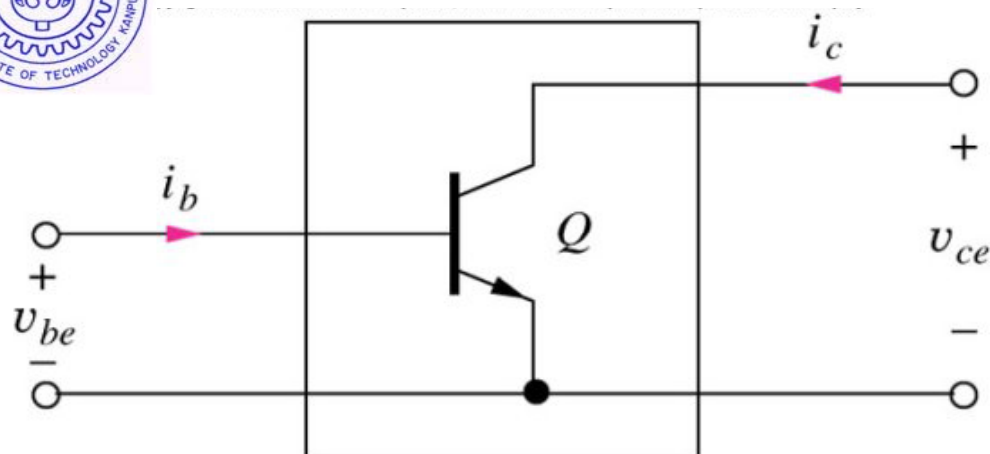

Using 2-port y-parameter network, the port variables can represent either time-varying part of total voltages and currents or small changes in them away from Q-point values.

$$\begin{aligned} i_b &= y_{11}v_{be} + y_{12}v_{ce} \\ i_c &= y_{21}v_{be} + y_{22}v_{ce} \end{aligned}$$

$$I_B = \frac{I_C}{\beta_F} = \frac{I_E}{\beta_F + 1} \cong \frac{I_{E_s} \times e^{V_{BE}/V_T}}{\beta_F}$$

$$y_{11} = \left. \frac{i_b}{v_{be}} \right|_{v_{ce}=0} = \left. \frac{\partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}} = \frac{I_C}{\beta_o V_T}$$

$$\begin{aligned} y_{21} &= \left. \frac{i_c}{v_{be}} \right|_{v_{ce}=0} = y_{21} = \left. \frac{\beta_o i_b}{v_{be}} \right|_{v_{ce}=0} \\ &= \left. \frac{\beta_o \partial i_B}{\partial v_{BE}} \right|_{Q\text{-point}} = \frac{I_C}{V_T} \end{aligned}$$

Assume that D.C.  $\beta_F = \text{A.C. } \beta_o$  and Transistor in forward active (CE reverse biased).

$$y_{12} = \left. \frac{i_b}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_B}{\partial v_{CE}} \right|_{Q\text{-point}} = 0$$


$$\begin{aligned} y_{22} &= \left. \frac{i_c}{v_{ce}} \right|_{v_{be}=0} = \left. \frac{\partial i_C}{\partial v_{CE}} \right|_{Q\text{-point}} \\ &= \frac{I_C}{V_A + V_{CE}} \cong 0 \end{aligned}$$

With the assumption that  $V_A \rightarrow \infty$  (slope = 0)



## ESc201, Lecture 19: Bipolar Junction Transistor (Small signal Model)

### Hybrid-Pi Model of BJT

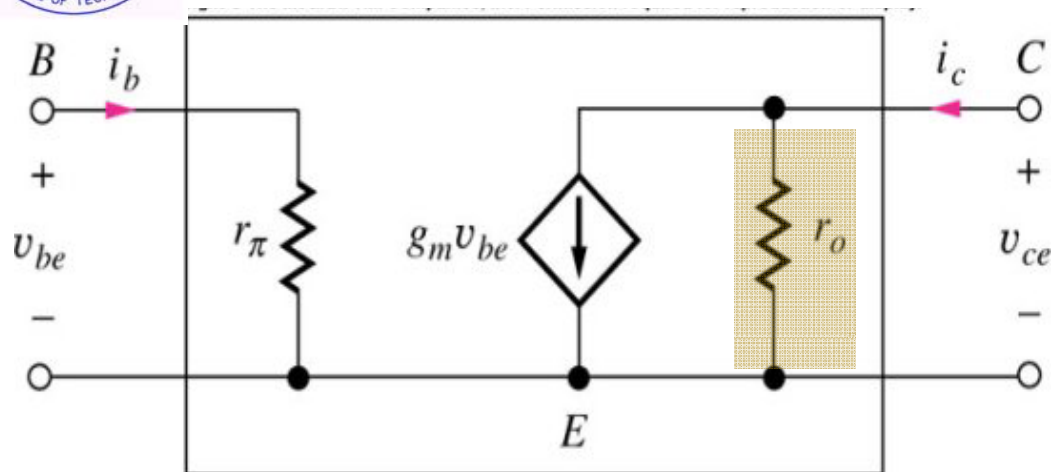


Input resistance =  $r_\pi$  (but there could be capacitance in parallel from the depletion layer capacitance for high frequency considerations)

$$\text{Transconductance} = y_{21} = g_m = \frac{I_C}{V_T}$$

$$\text{Input resistance} = r_\pi = \frac{1}{y_{21}} = \frac{\beta_o V_T}{I_C} = \frac{\beta_o}{g_m}$$


$$\text{Output resistance} = r_o = \frac{1}{y_{22}} = \frac{V_A + V_{CE}}{I_C} \cong \frac{V_A}{I_C} \rightarrow \infty (\text{Open})$$

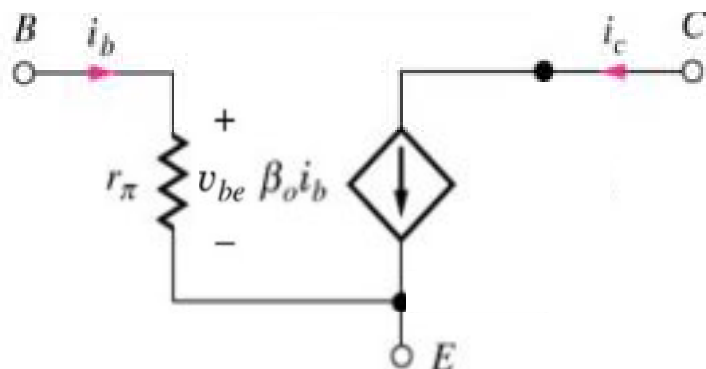Voltage-controlled current source  $g_m v_{be}$  can be transformed into current-controlled current source, as has been used earlier.



$$v_{be} = i_b r_\pi, \therefore g_m v_{be} = g_m i_b r_\pi = \beta_o i_b \quad \text{and} \quad i_c = \beta_o i_b + \frac{v_{ce}}{r_o} \cong \beta_o i_b \Big|_{r_o \rightarrow \infty}$$

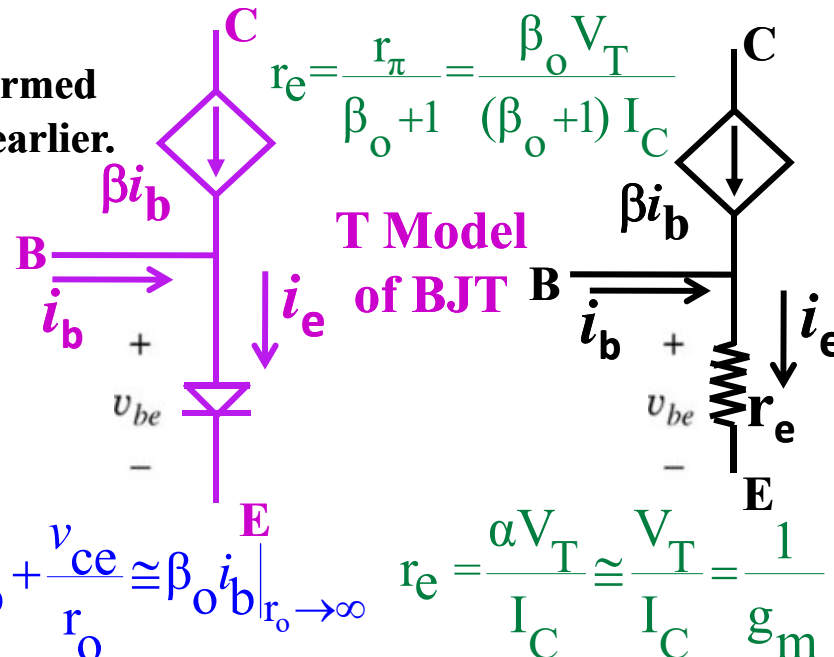Therefore Small-signal parameters are controlled by the Q-point biasing.



T Model of BJT




$$r_e = \frac{\alpha V_T}{I_C} \cong \frac{V_T}{I_C} = \frac{1}{g_m}$$


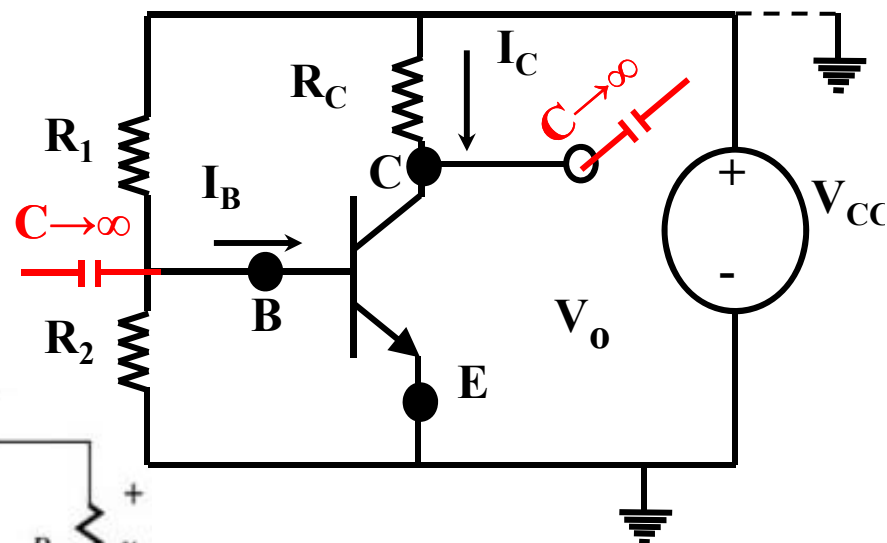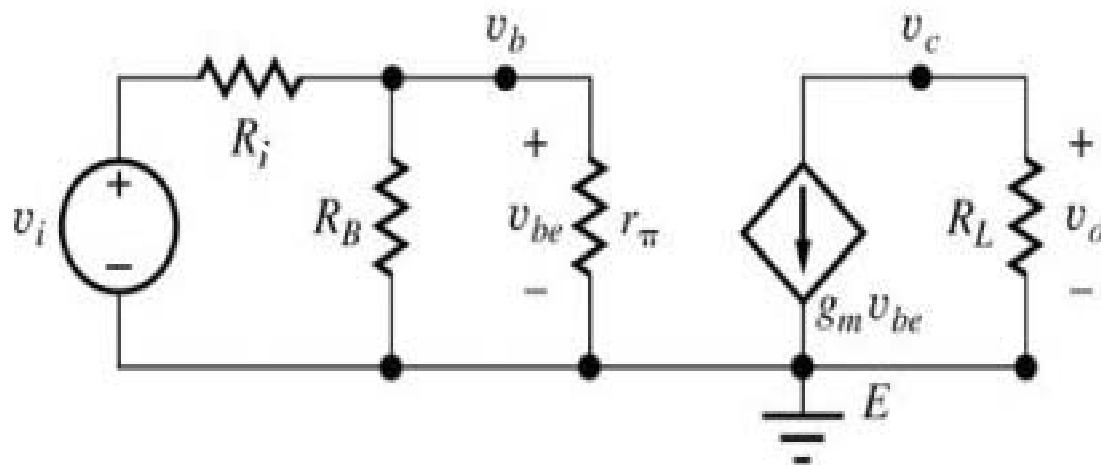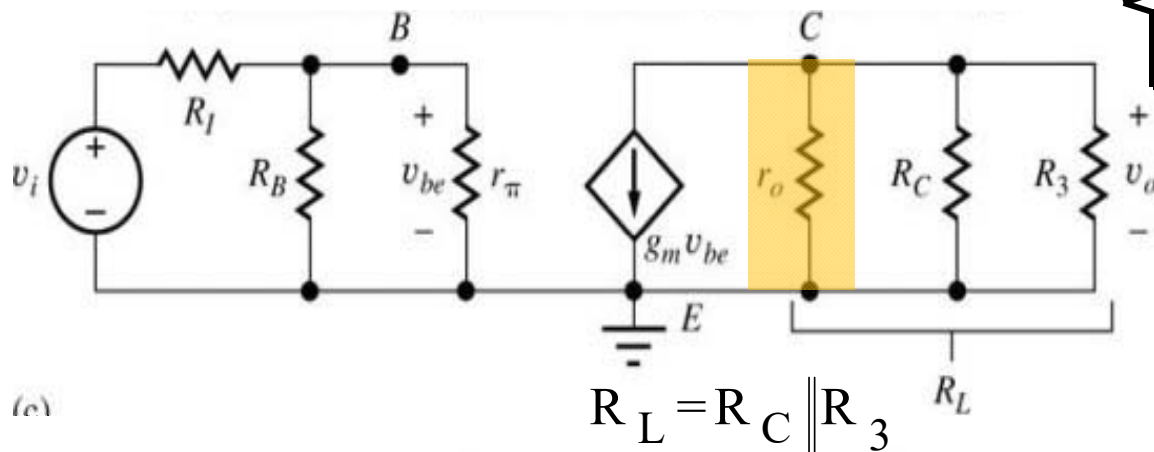
## ESc201, Lecture 19: Bipolar Junction Transistor (Small signal Model)

When Capacitor coupled output is taken, then the voltage offset at  $V_o$  does not matter, so  $V_o$  is chosen to give maximum swing.

$$A_{v_{\text{Transistor}}} = \frac{v_c}{v_b} = \frac{v_o}{v_{be}} = -g_m R_L$$



$$A_v = \frac{v_o}{v_i} = \left( \frac{v_o}{v_{be}} \right) \left( \frac{v_{be}}{v_i} \right)$$

$$= -g_m R_L \left( \frac{v_{be}}{v_i} \right)$$

$$A_v = -g_m R_L \left[ \frac{R_B \parallel r_\pi}{R_i + (R_B \parallel r_\pi)} \right]$$

Input potential divider



## ESc201, Lecture 19: Bipolar Junction Transistor (Biasing under different cases)

The story of how some students in the laboratory could not do the Transistor

Amplifier experiment as their Transistor went into saturation has been related to you in the class. This was due to variation of  $\beta$  over a wide range. How can one go around this problem?

Add a resistor to the emitter ( $R_E$ ). For large  $\beta$  there would be a larger voltage drop across  $R_C$  and  $R_E$ . Voltage drop across  $R_C$  changes  $V_{CE}$  but unless the drop is very large it would not take it into saturation. All it would do is reduce the dynamic range.

Whereas Voltage drop across  $R_E$  reduces  $V_{BE}$ , thus providing a feedback to reduce  $I_C$  and restores the currents closer to the design. BUT THERE CAN BE NO FREE LUNCH

$$v_o = -i_c(R_C \parallel R_{L'}) = -\alpha i_e R_L$$



$$r_e = \frac{\beta_o}{g_m(\beta_o + 1)} = \frac{\alpha}{g_m} \cong \frac{1}{g_m}$$

$$v_b = i_e(r_e + R_E)$$

$$A_v = \frac{v_o}{v_i} = \left( \frac{v_o}{v_b} \right) \left( \frac{v_b}{v_i} \right) = - \frac{\alpha i_e R_L}{i_e(r_e + R_E)} \left( \frac{v_b}{v_i} \right)$$

$$= - \frac{\alpha i_e R_L}{i_e(r_e + R_E)} \frac{i_i [R_B \parallel ((\beta + 1)(r_e + R_E))]}{i_i \{ R_i + [R_B \parallel ((\beta + 1)(r_e + R_E))] \}}$$
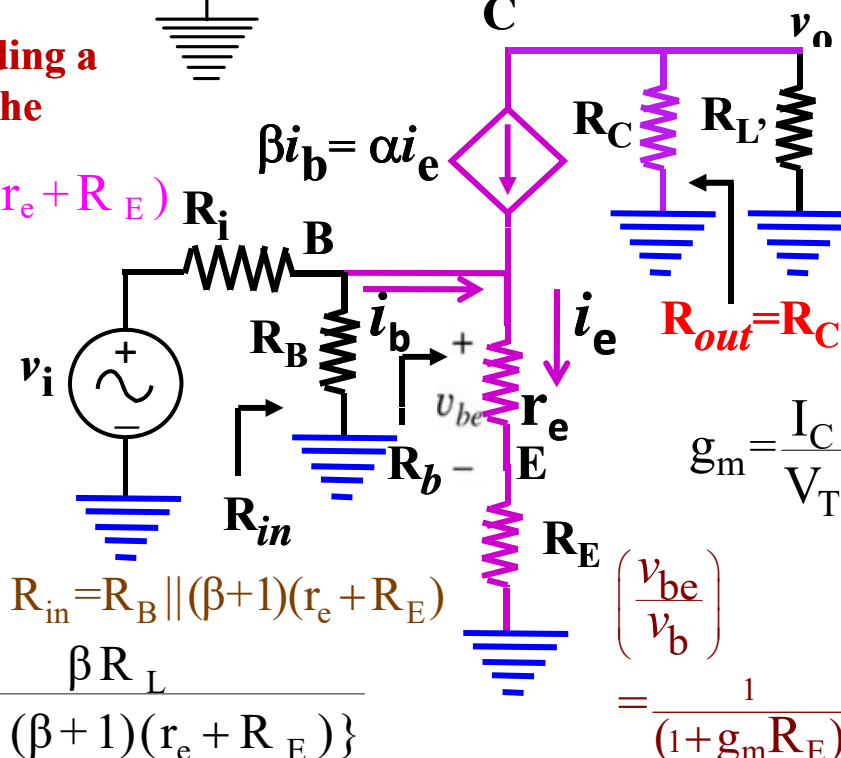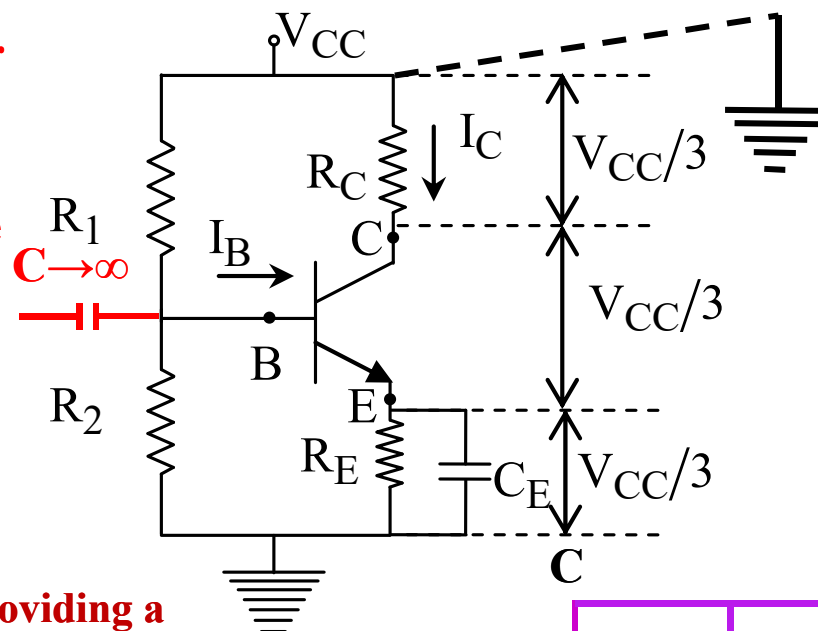
$$\cong - \frac{(\beta/(\beta + 1)) R_L}{(r_e + R_E)} \frac{(\beta + 1)(r_e + R_E)}{\{ R_i + (\beta + 1)(r_e + R_E) \}} = - \frac{\beta R_L}{\{ R_i + (\beta + 1)(r_e + R_E) \}}$$





## ESc201, Lecture 19: Bipolar Junction Transistor (Small signal Model)

### Effect of adding $R_E$

1. The voltage gain is now less dependent on  $\beta$ .
2. The input resistance is increased by a factor of  $(1+g_m R_E)$ .
3. The base to collector voltage gain is reduced by  $1/(1+g_m R_E)$
4. For the same nonlinear distortion the input can be increased by a factor of  $(1+g_m R_E)$
5. The frequency response is significantly improved.

As a particular example for  $\beta=100$ ,  $R_L = 4.12\text{k}\Omega$ ,  $R_E=300\Omega$ , and a  $C_{\text{Base-Collector}}=0.5\text{pF}$

Without  $R_E$  the values are :

$A_{\text{mid freq}} = -153$ ,  $f_H = 1.56\text{ MHz}$ ,  $\text{GBWP} = 239\text{ MHz}$ .

With  $R_E$  the values are :

$A_{\text{mid freq}} = -11.0$ ,  $f_H = 13.9\text{ MHz}$ ,  $\text{GBWP} = 153\text{ MHz}$ .

And  $R_{in}$  must have increased by approximately a ratio of  $(153/11)=14$  times.