




ESc201, Lecture 36: Digital counters

Check if the arguments are correct !!!

Remember that when the clock shifts the register SR-flip-flop also changes state depending on what was stored on its input earlier. So shift and state change happens at the same time.

 00101100 → (1's Compliment) 11010011 → (2's Compliment) 11010100



Inputs		Outputs	
S	R	Present State, Q_n	Next State, Q_{n+1}
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	invalid	
1	1	invalid	




ESc201, Lecture 36: Digital counters

Synchronous 3-bit Binary UP counter


Q_A Q_B Q_C

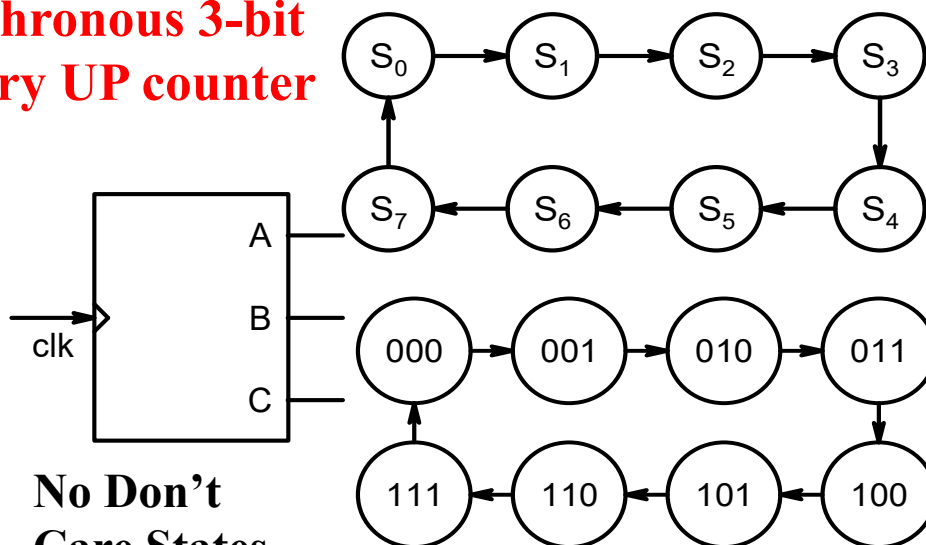0 0 0
0 0 1
0 1 0
0 1 1
1 0 0
1 0 1
1 1 0
1 1 1



No Don't Care States

PS			NS					
A	B	C	A	B	C	T_A	T_B	T_C
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	1
0	1	0	0	1	1	0	0	1
0	1	1	1	0	0	1	1	1
1	0	0	1	0	1	0	0	1
1	0	1	1	1	0	0	1	1
1	1	0	1	1	1	0	0	1
1	1	1	0	0	0	1	1	1

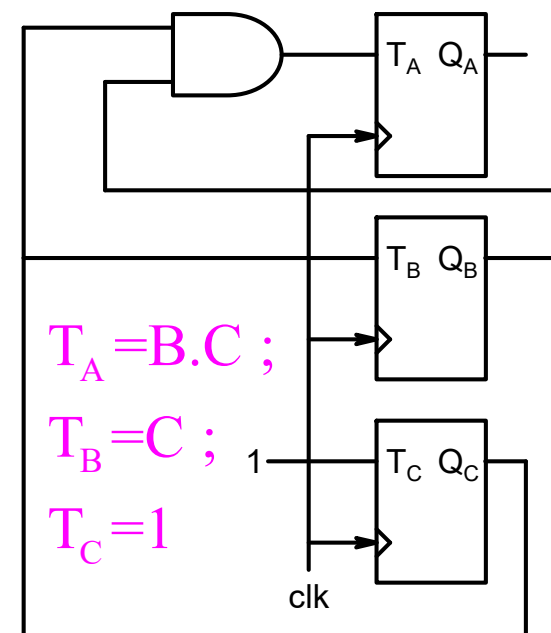

$T_B = C$

AB \ C	00	01	11	10
0				
1	1	1	1	1

$T_A = B.C$

AB \ C	00	01	11	10
0				
1		1	1	

$T_C = 1$



ESc201, Lecture 36: Digital counters

Synchronous 4-bit Binary UP counter

T FF toggles when T=1

4-bit Down Counter

Q_A	Q_B	Q_C	Q_D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1
1	0	1	0
1	0	1	1
1	1	0	0
1	1	0	1
1	1	1	0
1	1	1	1
0	0	0	0

$-Q_D$ toggles every clock cycle

$-Q_C$ toggles only when $Q_D = 1$

$-Q_B$ toggles only when Q_C & $Q_D = 1$

$-Q_A$ toggles only when $Q_B, Q_C, Q_D = 1$



$-Q_D$ toggles every clock cycle

$-Q_C$ toggles only when $Q_D = 0$

$-Q_B$ toggles only when both Q_C & $Q_D = 0$

$-Q_A$ toggles only when $Q_D, Q_C, Q_B = 0$

REQUIRED FOR ADC

  

Q_A	Q_B	Q_C	Q_D
1	1	1	1
1	1	1	0
1	1	0	1
1	1	0	0
1	0	1	1
1	0	1	0
1	0	0	1
1	0	0	0
0	1	1	1
0	1	1	0
0	1	0	1
0	1	0	0
0	0	1	1
0	0	1	0
0	0	0	1
0	0	0	0
1	1	1	1



ESc201, Lecture 36: Digital counters

Binary Coded Decimal (BCD): each decimal digit is coded as a 4-bit binary no.

BCD counter from 0 to 99 25 = 0010 0101

Decade counter

Modulo-10 Counter

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1


A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

Modulo-5 Counter

0 0 1 0
0 0 0 1
0 0 0 0
0 0 0 1
0 0 0 0
0 0 0 0
0 0 0 0
0 0 0 0

A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1

 0 0 0 0
1 0 0 1
0 0 0 1
0 0 0 0
1 0 0 1
0 0 0 1
0 0 0 0
0 0 0 0







ESc201, Lecture 36: Digital counters

Counter with Unused States

PS			NS								
A	B	C	A	B	C	J_A	K_A	J_B	K_B	J_C	K_C
0	0	0	0	0	1	0	X	0	X	1	X
0	0	1	0	1	0	0	X	1	X	X	1
0	1	0	1	0	0	1	X	X	1	0	X
1	0	0	1	0	1	X	0	0	X	1	X
1	0	1	1	1	0	X	0	1	X	X	1
1	1	0	0	0	0	X	1	X	1	0	X

  

A \ BC	$J_A = B$			
	00	01	11	10
0	0	0	X	1
1	X	X	X	X

$$J_A = B, K_A = B, J_B = C, K_B = 1$$

$$J_C = \bar{B}, K_C = 1$$



After synthesizing the circuit, one needs to check, if by chance the counter goes into one of the unused states, after one or more clock cycles, it enters a used state and then remains among the used states

We can see that if by chance the counter goes into unused states 111 or 011, then after a clock cycle it enters one of the used states.



ESc201, Lecture 36: Digital counters


Counter as frequency divider

  

A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

A	B	C	D
0	0	0	0
0	0	0	1
0	0	1	0
0	0	1	1
0	1	0	0
0	1	0	1
0	1	1	0
0	1	1	1
1	0	0	0
1	0	0	1

 Example: From a frequency of 10KHz, generate the following signal of frequency 1KHz.




This will have a frequency of 1KHz but it will not have the same waveform



ESc201, Lecture 36: Digital counters

 Example: From 10KHz, generate the following signal of frequency 2KHz




A	B	C
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0

Modify

A	B	C
0	0	0
0	0	1
1	1	0
1	1	1
1	0	0



A divide by 5 counter is required that has 5 states.

4-bit Parallel Data Output

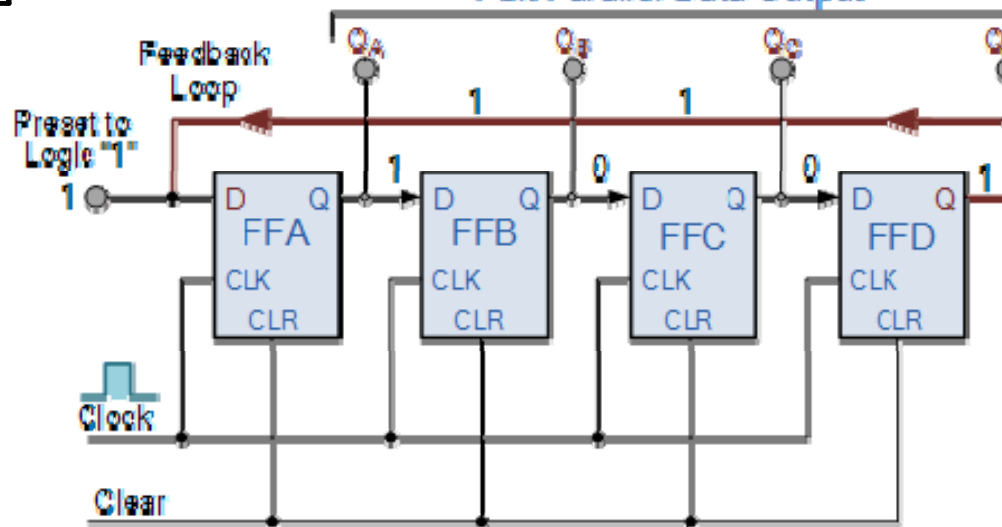

Ring Counter

T ₃	T ₂	T ₁	T ₀
0	0	0	1
0	0	1	0
0	1	0	0
1	0	0	0

 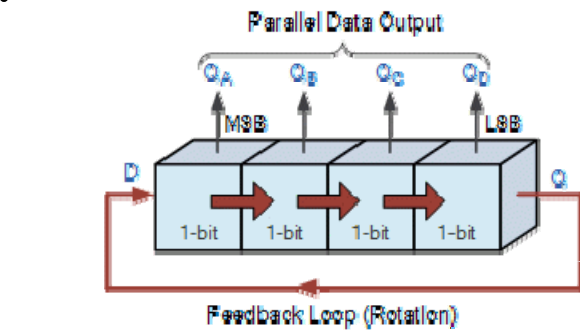



ESc201,
Lecture 36:
Digital
BCD Ripple
counters

Q_n	Q_{n+1}	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

