



## ESc201, Lecture 24: Operational Amplifier (LIMITATIONS) Input Offset Voltage.

**(MOS input OpAmps have high  $R_i$  but also higher  $V_{OS}$  than BJT input)**


With inputs being zero, the amplifier output rests at some dc voltage level instead of zero. The equivalent dc input offset voltage is:  $V_{OS} = V_o / A$  (1-10 mV).

The amplifier is connected as voltage-follower to give output voltage equal to offset voltage.

To include effect of offset voltage,  $v_o = A \left( v_{id} + \frac{v_{ic}}{CMRR} + V_{OS} \right)$

If  $v_{id} = 0$ ,
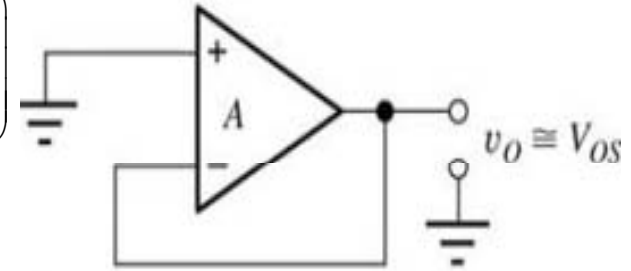
$$v_o = A \left( \frac{v_{ic}}{CMRR} + V_{OS} \right) = A(V_{OS}) \quad \therefore CMRR = \frac{v_{ic}}{V_{OS}} \mu V / V$$



### Limitations : Bandwidth (Unity Gain Cut-off) $f_T$ :

OpAmps are compensated for stability to suppress unwanted oscillations, which introduces a pole in the frequency response characteristic, typically  $\sim 5$ -10Hz.


After that, the gain rolls off at -20dB/decade. The frequency at which the magnitude of this gain becomes unity (i.e., 0 dB) is known as the unity gain cut-off frequency ( $f_T$ ). Where :

$$A_{v_{op. loop}} \times f_{op. loop} = A_{v_{feedback}} \times f_{3dB} = A_{v_{op. loop}} \times f_T = A_{v_{feedback}} \times f_{3dB}$$

For a closed-loop feedback amplifier:

$$A_V(s) = \frac{A_o / \{1 + A_o R_1 / (R_1 + R_2)\}}{1 + s / \{[1 + A_o R_1 / (R_1 + R_2)] \omega_{3dB}\}} = \frac{A_v(0)}{1 + s / \omega_H}$$
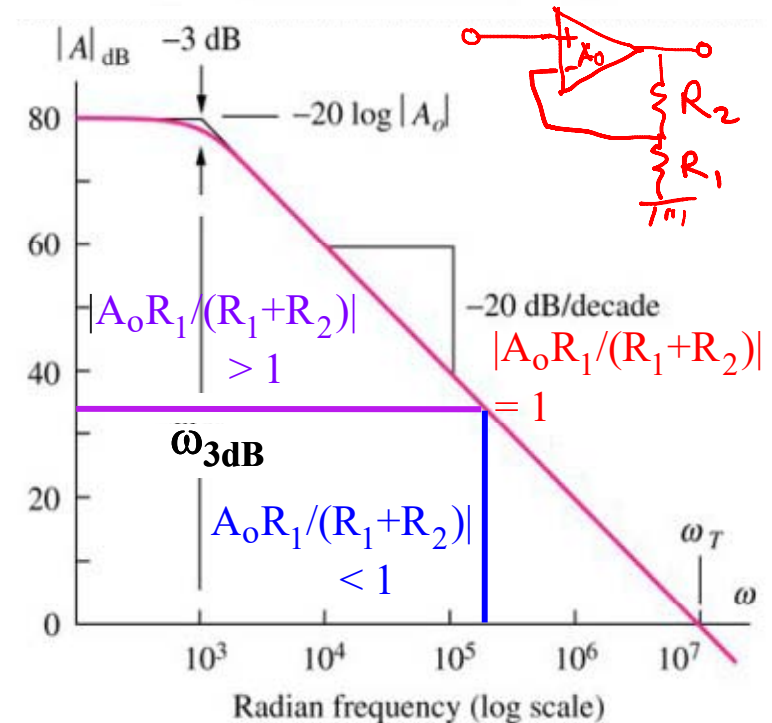
$$\omega_H = [1 + A_o R_1 / (R_1 + R_2)] \omega_{3dB} = \frac{\omega_T}{A_v(0)}$$





## ESc201, Lecture 25: Operational Amplifier (NON\_IDEAL)

**Practical OpAmps have limited output voltage and current ranges.**

1. **Voltage:** Limited to several volts less than power supply span.
2. **Current:** Limited by additional circuits (to limit power dissipation or protect against accidental short circuits).
3. **Current limit** specified as minimum load resistance that the amplifier can drive with a given voltage swing. Eg:  $i_o = V_{\max}/R_L$ .

### **Large Signal Limitations: Slew Rate and Full-Power Bandwidth**

### ***Effect of SR Limitation***


$$v_o = V_M \sin \omega t \quad \text{or} \quad \left. \frac{dv_o}{dt} \right|_{\max} = V_M \cos \omega t \big|_{\max} = V_M \cos \omega \Delta t \big|_{\Delta t \rightarrow 0} = V_M \omega$$

For no signal distortion,  $V_M \omega \leq \text{SR} \therefore V_M \leq \frac{\text{SR}}{\omega}$


Full-power bandwidth is highest frequency at which a full-scale signal can be developed.

$$f_M \leq \frac{\text{SR}}{2\pi V_{\text{FS}}}$$

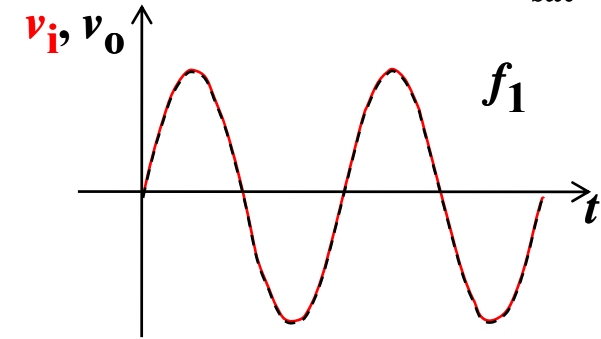
No SR Limitation within  $V_{\text{sat}}$



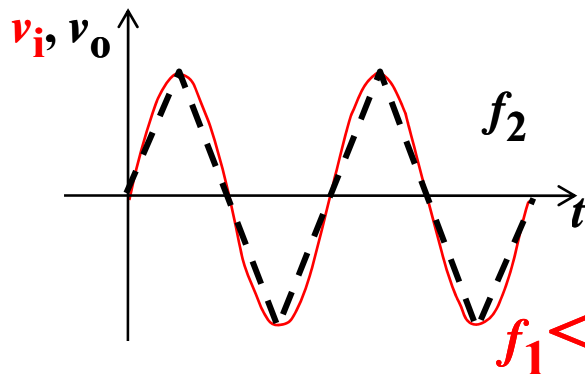Moderate SR Limitation within  $V_{\text{sat}}$




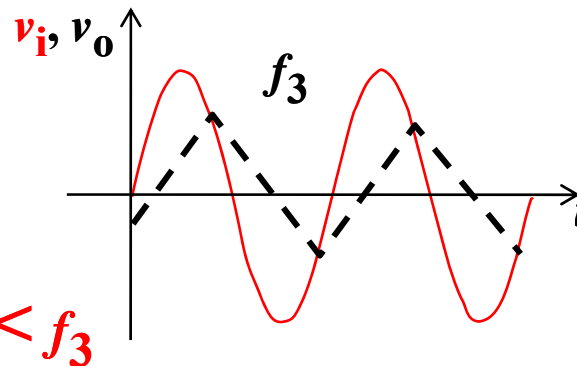Severe SR Limitation within  $V_{\text{sat}}$



Moderate SR

Limitation with  $V_{\text{sat}}$

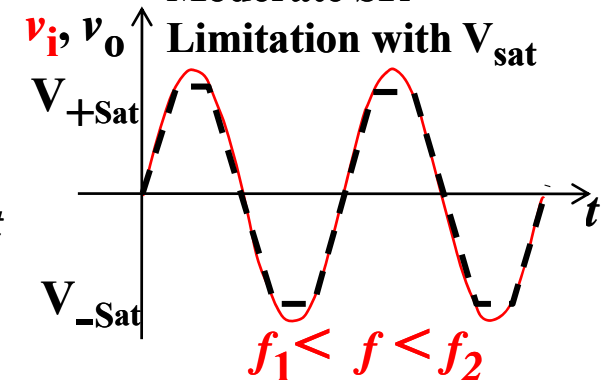




## ESc201, Lecture 25: Operational Amplifier

**OpAmp Filters:** Passive Filters (High Pass, Low Pass, and Band Pass that you have studied) does not have any gain and hence the signal can be degraded after a few operations. Filters using OpAmps (Known as Active Filters) help in providing gain also.

### Low Pass Filter

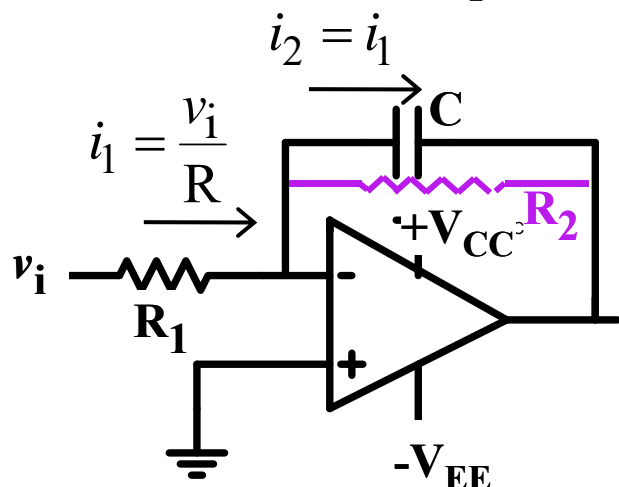

$v_-$  is at virtual ground. At low frequency  $X_C \rightarrow \infty$ . Hence gain is very large,  $v_o \rightarrow$  **large**. But at high frequency  $X_C \rightarrow 0$ . Hence gain is low,  $v_o \rightarrow 0$ . That's a Low Pass characteristic. Cutoff would be given by  $R_1 C$ .

**But in the pass band  $v_o \rightarrow$  large, can be accepted for the Pass Band as the out would be saturated, but this filter would not work as even outside the pass band the output is large enough to saturate the output.**

**Remedy :** Add a Resistor  $R_2$  in parallel to the capacitor. Where  $K = -R_2/R_1$  and  $\omega_c = 1/(R_2 C)$ .

$$\frac{v_o}{v_i} = -\frac{Z}{R_1} = -\frac{R_2 \parallel \frac{1}{j\omega C}}{R_1} = \frac{R_2 / R_1}{1 + j\omega C R_2} = \frac{K}{1 + j\frac{\omega}{\omega_c}}$$

Other complicated versions also exist where instead of adding  $R_2$  in parallel to  $C$ , a  $R_2$ - $C_2$  combination is used at the  $v_-$  node.

Also works as an Integrator

$\tau = R_1 C =$  integration time constant .

$$\frac{v_i}{R_1} = -C \frac{dv_o}{dt} \quad \text{or} \quad v_o(t) = -\frac{1}{R_1 C} \int v_i dt + V_o$$

Practical integrators would have  $R_2$  to avoid saturation, but design becomes tricky as  $R_2 C$  should in no way affect  $\tau$  . Also, the capacitor needs to be discharged periodically to prevent any undesirable accumulation of charges in it. That's why not much used.




## ESc201, Lecture 25: Operational Amplifier
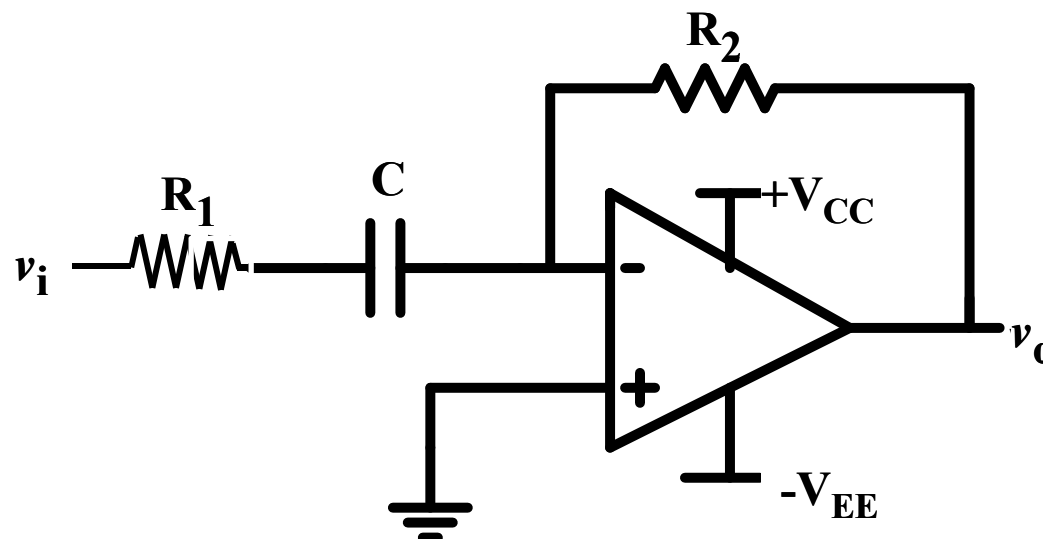
### High Pass Filter

$$i_1 = \frac{v_i}{R_1 + \frac{1}{j\omega C}} = i_2 = -\frac{v_o}{R_2}$$

$$\text{or } \frac{v_o}{v_i} = -\frac{j\omega R_2 C}{1 + j\omega R_1 C} = \frac{j\frac{\omega}{\omega_1}}{1 + j\frac{\omega}{\omega_c}}$$




$\omega_1 = 1/(R_2 C)$  is the lower zero crossing frequency, &  $\omega_c = 1/(R_1 C)$  is the lower cutoff frequency. Hence  $\omega_1 \ll \omega_c$  is required. Here  $|\text{Pass Band Gain}| = \omega_c/\omega_1 = R_2/R_1$ .

Also works as a Differentiator by removing  $R_1$ .

$$i_1 = C \frac{dv_i}{dt} = i_2 = -\frac{v_o}{R_2} \text{ or } v_o = -R_2 C \frac{dv_i}{dt} = -\tau \frac{dv_i}{dt}$$

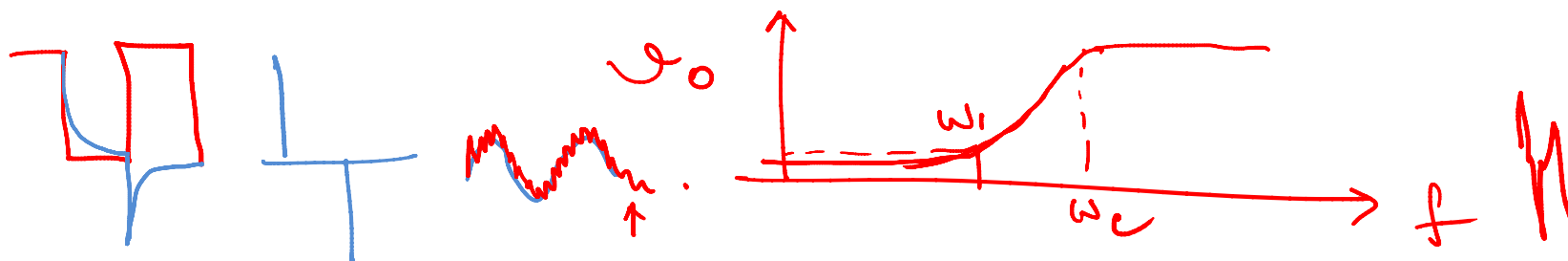The circuit tends to amplify the noise present at the input (**the derivative of a noise spike can be dangerously large !**) Therefore Occasionally used for waveshaping only.






## ESc201, Lecture 25: Operational Amplifier

### Low Pass filter Example

- Design second-order low-pass filter with maximally flat response.
- Given data:  $f_H = 5 \text{ kHz}$
- Analysis:  $C_1 = 2C_2 = 2C$   
and  $R_1 = R_2 = R$ .

$$R = \frac{1}{\sqrt{2}\omega_0 C} \quad Q = \frac{1}{\sqrt{2}}$$
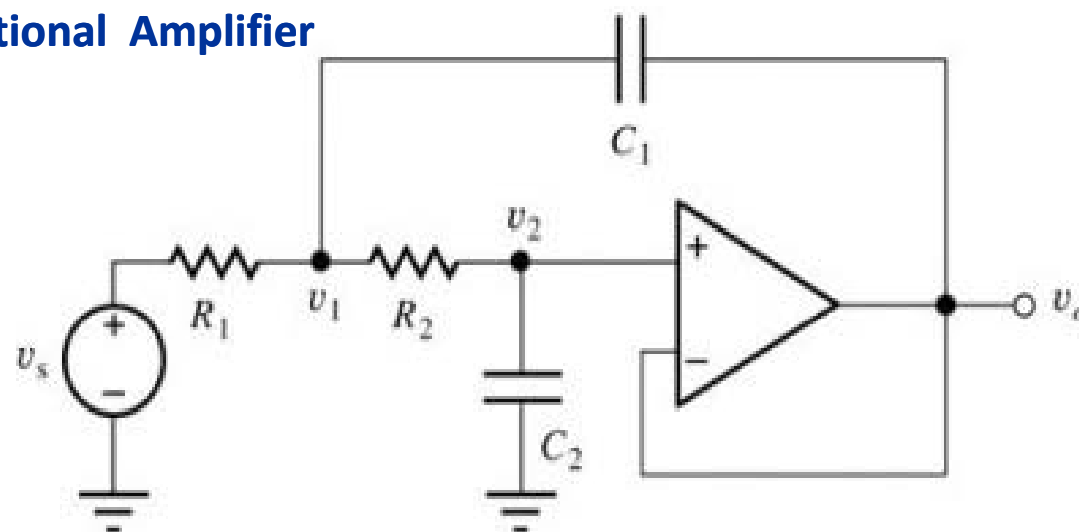
$$A_{LP}(s) = \frac{V_o(s)}{V_s(s)} = \frac{\frac{G_1 G_2}{C_1 C_2}}{s^2 + s \frac{G_1 + G_2}{C_1} + \frac{G_1 G_2}{C_1 C_2}}$$



$$A_{LP}(s) = \frac{s^2}{s^2 + s \frac{\omega_0}{Q} + \omega_0^2}$$

$$\omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$Q = \sqrt{\frac{C_1}{C_2}} \frac{\sqrt{R_1 R_2}}{R_1 + R_2}$$

Often, circuits are designed with  $C_1 = C_2 = C$ .

$1/(\omega_0 C)$  is the reactance of  $C$  at  $\omega_0$ ,  $R$  is 30% smaller than this value. Thus impedance level of filter is set by  $C$ . If impedance level is too low, op amp will not be able to supply current required to drive feedback network.

At 5 kHz, for a  $0.01 \mu\text{F}$  capacitor,  $\frac{1}{\omega_0 C} = \frac{1}{10^4 \pi (10^{-8})} = 3180 \Omega$ ,  $R = \frac{3180 \Omega}{\sqrt{2}} = 2250 \Omega$

Final values:  $R_1 = R_2 = 2.25 \text{ kW}$ ,  $C_1 = 0.02 \mu\text{F}$ ,  $C_2 = 0.01 \mu\text{F}$