





# ESc201, Lecture 15: Unregulated Power Supply 1

## Half Wave Rectifier

Ripple Voltage :  $V_r = V_{\max} - V_{\min}$   
 $= V_s - V_{\text{on}} - V_{\min}$

$V_L \approx V_{\text{DC}} + V_r(t)$

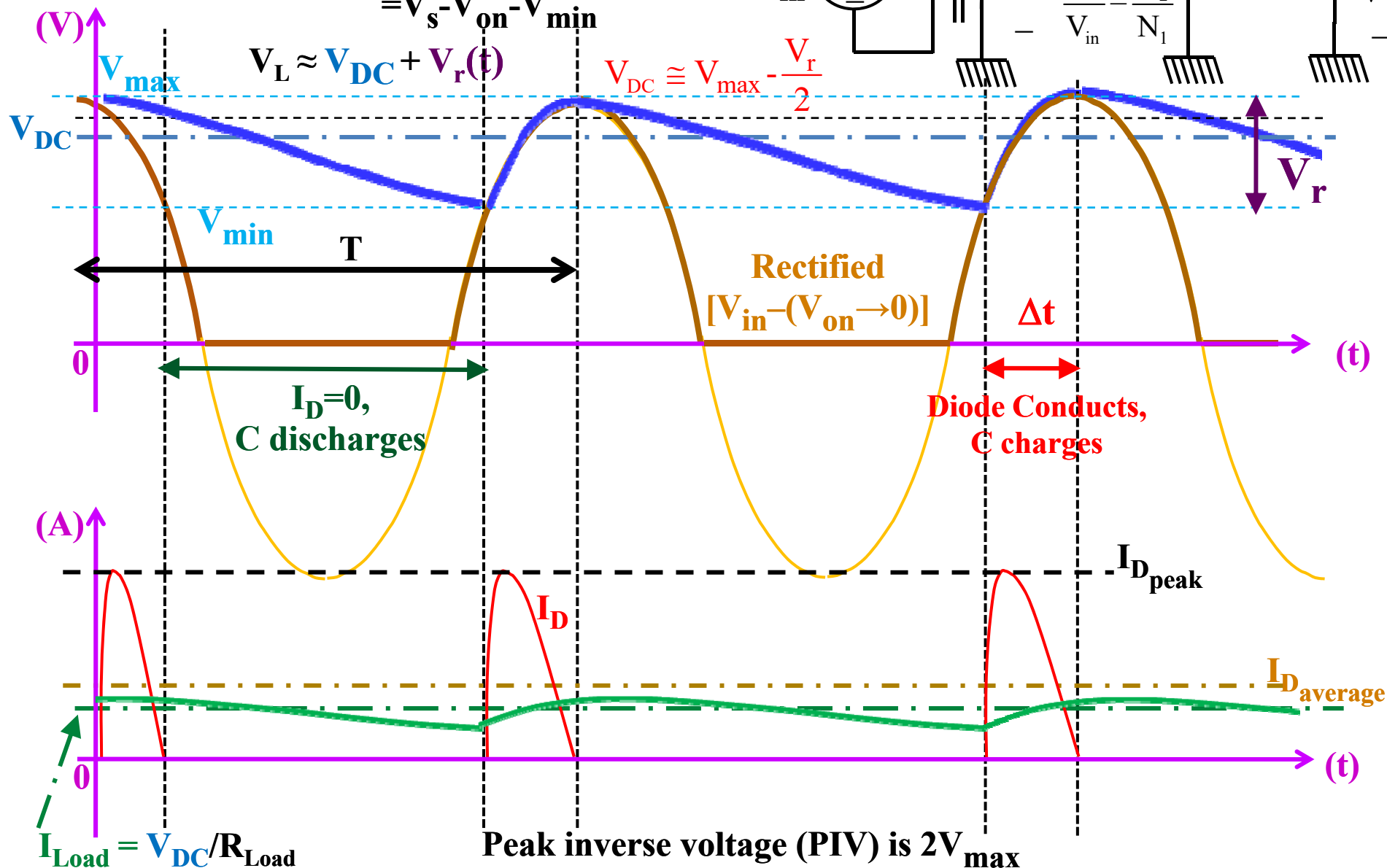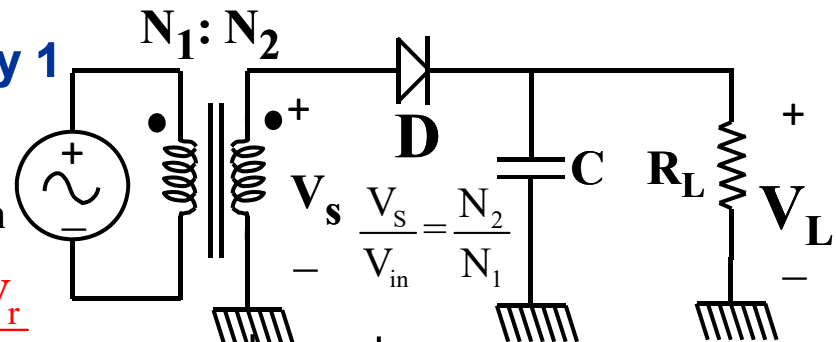
$V_{\text{DC}} \cong V_{\max} - \frac{V_r}{2}$




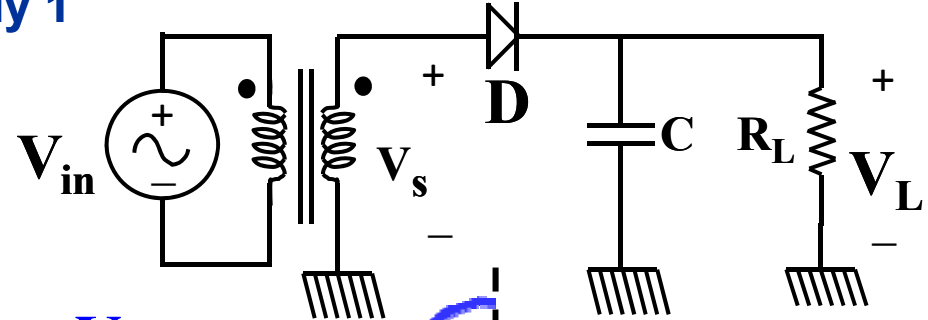
# ESc201, Lecture 15: Power Supply 1

220V rms  $V \rightarrow 311.13$  Peak  $V$



$$V_{DC} \cong V_{max} - \frac{V_r}{2}$$

$$CV_r = I_L(T - \Delta t) \cong I_L T \text{ or } V_r = \frac{I_L T}{C} = \frac{I_L}{\omega C / 2\pi}$$

For very small  $V_r$ ,  $V_{DC} \cong V_{max}$

$$v_c(t) = v_c(\infty) + \{v_c(0^+) - v_c(\infty)\} e^{-\frac{t}{RC}}$$

$$V_{min} = V_{max} - V_r = V_{max} e^{[-(T - \Delta t)/\tau]}$$

$$\cong V_{max} e^{-T/\tau} \cong V_{max} [1 - T/\tau]$$

$$T/\tau \ll 1, e^{-T/\tau} \cong [1 - T/\tau]$$

$$V_r = V_{max} \frac{T}{\tau} = V_{max} \frac{T}{R_L C}$$

$$I_{C, av} = I_{D, av} - I_{L, av} \quad I_{L, av} \cong I_L \cong V_{max} / R_L$$

Charge conservation gives

$$\text{Gained } I_{C, av} \Delta t = (I_{D, av} - I_L) \Delta t = \text{Lost } CV_r$$


$$\text{Or } (I_{D, av} - I_L) \left( \frac{1}{\omega} \sqrt{\frac{2V_r}{V_{max}}} \right) = I_L T = \frac{I_L}{\omega / 2\pi} = \frac{2\pi I_L}{\omega}$$

KCL at the output node at  $t = -\Delta t$

$$I_{D, av} = I_L \left[ 1 + \pi \sqrt{\frac{V_{max}}{2V_r}} \right] \quad I_{D, max} = C \frac{dV_s}{dt} \Big|_{t = -\Delta t} + I_L = -C\omega V_{max} \sin(-\Delta t\omega) + I_L \cong C\omega V_{max} \Delta t\omega + I_L$$



$$I_{D, max} = I_L \left[ 1 + 2\pi \sqrt{\frac{2V_{max}}{V_r}} \right] = I_L \left[ 1 + 2\pi \sqrt{2fCR_L} \right] \quad V_r \frac{I_L}{fC} \cong \frac{V_{max}}{R_L}$$

$$V_s = V_{max} \cos[\omega t]$$

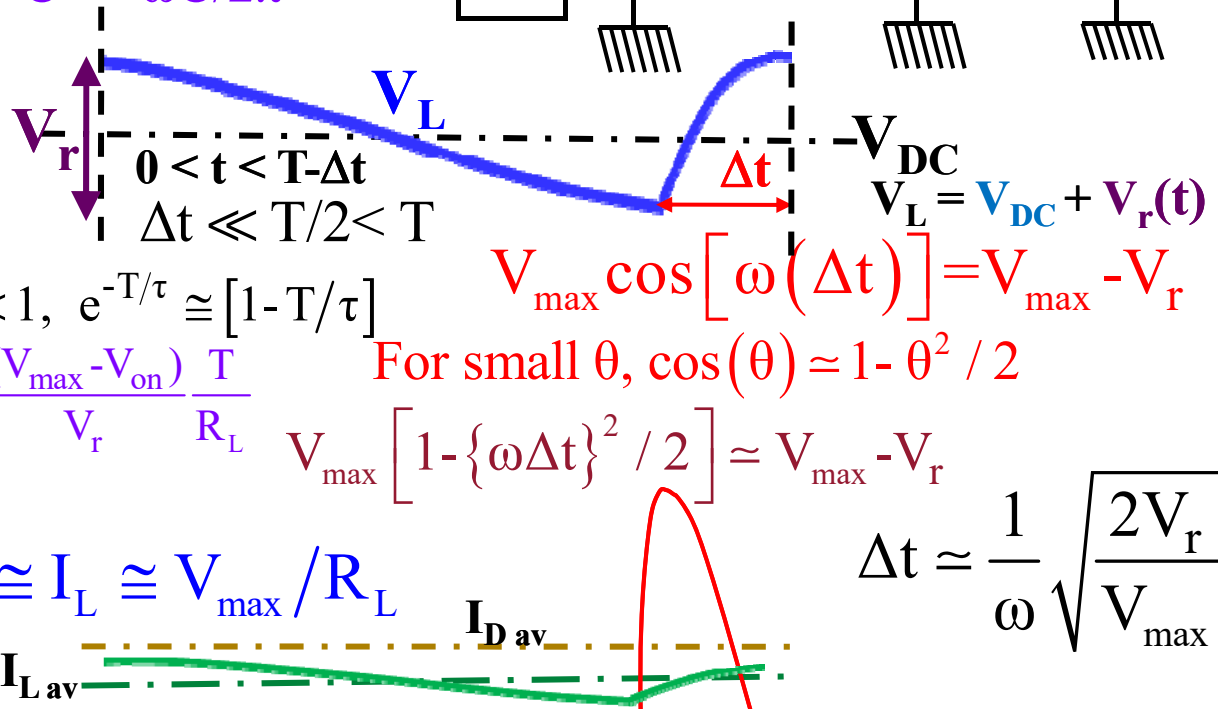



## ESc201, Lecture 15: Power Supply 1

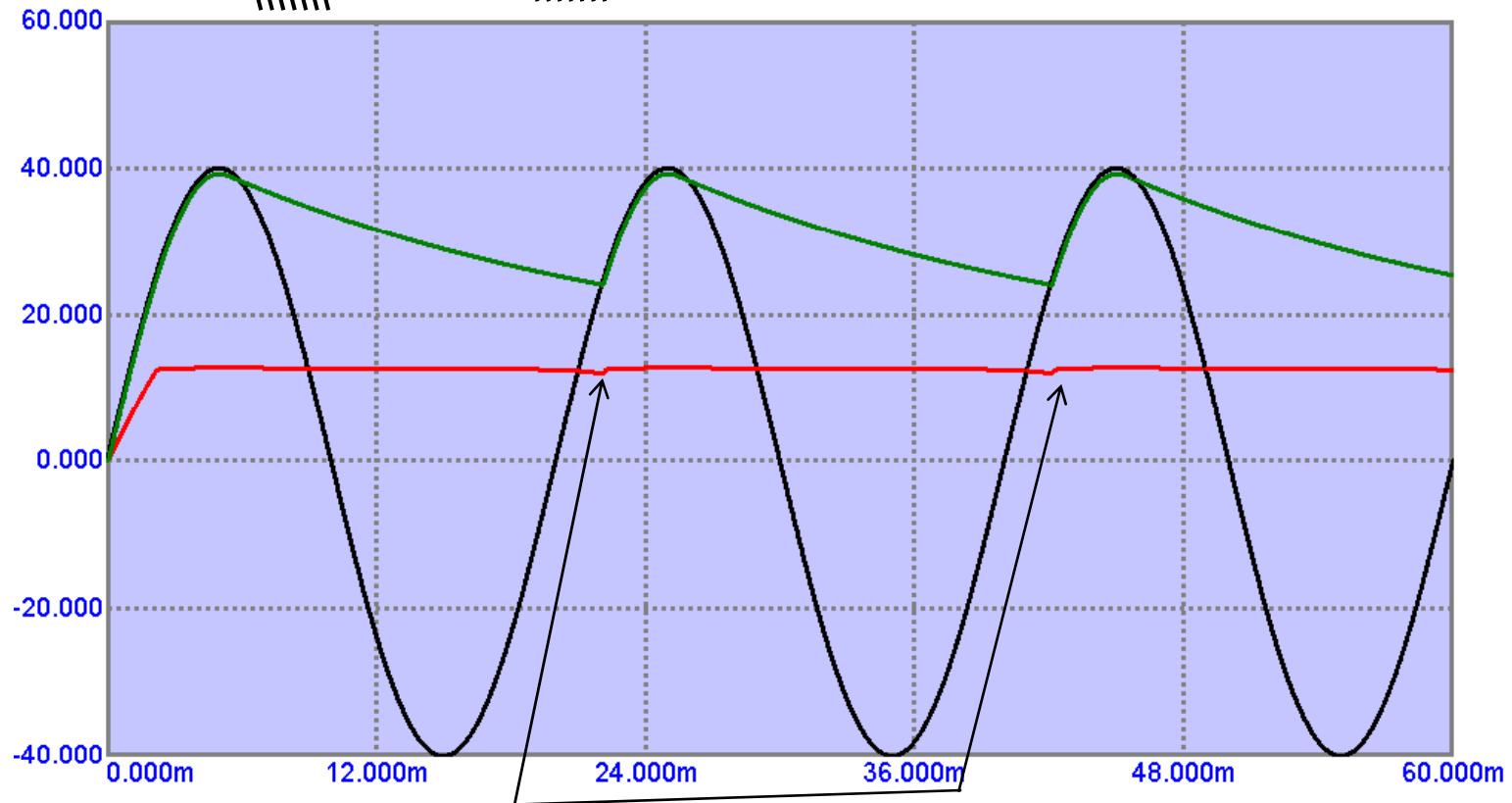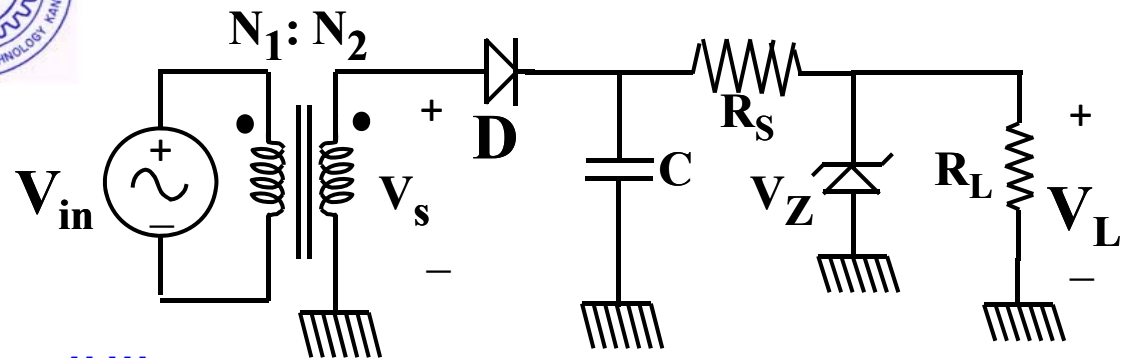



**Still some ripple due to finite resistance of the Zener is observed.**



## Full Wave Rectifier using a Center
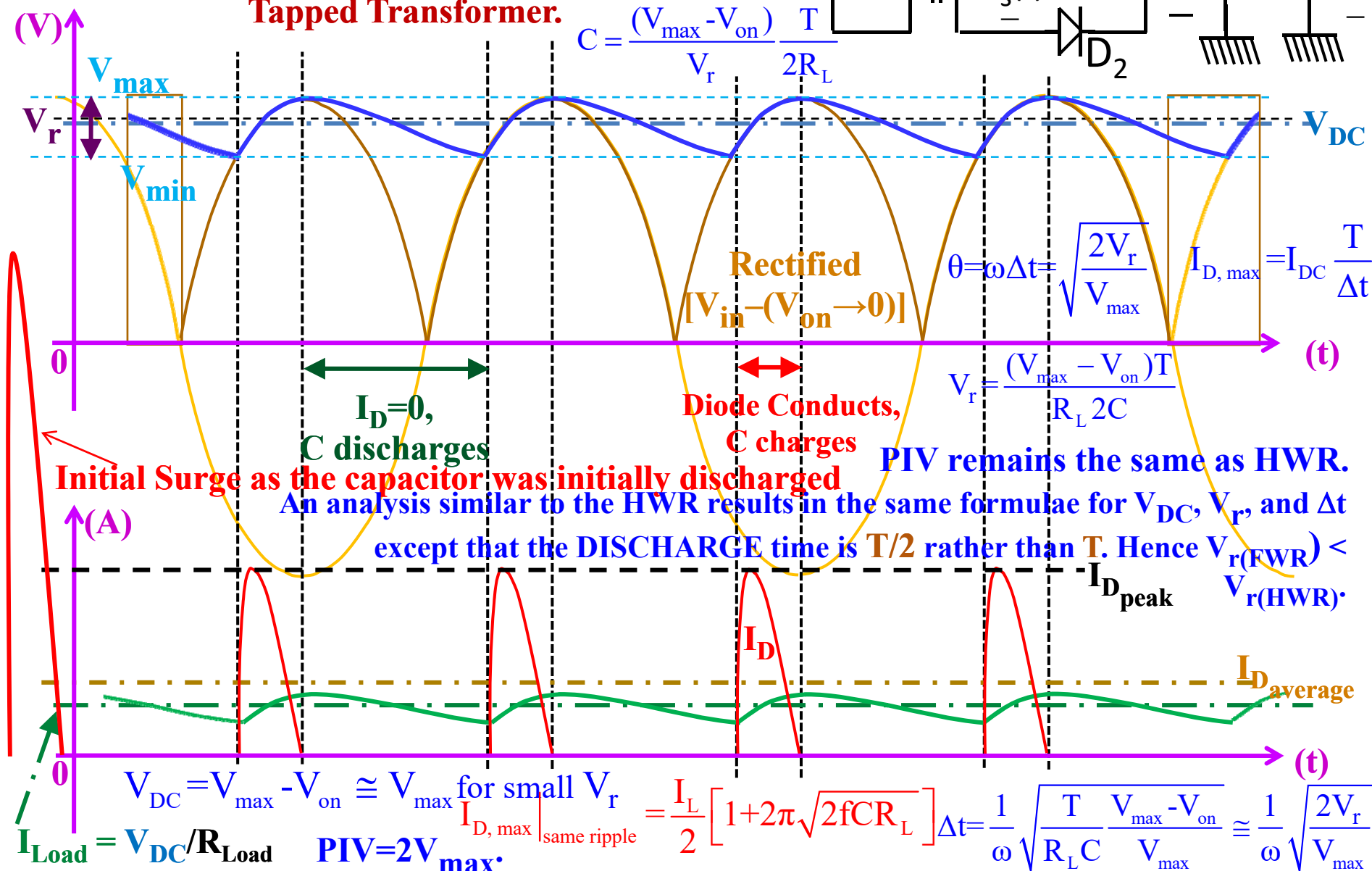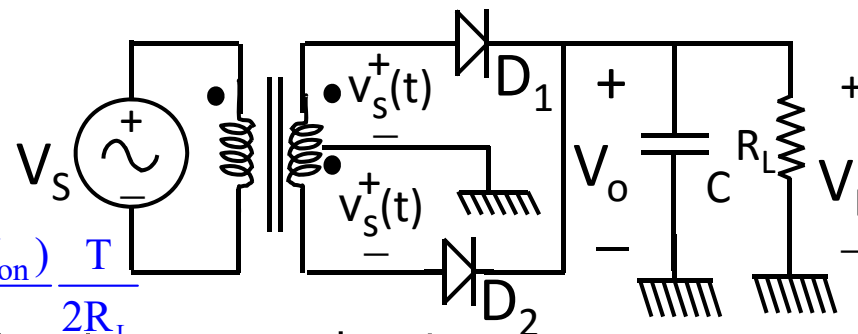
## Tapped Transformer.

$$C = \frac{(V_{\max} - V_{on})}{V_r} \frac{T}{2R_L}$$






## ESc201, Lecture 16: Power Supply

**Crossover Distortion :** For diodes, generally  $V_{on} \neq 0$ , even if  $r_F=0$  is assumed, and cannot conduct until  $V_{in}=V_D \geq V_{on}$ . This creates a dead-band of around  $2V_{on}$  at all the crossover points (i.e., points where the input signal crosses zero in the time axis). This problem becomes more acute if  $V_{max}$  is not much larger than  $V_{on}$  and for  $V_{max} \sim V_{on}$ , the entire signal is mixed up.

$\theta = \sin^{-1}(V_{on}/V_{max})$  = Angle of Crossover Distortion, appears 4 times in a complete cycle.

Hence the Total Crossover Distortion =  $(2\theta/\pi) \times 100\%$ .

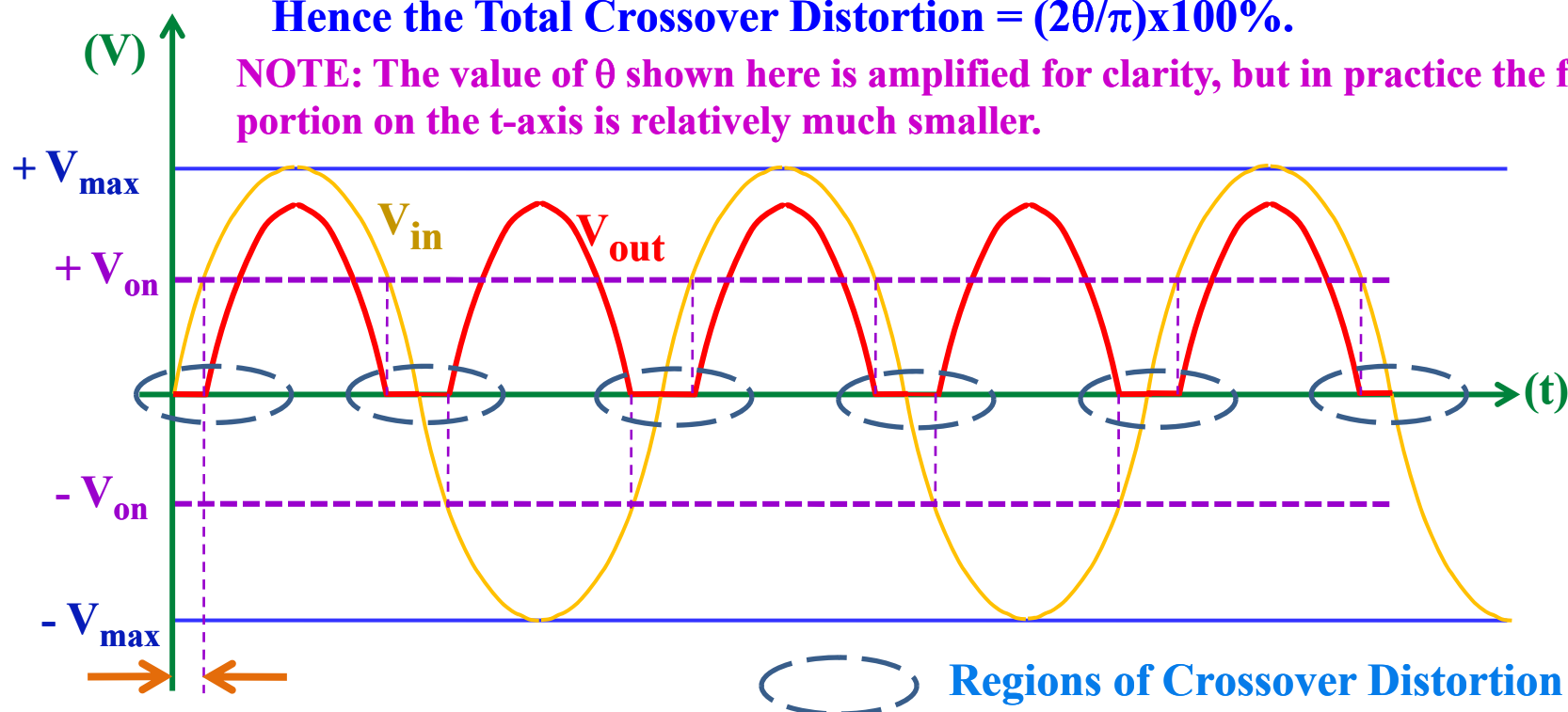NOTE: The value of  $\theta$  shown here is amplified for clarity, but in practice the flat portion on the t-axis is relatively much smaller.



Angle of no diode conduction ( $\theta$ )



## ESc201, Lecture 16: Power Supply

$$h = P.n \pm 1$$




where:

$n$  = an integer (1, 2, 3, 4...  $\infty$ ).

$h$  = harmonic order.

$P$  = the number of pulses of the rectifier.

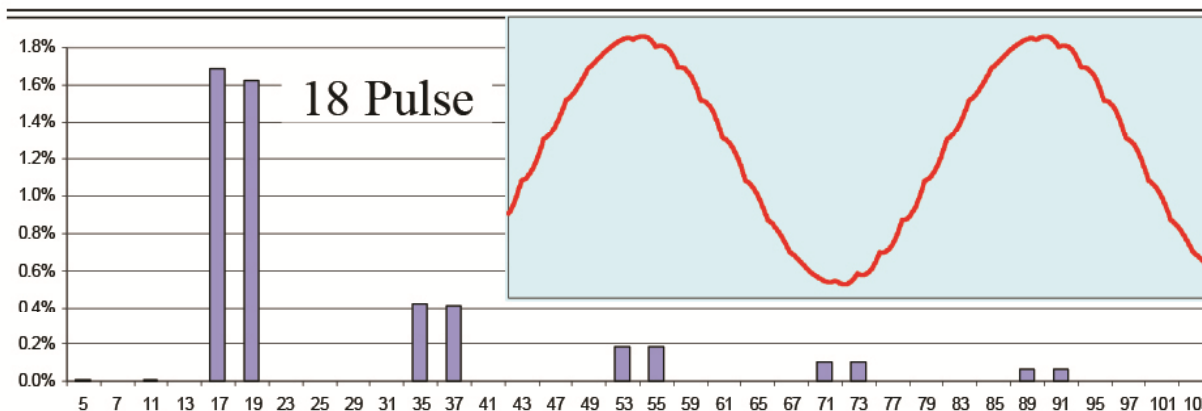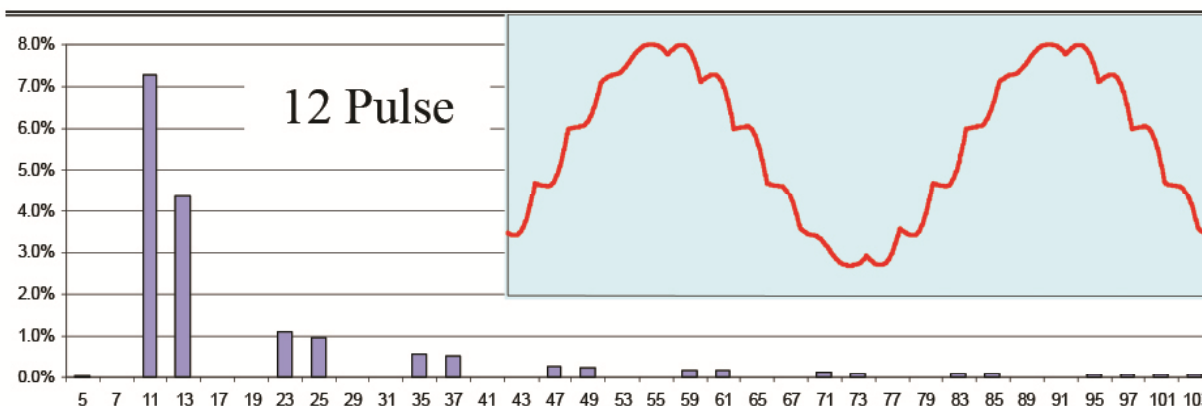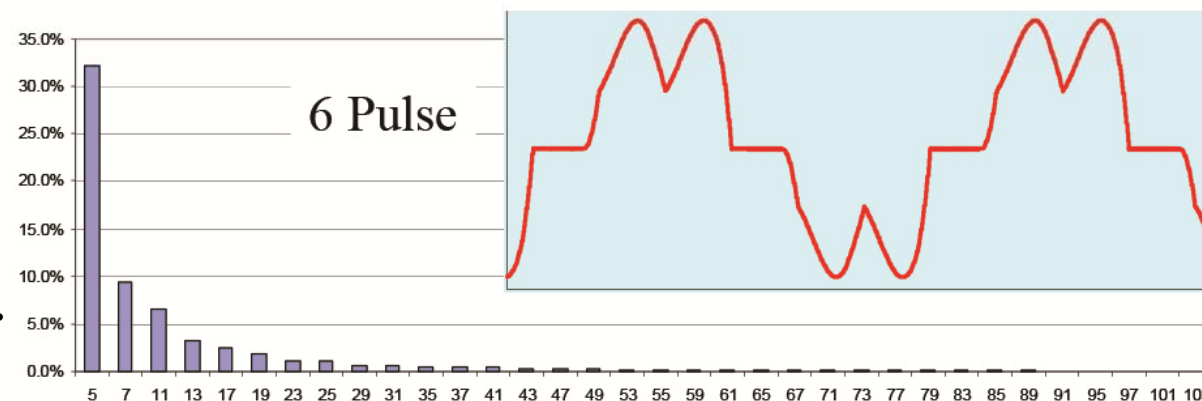There are some residual non-characteristic harmonics such as the 5th and 7th in 12 and 18-pulse topologies due to the non-ideal behaviour of the transformer causing angle phase errors



characteristic harmonics