





## ESC201 UDas Lec5 Electrical Energy storage

### Ideal Capacitor

$$q = C v$$

coulombs      farads      volts

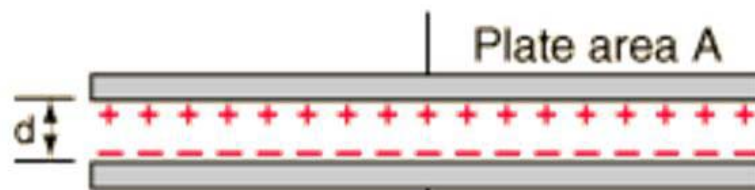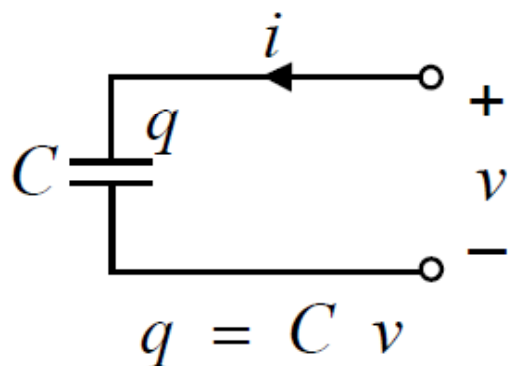

$$C = \frac{\epsilon A}{d} = \frac{k\epsilon_0 A}{d}$$

$$E = \frac{1}{2} C v(t)^2$$

For dc or steady state when the voltage does not vary with time. A capacitor under dc or steady state acts like an **open circuit (i=0)**.

$$i(t) = \frac{dq(t)}{dt} = \frac{d[Cv(t)]}{dt} = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_o}^t i dt + v(t_o)$$

$$i_1(t) = C \frac{dv_1(t)}{dt} \quad i_2(t) = C \frac{dv_2(t)}{dt}$$


$$\alpha i_1(t) + \beta i_2(t) = C \frac{d}{dt} (\alpha v_1(t) + \beta v_2(t)) = \alpha C \frac{dv_1(t)}{dt} + \beta C \frac{dv_2(t)}{dt}$$

**Therefore Capacitors linear elements. Hence Superposition, Combination rules, Thevenin/Norton are valid.**

From K. Rajawat




# Capacitor: series/parallel

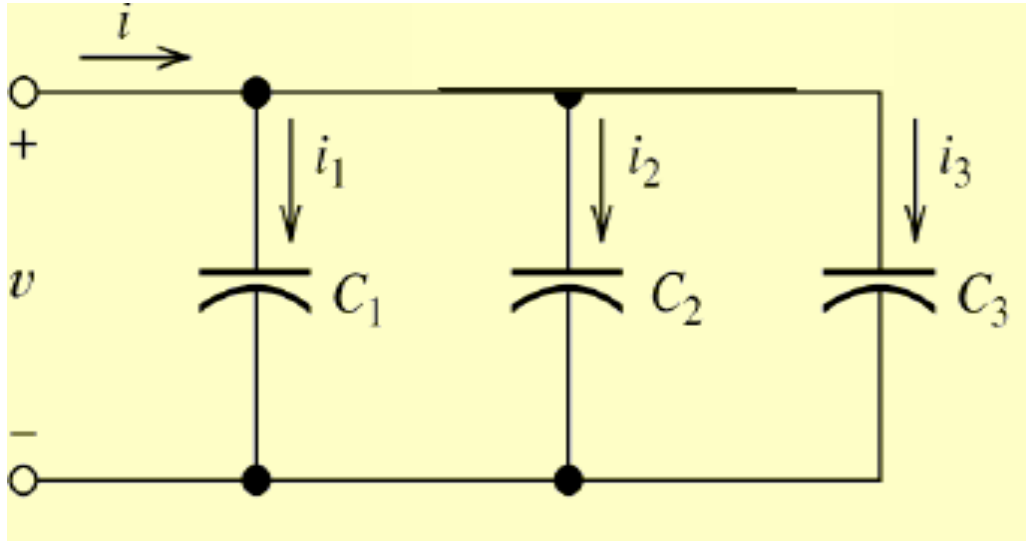

$$i = C \frac{dv}{dt}$$

$$C_{eq} = C_1 + C_2 + C_3$$

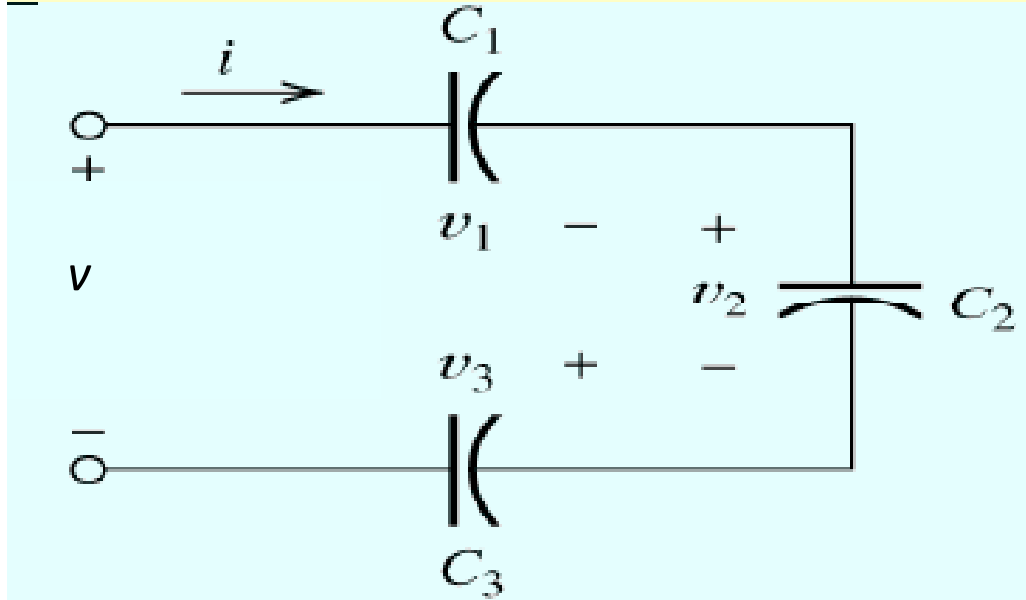

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$



# ESC201 UDas Lec5 Magnetic Energy storage

## Inductors


**Self inductance is defined as flux linked per unit current.**  
**Or  $L = \phi(t)/i(t)$ .**

$$\phi(t) = L \times i(t)$$

From Faraday's Law

e.m.f. generated is  $-\frac{d\phi}{dt}$


**Two things to remember:**

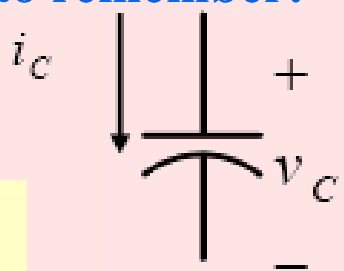

$$i_c = C \frac{dv_c}{dt}$$

**Voltage across a capacitor cannot change instantaneously**

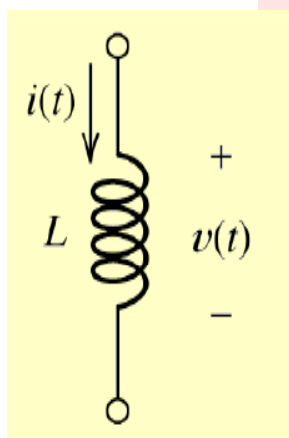**Instantaneous change in voltage implies infinite current!**



$$v = L \frac{di}{dt}$$


**Current through an inductor cannot change instantaneously**

**Instantaneous change in current implies infinite voltage!**

If  $\mu$  is the permeability of the core of the coil,  $N$  is the number of coil turns, for  $\ell$  (length of the coil)  $\gg r$  (mean radius of coil).

$$L = \frac{\mu N^2 \pi r^2}{\ell} \quad \text{Henry}$$
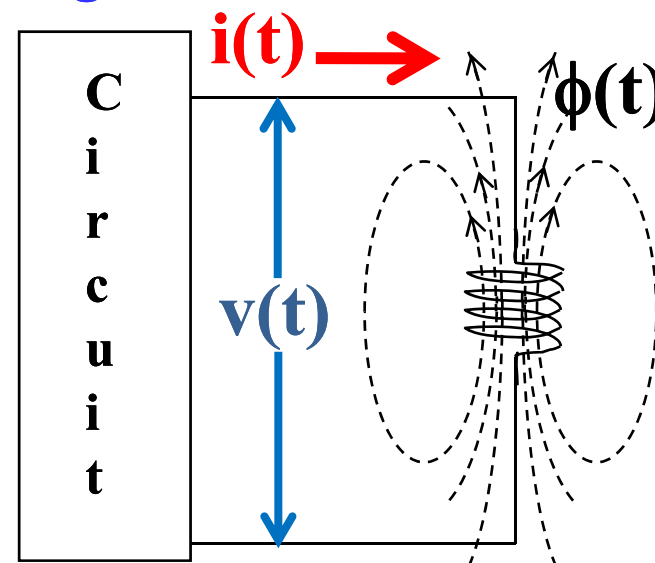
$$v(t) = \frac{d\phi(t)}{dt} = L \times \frac{di(t)}{dt}$$




**For dc or steady state when the current does not vary with time, an inductor acts like a short circuit ( $v=0$ )**




# Inductors: series/parallel


$$E = \frac{1}{2} Li(t)^2$$

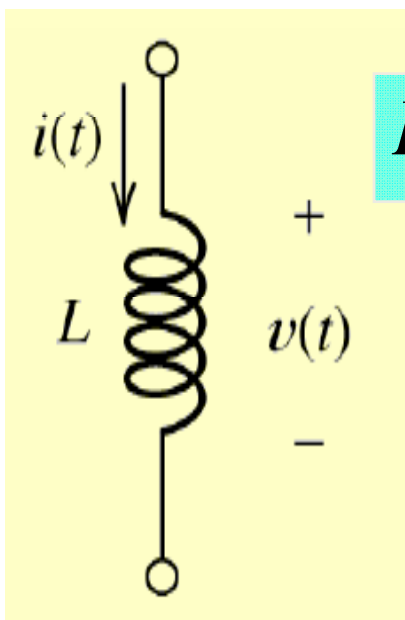

$$L_{eq} = L_1 + L_2 + L_3$$

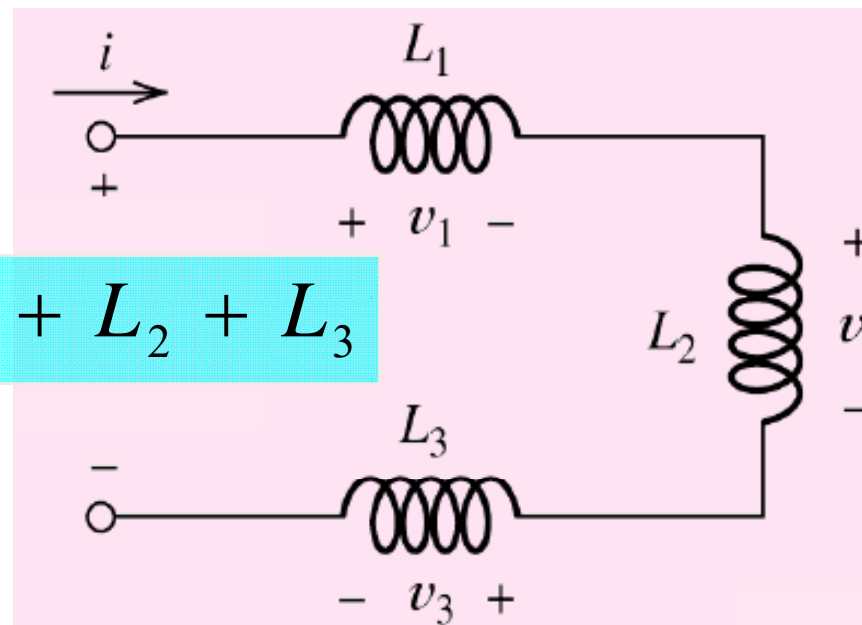
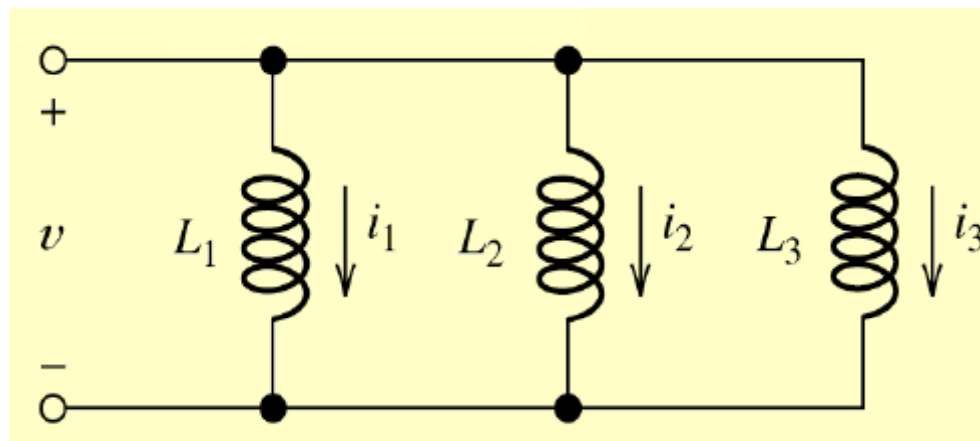
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$






## ESC201 UDas Lec5 Circuit equivalents


Not every circuit requires that all Node-voltages and Mesh-currents for a circuit be found, but to drive a load only those at the Load-Nodes and Load-Branch be found. Then it is unnecessary to do a full analysis on the circuit. Rather any equivalent circuit which provides the required information is sufficient.

**Thevenin's Theorem:** Any network containing independent and dependent sources and resistors, when viewed from the load, can be represented by an **equivalent voltage source**  $V_T$  in series with an **equivalent resistance**  $R_{Th}$

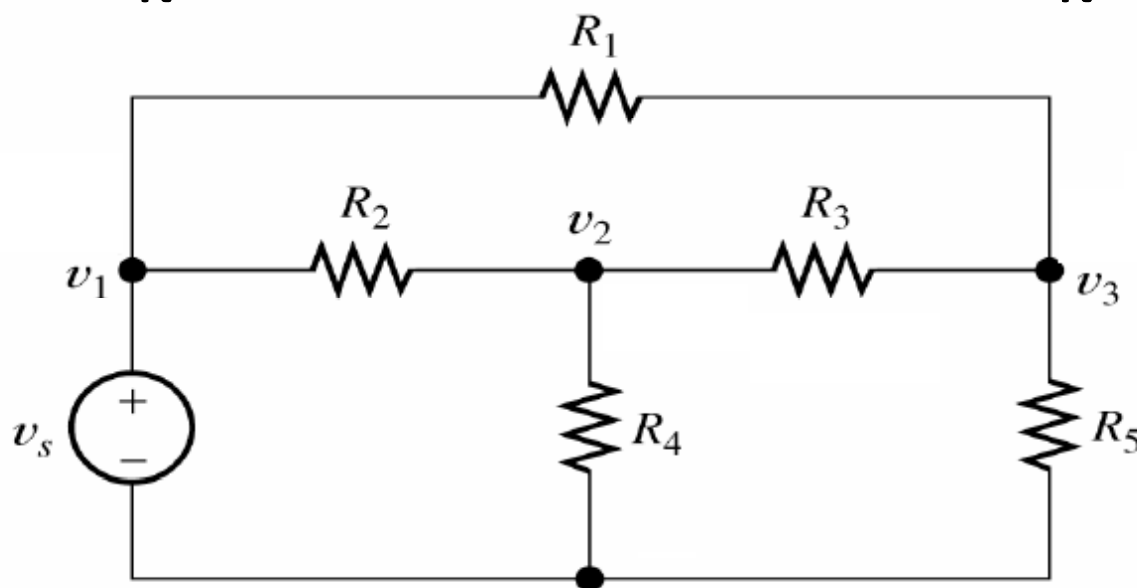**Norton's Theorem:** Any network containing independent and dependent sources and resistors, when viewed from the load, can be represented by an **equivalent current source**  $I_N$  in shunt with an **equivalent resistance**  $R_N$


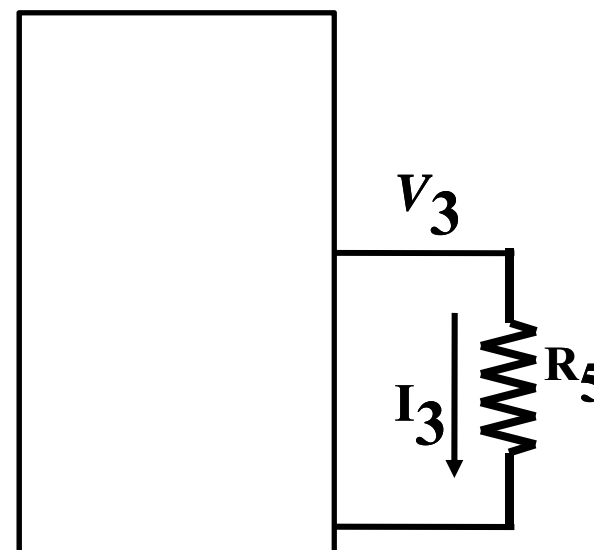
$$R_{Th} = R_1 \parallel (R_3 + R_2 \parallel R_4)$$





### **Thevenin's (Voltage Source) & Norton's (current Source) equivalent circuits:**

#### **Thevenin's Theorem:**



- Any network containing independent and dependent sources and resistors, when viewed from the load, can be represented by an **equivalent voltage source**  $V_{Th}$  in series with an **equivalent resistance**  $R_{Th}$ .


The Thevenin voltage  $V_{Th}$  is also referred to as the **Open-Circuit Voltage** ( $V_{oc}$ ).

$R_{Th}$  is defined as the **effective resistance of the** network, looking from the two open-circuited terminals.
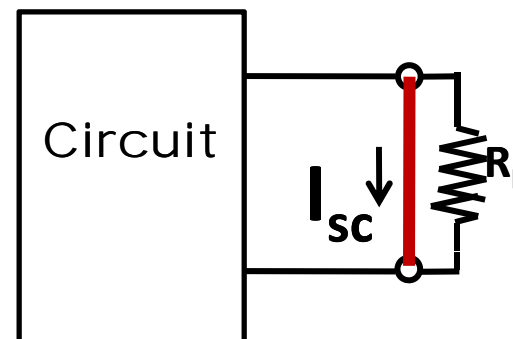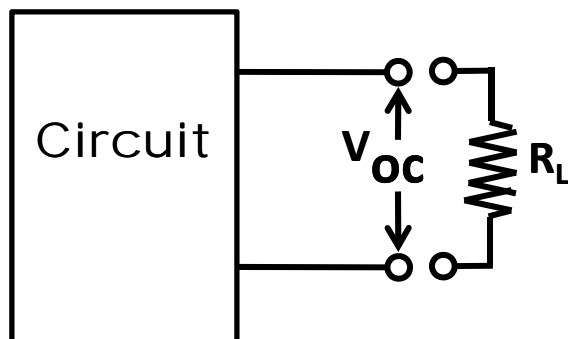
#### **Norton's Theorem:**

- Any network containing independent and dependent sources and resistors, when viewed from the load, can be represented by an **equivalent current source**  $I_N$  in shunt with an **equivalent resistance**  $R_N$ . But value of  $R_N = R_{Th}$  and  $I_N$  is referred to as the **Short circuit Current** ( $I_{sc}$ ).



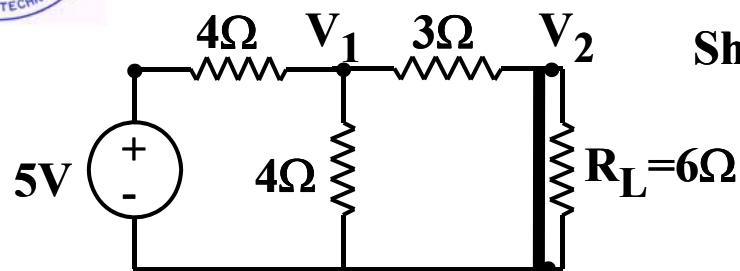


$$R_{Th} = 3 + 4 \parallel 4 = 5\Omega, V_{oc} = (5/8) \times 4 = 2.5V$$

Short  $R_L$  :  $I_{sc} = I_{3\Omega} \big|_{V_2=0}$  and apply KCL at node 1.

$$\frac{V_1 - 5}{4} + \frac{V_1}{4} + \frac{V_1}{3} = 0$$

$$0.833 \times V_1 = 1.25, I_3 = I_{sc} = \frac{V_1}{3} = \frac{1.5}{3} = 0.5A$$

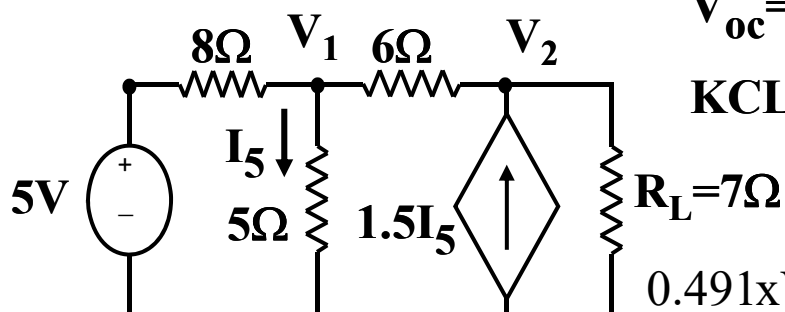Sure,  $V_{oc}/I_{sc}$  give the same value of  $R_{Th} = 5\Omega$



$V_{oc} = V_2$  when  $R_L$  is taken out.

$$\text{KCL at node 1 gives : } \frac{V_1 - 5}{8} + \frac{V_1}{5} + \frac{V_1 - V_{oc}}{6} = 0$$

$$0.491 \times V_1 = (1/6)V_{oc} + (5/8)$$

$$0.491 \times V_1 = (1/6)V_{oc} + (5/8)$$

$$V_1 = 0.34V_{oc} + 1.27, \therefore V_{oc} = 0.467 \times 6 \times 0.34V_{oc} + 1.27 \times 0.467 \times 6$$

$$V_{oc} = \frac{1.27 \times 0.467 \times 6}{0.0473} = 75.2V$$

KCL at node 2 gives :

$$\frac{V_1 - V_{oc}}{6} + 1.5I_5 = 0$$

$$\frac{V_1 - V_{oc}}{6} + 1.5 \frac{V_1}{5} = 0$$



$$0.467 \times 6 V_1 = V_{oc}$$

when  $R_L$  is shorted  $V_2 = 0$ ,

$$\text{and } I_{sc} = 1.5I_5 + V_1/6 = 1.5(V_1/5) + V_1/6 = 0.467V_1$$


$$\text{KCL at node 1 gives: } (V_1 - 5)/8 + V_1/5 + V_1/6 = 0$$
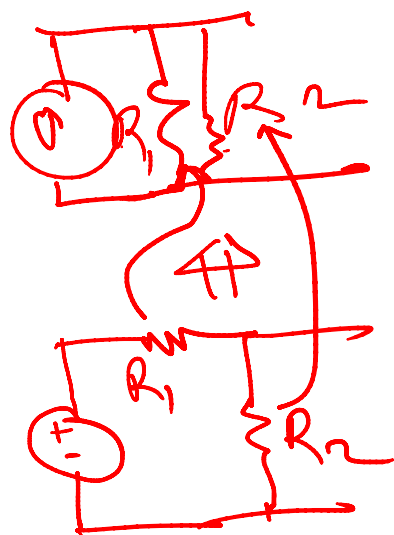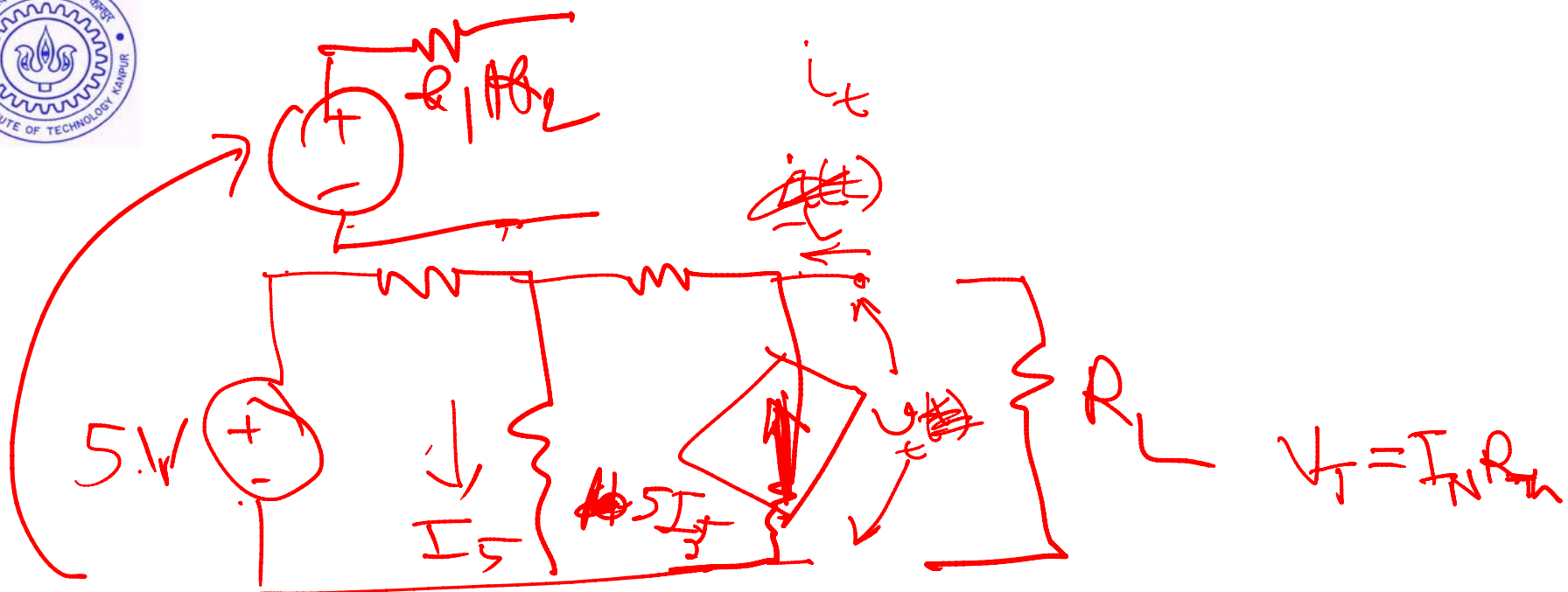
$$V_1 = (1/0.492) \times (5/8) = 1.27V \quad \text{or } I_{sc} = 0.59A, R_{Th} = 126.7\Omega$$



$$V_t \rightarrow I_t$$

$$\frac{V_t}{I_t} = R_{Th}$$

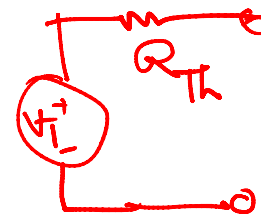

$$R_N = R_{Th}$$

