 





ESc201, Lecture 34: (Digital) Sequential Circuits **SR Latch: invalid input**

The inputs do not change simultaneously and arises a situation of $11 \rightarrow 01^* \rightarrow 00$

$Q = 0 \rightarrow 1$ and 00 input holds $Q=1$, whereas it should have held 00




 If on the other hand the inputs changed as $RS = 11 \rightarrow 10^* \rightarrow 00$




$Q = 0 \rightarrow 0$ and the 00 input holds $Q = 0$, whereas it should have held 00.


SR Latch: gate delays

 

If gate-1 is faster

 

$Q = 1$

 


S	R	Q	\bar{Q}	State
1	0	1	0	SET
0	1	0	1	RESET
0	0	Q	\bar{Q}	HOLD
1	1	0	0	INVALID




ESc201, Lecture 34: (Digital) Sequential Circuits **SR Latch: gate delays**

On the other hand if gate-2 is faster.

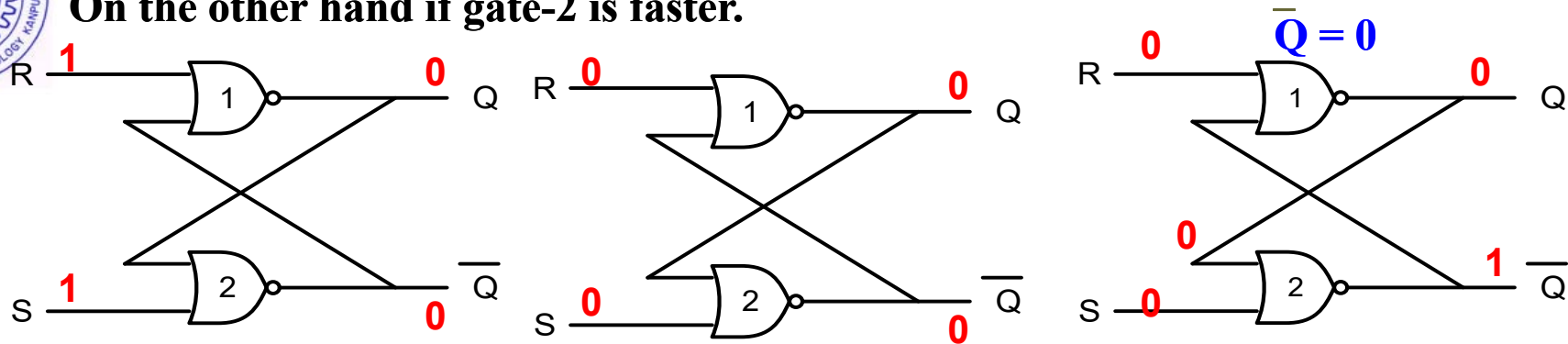



Again the output is, in general, unpredictable.

 So although output is well defined when $RS = 11$ is applied, it becomes unpredictable once the inputs are switched to the latch-hold state by applying $RS=00$. That is why $RS=11$ is not used as an input. Use Enable Or Clock.



S	R	Q	\bar{Q}	State
0	1	1	0	SET
1	0	0	1	RESET
1	1	Q	\bar{Q}	HOLD
0	0	1	1	INVALID

Hold State

 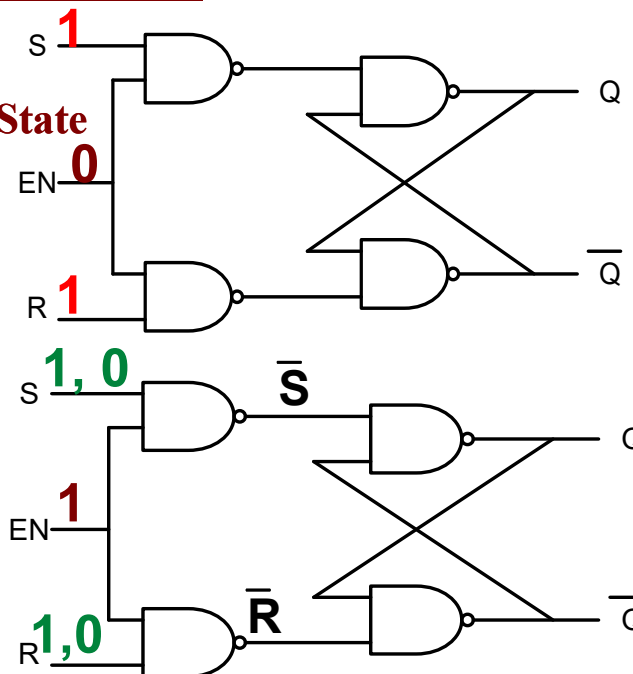

Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid




ESc201, Lecture 34: (Digital) Sequential Circuits **D-FlipFlop**


For the inputs **S** and **R** never to show up as 1, 1 one might make sure that one input is invert of the other by using a NOT or i-input NAND gate.

Enable	S	R	Q	\bar{Q}	State
0	x	x	Q	\bar{Q}	Hold
1	1	0	1	0	Set
1	0	1	0	1	Reset
1	0	0	Q	\bar{Q}	Hold
1	1	1	0	0	Invalid

 
So the D-Flip-Flop just transfers the data for storage with a delay of one Ck cycle.



Positive edge triggered flipflop

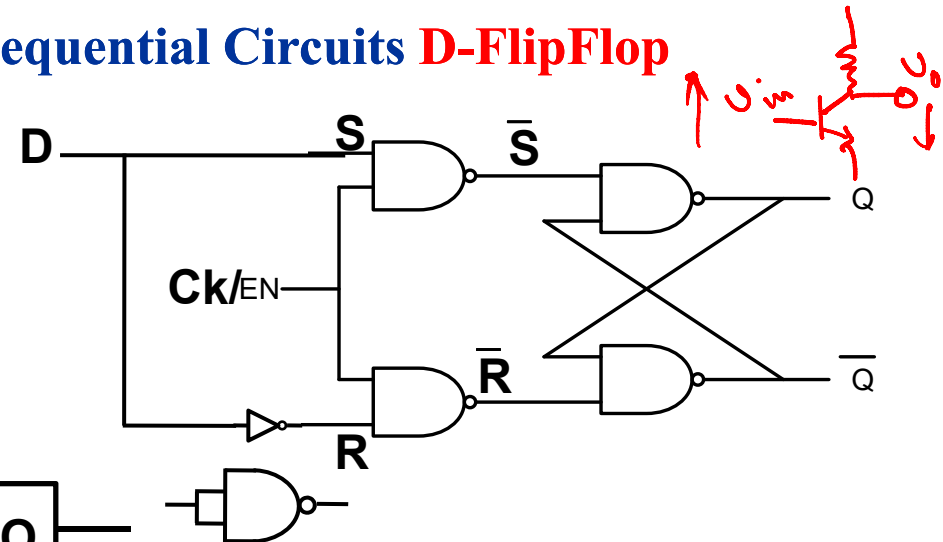

 As long as $Ck=0$, the output Q , \bar{Q} holds. The input D is only sampled at the arrival of the Ck pulse. If $D=0$, $Q=0$, $\bar{Q}=1$. If at the next Ck pulse the input has changed to $D=1$, then the output switches to $Q=1$, $\bar{Q}=0$. Sometimes called **gated D-Latch**.



Negative edge triggered flipflop



ESc201, Lecture 34: (Digital) Sequential Circuits **JK-FlipFlop**


To remove the ambiguity faced in SR-flipflop a **feedback** is required from the complementary output to the additional AND gate used for the clock.

J (Jack) and K (Kilby) are the input states for the JK flip-flop.

Q_n	J	K	Q_{n+1}	Q_{n+1}
0	0	0	0	Q_n
0	0	1	0	Q_n
0	1	0	1	\bar{Q}_n
0	1	1	1	\bar{Q}_n
1	0	0	1	Q_n
1	0	1	0	\bar{Q}_n
1	1	0	1	Q_n
1	1	1	0	\bar{Q}_n



Q_n is the output at the n^{th} clock pulse.

J_n	K_n	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	\bar{Q}_n

 

Ambiguity Removed: The last line gives a new T-flipflop.

  Not a very good example where \bar{Q} comes out of the 'S' input NOR gate.



T-flipflop is supposed to Toggle at each clock pulse if the input T is 1, or hold if input is 0.

$$Q_{n+1} = T \oplus Q_n$$

Q_n	T	Q_{n+1}
0	0	0
0	1	1
1	0	1
1	1	0




ESc201, Lecture 34: (Digital) Sequential Circuits JK Master-Slave

All worries over? ---- Not quite. Technology comes into play.

For $J=1, K=1$ if the it is positive edge triggered, as soon as the clock arrives the output state toggles after two NAND gate delays (Δt).

 If the clock pulse is t_p and $t_p < \Delta t$, then no problem. However, if $t_p > \Delta t$, then J & K being still held at 1, the output will toggle again. This sets a **race around** condition. So the final state of the output after the end of the clock pulse is unknown.




Q_n	J	K	Q_{n+1}	Q_{n+1}
0	0	0	0	Q_n
0	0	1	0	Q_n
0	1	0	1	\bar{Q}_n
0	1	1	1	\bar{Q}_n
1	0	0	1	Q_n
1	0	1	0	\bar{Q}_n
1	1	0	1	Q_n
1	1	1	0	\bar{Q}_n

CLOCK	J	K	$\overline{\text{SET}}$	$\overline{\text{RESET}}$	Q	\bar{Q}
-	-	-	0	1	1	0
-	-	-	1	0	0	1
$\overline{\text{L}}$	0	0	1	1	Q	\bar{Q}
$\overline{\text{L}}$	1	0	1	1	1	0
$\overline{\text{L}}$	0	1	1	1	0	1
$\overline{\text{L}}$	1	1	1	1	\bar{Q}	Q



ESc201, Lecture 34: (Digital) Sequential Circuits

Solution: JK Master-Slave

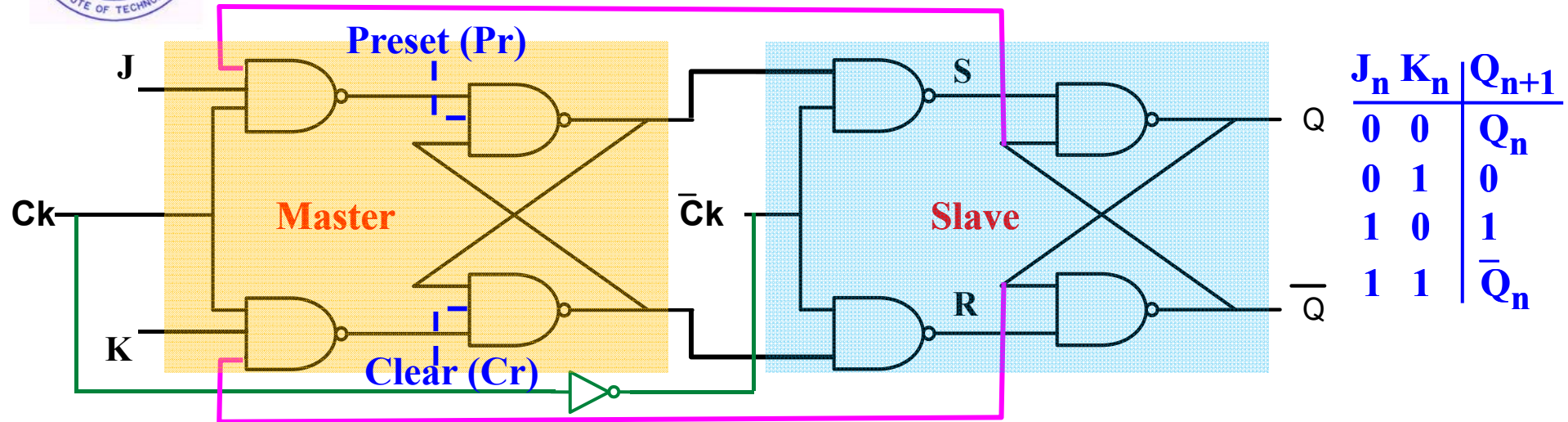

Analysis of clock sequential circuits-

1. The behavior of sequential circuit is determined from the inputs, the outputs and the states of its flip flops. Both the outputs and the next state are the function of the inputs and the present state.
2. The Analysis of sequential circuits consists of obtaining a table or a **diagram** for the time sequence of inputs, outputs and the internal states. It is also possible to write Boolean expression that describe the behavior of sequential circuits. However these expressions must include the necessary time sequence .
3. A clocked sequential circuit has one input variable X, one output variable Y and two clocked RS flip flops labeled A and B.



ESc201, Lecture 33: (Digital) 3-bit Bi-directional Shift register

RIGHT /
LEFT

Serial Data in
for right shift

Serial Data in
for left shift
D-FF

Triggering of flip flop-

1. A sequential circuit has a feedback path between the combinational circuit and the memory elements. This path can produce instability if the outputs of the memory elements are changing while the outputs of the combinational circuit that go to flip flop input are being sampled by the clock pulse.
2. One way of solving the feedback timing problem is to make the flip flop sensitive to the pulse 'transition' rather than the pulse duration (i.e. **the negative transition of clock used**).

